
Electronics for Computer Scientists

Ohm's Law to VLSI


Erik Brunvand




Why do we want to know?

- ❑ It's important to know something about computing hardware
- ❑ If only to not sound like a dummy...
 - How much power does your PC draw?
 - Why does your laptop only last a hour on a battery, but your watch lasts 2 years?
 - Why does a faster processor burn more power?
 - 700MHz is pretty fast. What are the issues in making things go faster?
 - How are logic gates built? How do they work?
 - How are logic gates used to build computing systems?
- ❑ It also lets you understand and appreciate limitations and advances in hardware

The Big Picture

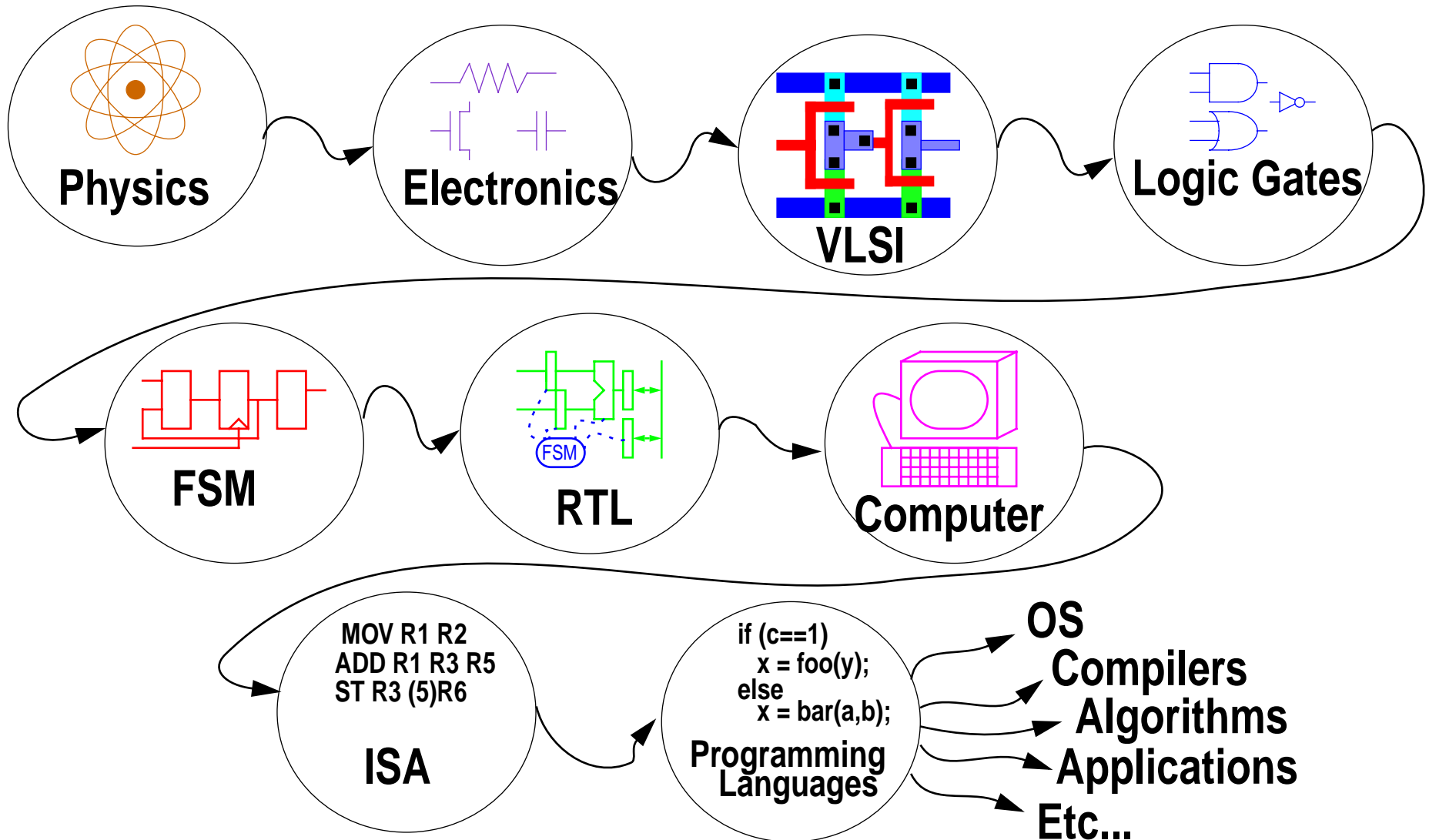

This Talk

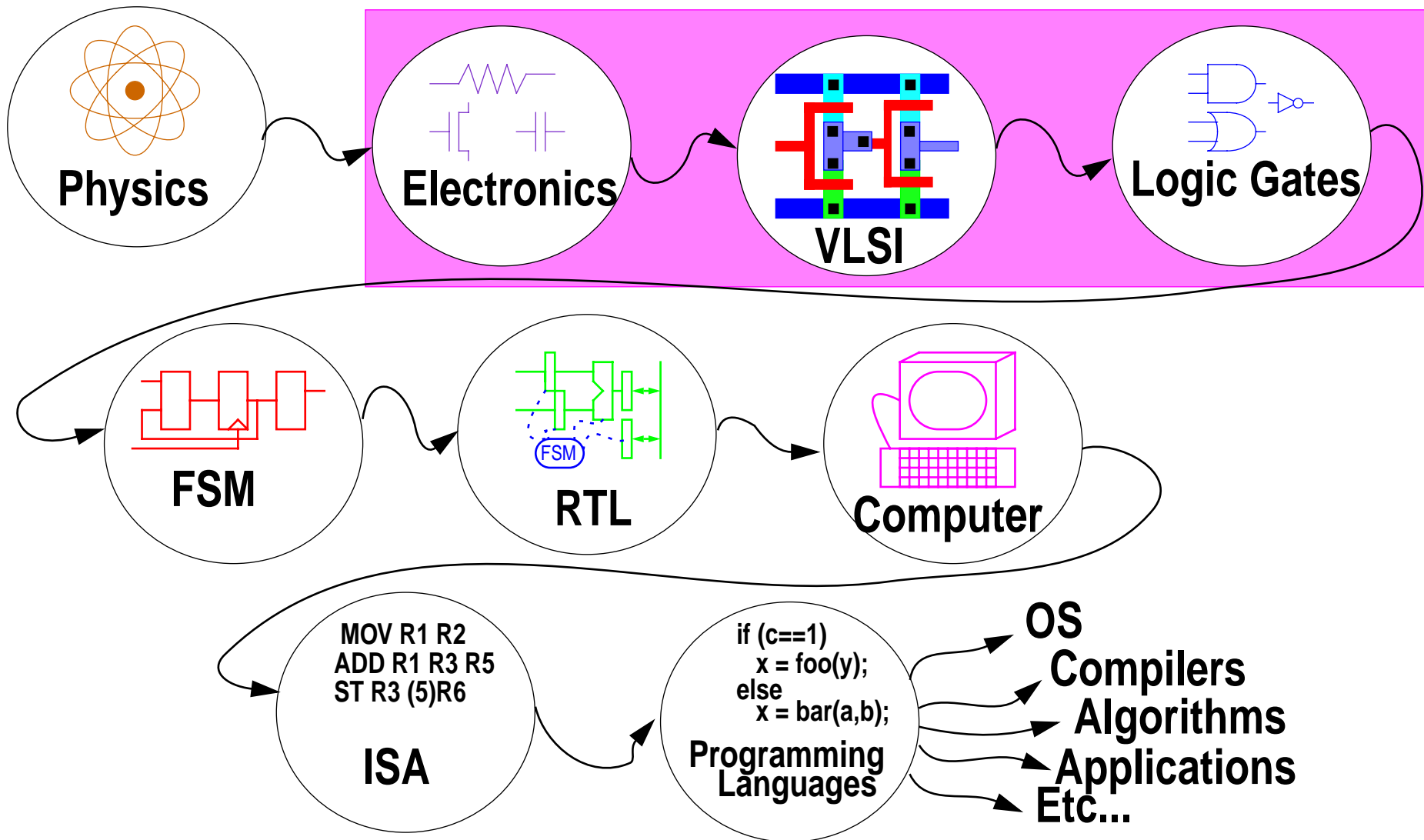

Electric Charge

❑ Atomic-level property

- Positive charge = Proton
- Negative charge = Electron

❑ Charges produce force against each other

- Like charges repel
- Different charges attract


❑ SI unit of charge is **Coulomb** (Q, q are quantity symbols)

- Charge on electron is -1.602×10^{-19} Coulombs
- 6.241×10^{18} electrons = 1 Coulomb

Electric Current

Results from charge moving in a conductor

- ❑ SI unit of current is Ampere, Amp, A (I, i are quantity symbols)
 - 1 Amp is 1 Coulomb of charge passing a point in 1 second
 - $I \text{ (Amperes)} = Q \text{ (Coulombs)} / t \text{ (seconds)}$
- ❑ Current has a direction: it flows from positive to negative points (positive current)
 - But, electrons are really the things that move in the conductor
 - And, they move from negative to positive
 - So, the electrons move in the opposite direction as current flow
 - *Blame Ben Franklin!*

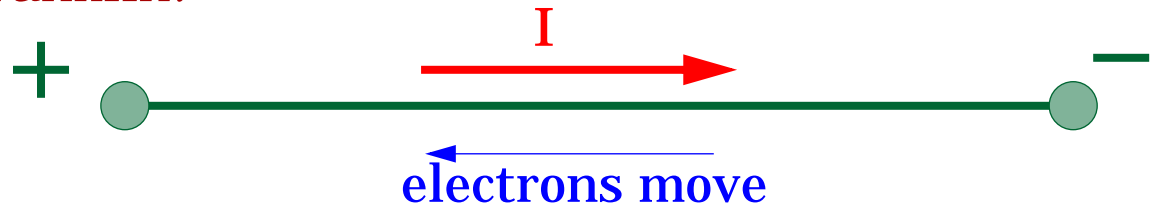

Voltage

Difference in electrical potential at two points in a circuit

- ❑ A measure of how much work is involved in moving charge between those points
 - $W \text{ (joules)} = F \text{ (newtons)} * s \text{ (meters)}$
- ❑ Energy is the capacity to do work.
 - Potential energy is energy something has because of position
 - Voltage difference is a potential difference
- ❑ Voltage is the energy that causes current to flow
 - Current flows from higher potential to lower potential

Voltage is Relative


Measured relative to two points in a system

- ❑ 1 Volt is the work required to move 1 Coulomb of charge from one point to another
 - $V_{a-b} \text{ (volts)} = W \text{ (joules)} / Q \text{ (Coulombs)}$
- ❑ Raising the voltage of one Coulomb of charge by 1 volt takes 1 joule of energy...
- ❑ One point is arbitrarily called 0v or Ground (GND)
 - Which means that voltage can easily be negative with respect to that arbitrary point

Water Analogy

- ❑ Current flow = water flow
- ❑ Amount of current = how much water
- ❑ Voltage = potential energy of the water
 - 0v = stagnant pool of water, no flow
 - Small voltage = tiny waterfall, not much energy
 - Large voltage = large waterfall, lots of energy
 - Negative voltage = dig a hole under the pond
- ❑ More water analogy later....

Lots of potential

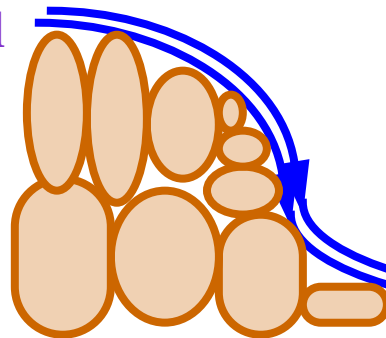

Pitiful attempt at drawing a waterfall...

Lower potential

Power

The rate at which something produces or consumes energy

$$\square P \text{ (watts)} = W \text{ (joules)} / t \text{ (seconds)}$$

$$P \text{ (watts)} = \frac{W \text{ (joules)}}{Q \text{ (coulombs)}} * \frac{Q \text{ (coulombs)}}{t \text{ (seconds)}}$$

$$P \text{ (watts)} = V \text{ (volts)} * I \text{ (Amperes)}$$


Example

- How much current flows in a light bulb from a steady movement of 10^{22} electrons in 1 hour?

$$\frac{10^{22} \text{ electrons}}{1\text{h}} * \frac{1\text{h}}{3600\text{s}} * \frac{-1.602 \times 10^{-19} \text{ C}}{1 \text{ electron}} = -0.445 \text{ C/s}$$
$$= -0.445 \text{ A}$$

Example

- How much current does a 1200w toaster draw from a 120v power connection?

$$P = V I$$


$$I = P/V = 1200\text{w}/120\text{v} = 10\text{A}$$


How fast do electrons move?

What is the “drift velocity” of an electron?

□ Example: 14 gauge copper wire, 10A current

- Copper wire has 1.38×10^{24} free electrons/in³
- 14 gauge cross section is $3.23/10^{-3}$ in²
- Electron velocity is (current)/(area * electron density)

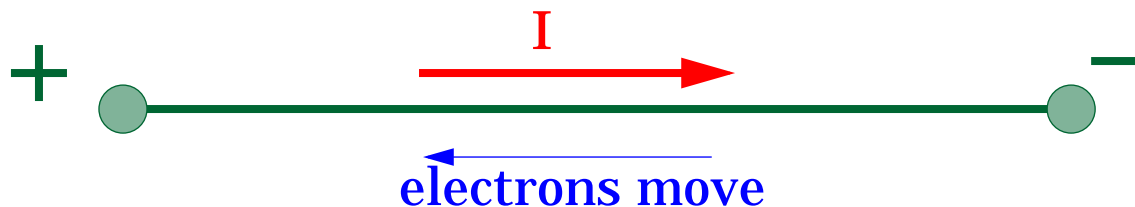Electrical impulse moves at 2.998×10^8 m/s
(i.e. close to speed of light)



How fast do electrons move?

What is the “drift velocity” of an electron?

□ Example: 14 gauge copper wire, 10A current

- Copper wire has 1.38×10^{24} free electrons/in³
- 14 gauge cross section is 3.23×10^{-3} in²
- Electron velocity is (current)/(area * electron density)

$$\text{velocity} = \frac{10\text{C}}{1\text{s}} * \frac{1}{3.23 \times 10^{-3} \text{in}^2} * \frac{1 \text{in}^3}{1.38 \times 10^{24} \text{ electrons}}$$

$$= \frac{10\text{C}}{1\text{s}} * \frac{1}{3.23 \times 10^{-3} \text{in}^2} * \frac{1 \text{in}^3}{1.38 \times 10^{24} \text{ electrons}} * \frac{0.0254\text{m}}{1\text{in}} * \frac{1 \text{ electron}}{-1.602 \times 10^{-19} \text{C}}$$

$$= -3.56 \times 10^{-4} \text{ m/s} * 3600 \text{s/h} = -1.28 \text{m/h} \quad (\text{Very slow!!!})$$

Resistance

The property that opposes or resists current flow

❑ Water analogy:

- friction of water in a small pipe

❑ Electronics:

- Electrons collide with conductor atoms and lose energy in the form of heat

❑ Current is proportional to applied voltage

- Unit is the Ohm, symbol is Ω
- Ohm's Law: $I \text{ (amps)} = V \text{ (volts)} / R \text{ (Ohms)}$
- $I = V/R$ or $V = I R$

Resistance of Materials

Proportional to length
inversely proportional to cross-section area

- ❑ Big Pipe = less force (voltage) required to push water (current) through
- ❑ Little Pipe = more force (voltage) required to force the same amount of current through
 - Resistance = $\rho (L / A)$ where ρ is “resistivity” in Ωm

Material	Resistivity	Material	Resistivity
Silver	1.64×10^{-8}	Nichrome	100×10^{-8}
Copper	1.72×10^{-8}	Silicon	2500
Aluminum	2.83×10^{-8}	Quartz	10^{17}

(note, this property is measurable over 25 orders of magnitude!)

Example

- Given a 240v heating element in a stove that has $24\ \Omega$ resistance, what fuse to use?
 - Fuse must be able to carry the current of the heating element
 - $I = V / R = 240\text{v} / 24\Omega = 10\text{A}$
- How much power does this heating element dissipate?
 - Recall $P = V I$, and $V = I R$, so $P = I^2 R$
 - So $P = 10^2 * 24\text{W} = 2400\ \text{W}$

Example

□ What is the resistance of an Al wire 1000m long with diameter 1.626mm?


- Cross sectional area = Πr^2 , $r = d/2 = 0.813 \times 10^{-3} \text{m}$
- $R \text{ (ohms)} = \rho (L / A)$

$$= \frac{(2.83 \times 10^{-8} \Omega \text{m}) (1000 \text{m})}{\Pi (0.813 \times 10^{-3} \text{m})^2} = 13.6 \Omega$$

Series and Parallel Connections of Resistors

❑ Resistors in series = more total resistance

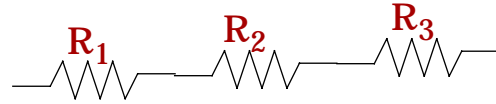
- $R_{\text{tot}} = R_1 + R_2 + \dots + R_n$



❑ Resistors in parallel = less total resistance

❑ Think about conductance as the inverse of resistance

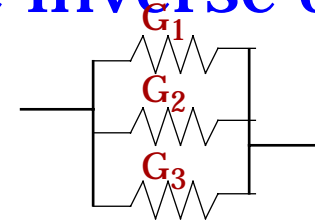- G (conductance) = $1 / R$ (resistance)
- $G_{\text{tot}} = G_1 + G_2 + \dots + G_n$
- $= 1/R_1 + 1/R_2 + \dots + 1/R_n$
- So, $R_{\text{tot}} = 1 / G_{\text{tot}} = 1 / (1/R_1 + 1/R_2 + \dots + 1/R_n)$



❑ Example, in case of 2 parallel resistors


- $R_{\text{tot}} = (R_1 * R_2) / (R_1 + R_2)$

Series and Parallel DC Circuits

- ❑ Series connected:
 - All components see the same current
- ❑ Parallel connected:
 - All components see the same voltage drop
- ❑ Loop: A simple closed path in the circuit
- ❑ Brings us to Kirchhoff's Laws...

Kirchhoff's Voltage Law (KVL)


- Sum of voltages around a loop is 0

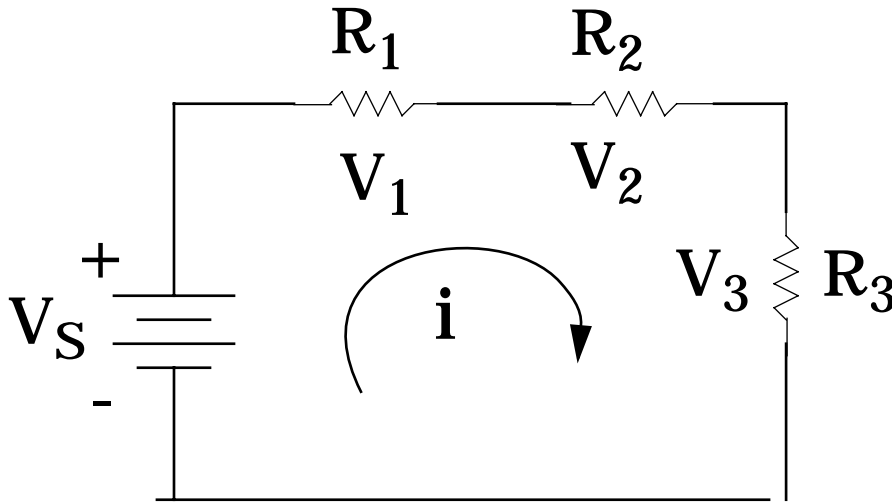

$$V_S = V_1 + V_2 + V_3 = I R_1 + I R_2 + I R_3 = I R_{\text{tot}}$$

Voltage Division

- Find V_2 , the voltage drop across R_2

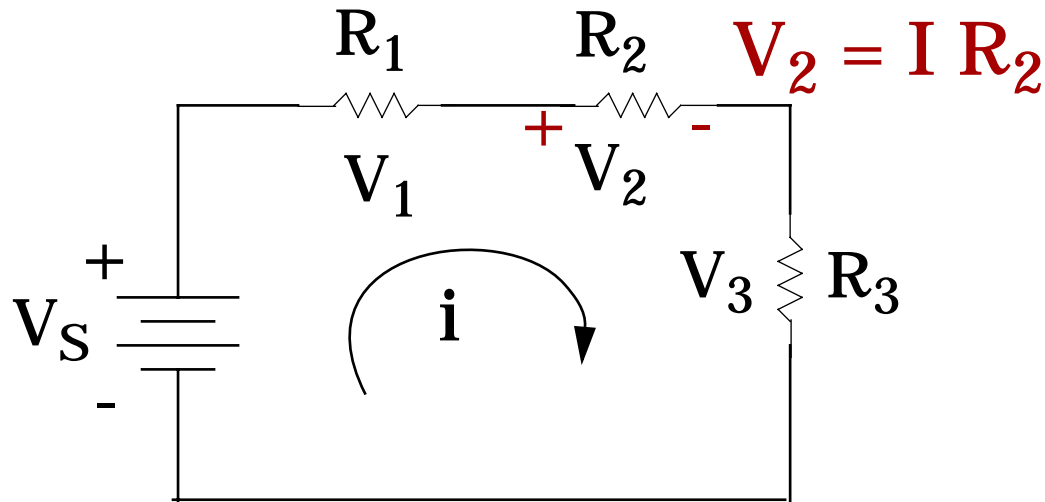

$$V_S = V_1 + V_2 + V_3 = I R_1 + I R_2 + I R_3 = I R_{\text{tot}}$$

$$I = V_S / (R_1 + R_2 + R_3)$$

$$\text{So } V_2 = \frac{R_2}{R_1 + R_2 + R_3} V_S$$

Voltage Division General Form


- Find voltage across any series-connected resistor

The diagram shows the voltage division formula $V_X = \frac{R_X}{R_{tot}} V_S$ with green text labels and arrows pointing to the variables:


- V_X : Voltage across resistor X
- R_X : Resistance of resistor X
- R_{tot} : Total series resistance
- V_S : Total voltage

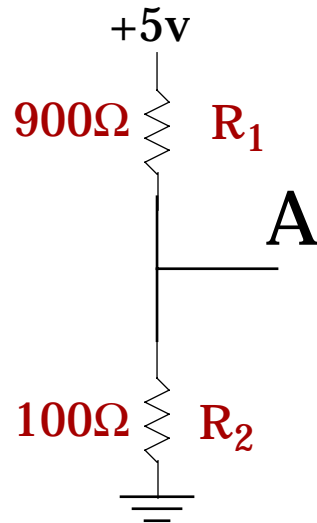Example of Voltage Division

- Find voltage at point A with respect to GND



$$V_X = \frac{R_X}{R_1 + R_2} V$$

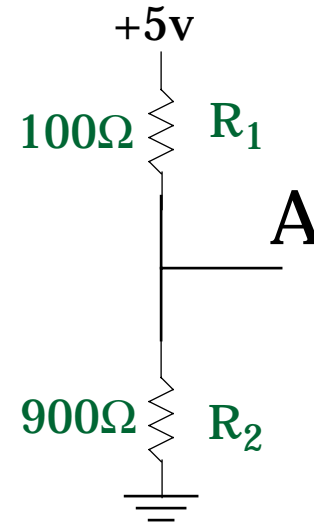

$$V_1 = (900/1000) 5\text{v} = 4.5\text{v}$$

$$V_2 = (100/1000) 5\text{v} = 0.5\text{v}$$

$$\text{So, } V_{A-\text{GND}} = 0.5\text{v}$$


$$V_1 = (100/1000) 5\text{v} = 0.5\text{v}$$

$$V_2 = (900/1000) 5\text{v} = 4.5\text{v}$$

$$\text{So, } V_{A-\text{GND}} = 4.5\text{v}$$

Kirchhoff's Current Law

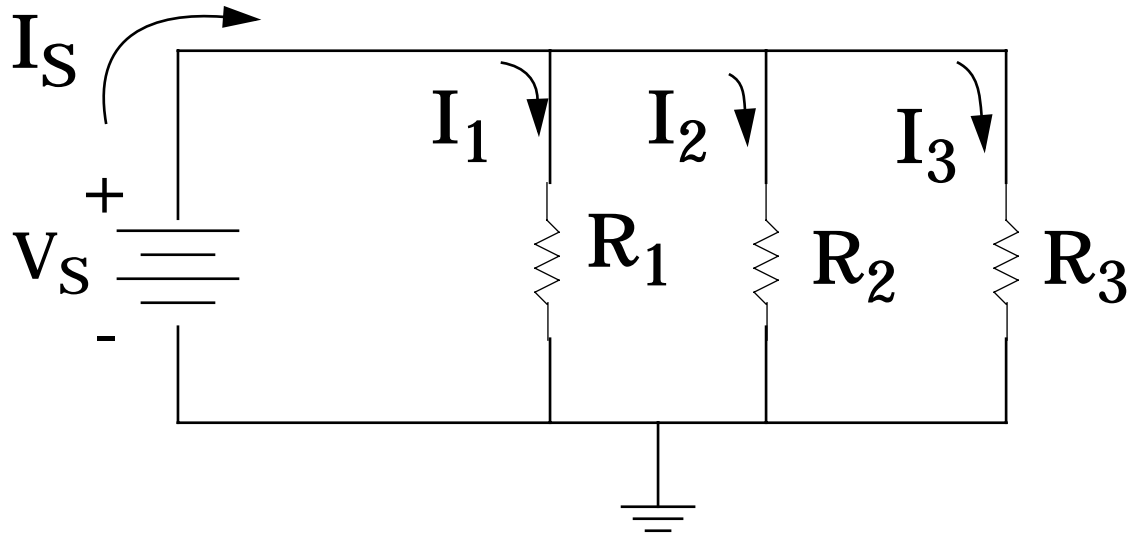- Sum of currents at any node in a circuit is 0



$$I_S = I_1 + I_2 + I_3$$

Example: Current limiting

- ❑ Suppose you had a 20w horn from an old 6v car
- ❑ Want to put it in a new car with 12v system
- ❑ How do you make it work?
 - $P = V I$ so if you increase the voltage without limiting current, the power goes up and the horn burns out
 - So, you need to limit the total current so that the horn sees the same current it was designed for
 - How? $I = V / R$, so if V goes up, R must also go up to keep current constant
 - So, what size resistor should you put in series with the horn to make this work?


Example: Current Limiting

- ❑ First compute how much current the horn would have seen in the 6v car


- $P = VI$ so $I = P / V = 20\text{w} / 6\text{v} = 3.33\text{A}$

- ❑ So, the series resistor should see the same current

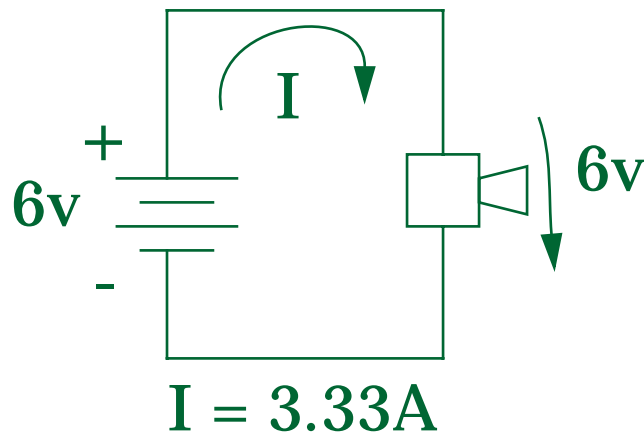- $R = 6\text{v} / 3.33\text{A} = 1.8\Omega$



Original System

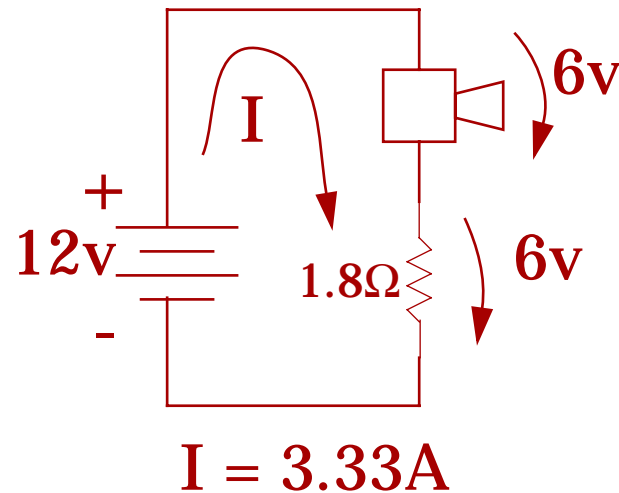


New System

Capacitors

Components that store electrical charge

❑ Two conductors separated by an insulator

- Accumulates charge on the plates

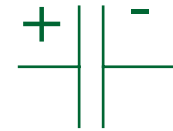

❑ SI unit is Farad

- $C \text{ (farads)} = Q \text{ (Coulombs)} / V \text{ (volts)}$
- Capacitance of 1 farad means that putting +1 and -1 coulomb of charge on the plates results in a voltage difference of 1 volt
- Or, a voltage of 1 volt forces 1 coulomb of charge on a capacitor


❑ Farad is *much* too large to be useful!

- μF and pF are more common

Series and Parallel Capacitors


□ Parallel connection: stores more charge

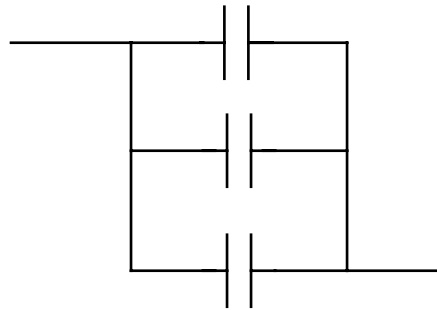- $C_{\text{tot}} = C_1 + C_2 + \dots + C_n$



□ Series connection: each plate steals charge from neighbor, so total capacitance is less

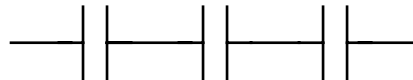
- $C_{\text{tot}} = 1 / (1 / C_1 + 1 / C_2 + \dots + 1/C_n)$



Charging a Capacitor

Each electron that comes in one lead “pushes” one electron from the other plate through the other lead

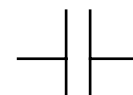□ Changing the voltage across a capacitor requires changing the charge stored on each plate, which requires current



- In a resistor, fixed current causes a fixed voltage drop: $I = Q / t$
- In a capacitor, a fixed current causes a steadily increasing voltage drop as charge accumulates on the plates: $i = dq / dt$
- We can't change voltage instantly across a capacitor because that would require infinite current!

$$q = cv$$

But c is constant, so

$$i = \frac{dq}{dt} = \frac{d}{dt}(cv)$$


$$i = c \frac{dv}{dt}$$

$$\frac{dv}{dt} = \frac{i}{c}$$

Time to Charge a Capacitor

Initially very fast, then slows down exponentially

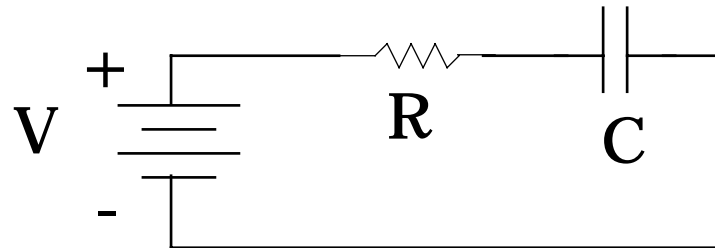
- ❑ Precise relationship depends on both R and C
- ❑ R (ohms) * C (farads) = what unit?
 - Answer: t (seconds)!
 - $R = V / I$
 - $I = Q / t$
 - $C = Q / V$
 - So, $R C = (V) / (Q / t) * Q / V = (V)(t / Q)(Q / V) = t$



RC Time Constant

□ Charging and discharging are exponential processes

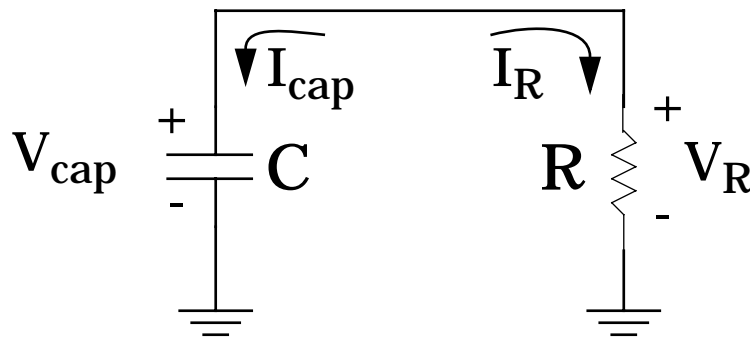- Changing the voltage across a capacitor requires current
- If the current flows through a resistor, it requires voltage across that resistor
- If voltage decreases as the capacitor discharges, the current, and the rate of discharging decrease exponentially with time
- Consider discharging a fully charged capacitor



Discharging a Capacitor

□ According to Kirchhoff:

- $V_R = V_{\text{cap}}$, and $I_R = -I_{\text{cap}}$

□ Also:


- $I_R = V_R / R$, and $dV_{\text{cap}} / dt = I_{\text{cap}} / C$

□ Substituting, we get:

- $dV_{\text{cap}} / dt = I_{\text{cap}} / C = -I_R / C = -V_{\text{cap}} / RC$

□ Solving this differential equation:

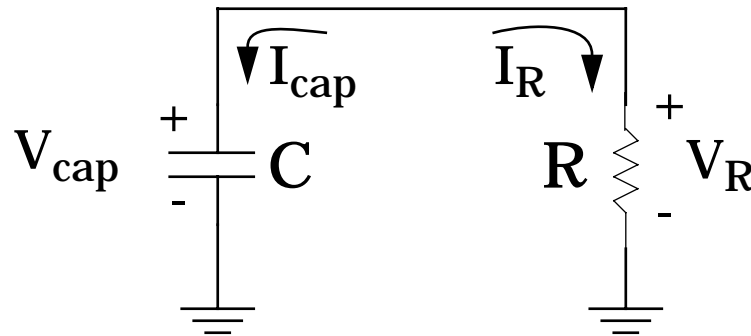- $V_{\text{cap}}(t) = V_{\text{cap}}(0) * e^{-t/RC} = V_{\text{cc}} * e^{-t/RC}$



RC Time Constants

❑ General form:

- $V_{(t)} = V_{(oo)} + [V_{(0)} - V_{(oo)}] e^{-t/RC}$

❑ Discharge from V_{cc} :

- $V_{(t)} = V_{cc} e^{-t/RC}$

❑ Charge from GND:

- $V_{(t)} = V_{cc} (1 - e^{-t/RC})$

❑ Short cut:


- 99% of final charge or discharge in $5RC$!

Example: RC Timer

*Switch connects 300v, 16M Ω resistor,
uncharged 10 μ F capacitor*

□ How long is switch closed if charge on capacitor is 10v?

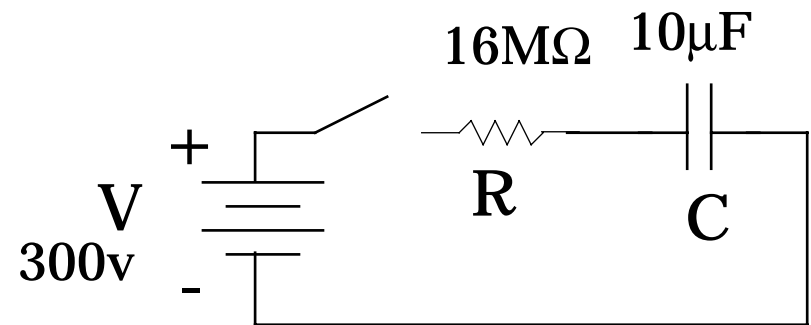- Charging equation: $V_{(t)} = V_{cc} (1 - e^{-t/RC})$
- $RC = 16,000,000 \Omega * 10 \times 10^{-6} F = 160s$, $V_{(t)} = 10v$, $V_{cc} = 300v$
- So, $10v = 300v (1 - e^{-t/160s})$
- $300 - 10 = 300 * e^{-t/160}$
- $290/300 = e^{-t/160}$
- $\ln(290/300) = \ln(e^{-t/160})$
- $\ln(290/300) = -t/160$
- $t = -160 \ln(290/300)$
- $t = 5.42s$



Energy Stored in a Capacitor

□ Work must be done to separate charge

- This energy is stored in the system and can be recovered by allowing the charge to come together again
- I.e. a charged capacitor has potential energy equal to the work required to charge it

□ Suppose at time t a charge of $q(t)$ has been transferred from one plate to the other

- The potential difference $V(t)$ at this point is $Q(t) / C$
- If an extra increment of charge dq is transferred, the extra work is $dw = V dq = (q/c)dq$

□ So, the total work to move all the charge is

$$w = \int dw = \int_0^q (q/c) dq = 1/2 q^2 / c$$

□ Since $q = cv$, $w = (1/2) cv^2$


Whew! Electronics Summary...

- ❑ Voltage is a measure of electrical potential energy
- ❑ Current is moving charge caused by voltage
- ❑ Resistance reduces current flow
 - Ohm's Law: $V = I R$
- ❑ Power is work over time
 - $P = V I = I^2 R$
- ❑ Capacitors store charge
 - It takes time to charge/discharge a capacitor
 - Time to charge/discharge is related exponentially to RC
 - It takes energy to charge a capacitor
 - Energy stored in a capacitor is $(1/2) C V^2$

How Does All This Relate To VLSI?


□ Recall the voltage division example:

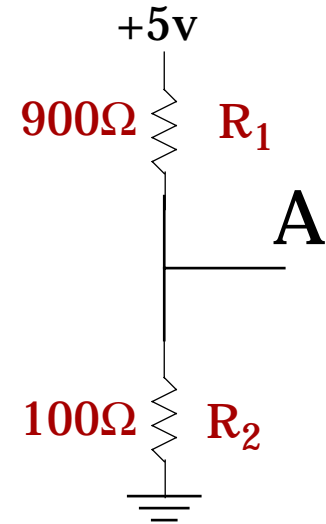- Consider what we could do if we had a device that we could switch from high resistance to low resistance
- We could use it to force **A** high or low depending on the relative resistance of the elements




□ This is a transistor

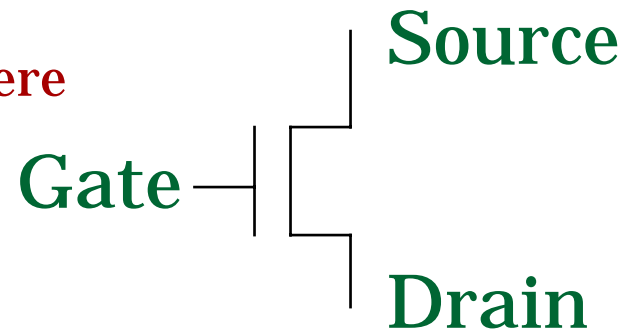
- Specifically a CMOS FET
- Complementary Metal-Oxide Semiconductor Field Effect Transistor
- If voltage on Gate is high, then there is a low-resistance between Source and Drain, otherwise it's a very high-resistance




Electrical Model of a CMOS Transistor

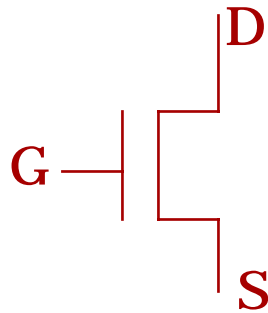

Switch Level Model

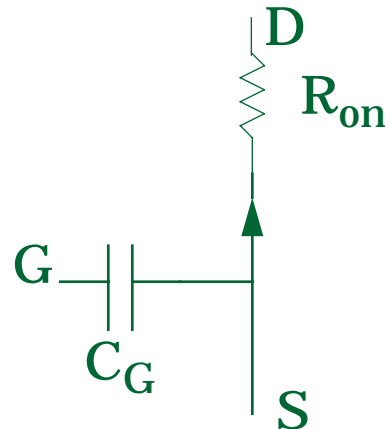

Switch is closed
if Gate voltage is
high

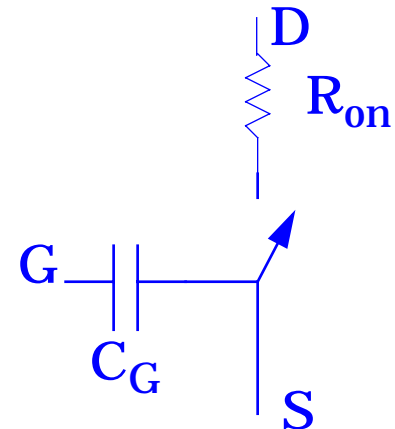

Switch is open
if Gate voltage is
low


R_{on} = Some resistance in FET itself

C_G = Capacitance of the gate

Two Types of CMOS Transistors


□ N-type transistor

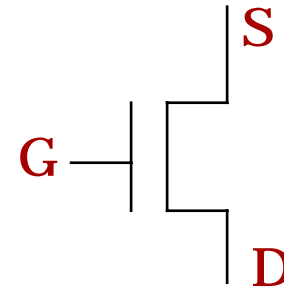- High voltage on Gate connects Source to Drain
- Passes 0 well, passes 1 poorly




□ P-type transistor

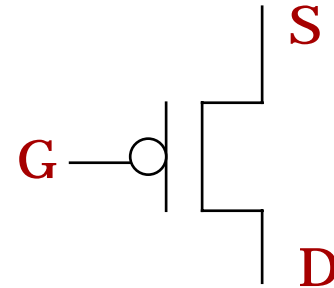- Low voltage on Gate connects Source to Drain
- Passes 1 well, passes 0 poorly




CMOS Inverter

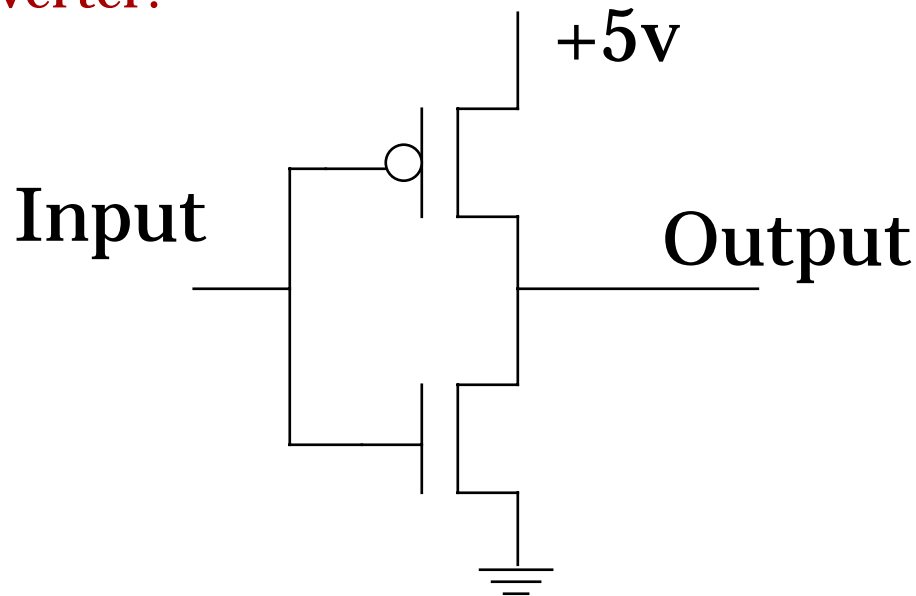- ❑ Consider this connection of transistors
 - If input is at a high voltage, output is low
 - If input is at a low voltage, output is high
- ❑ By changing the resistances, it becomes one of two different voltage dividers
 - It's a voltage inverter!




Timing Issues in CMOS

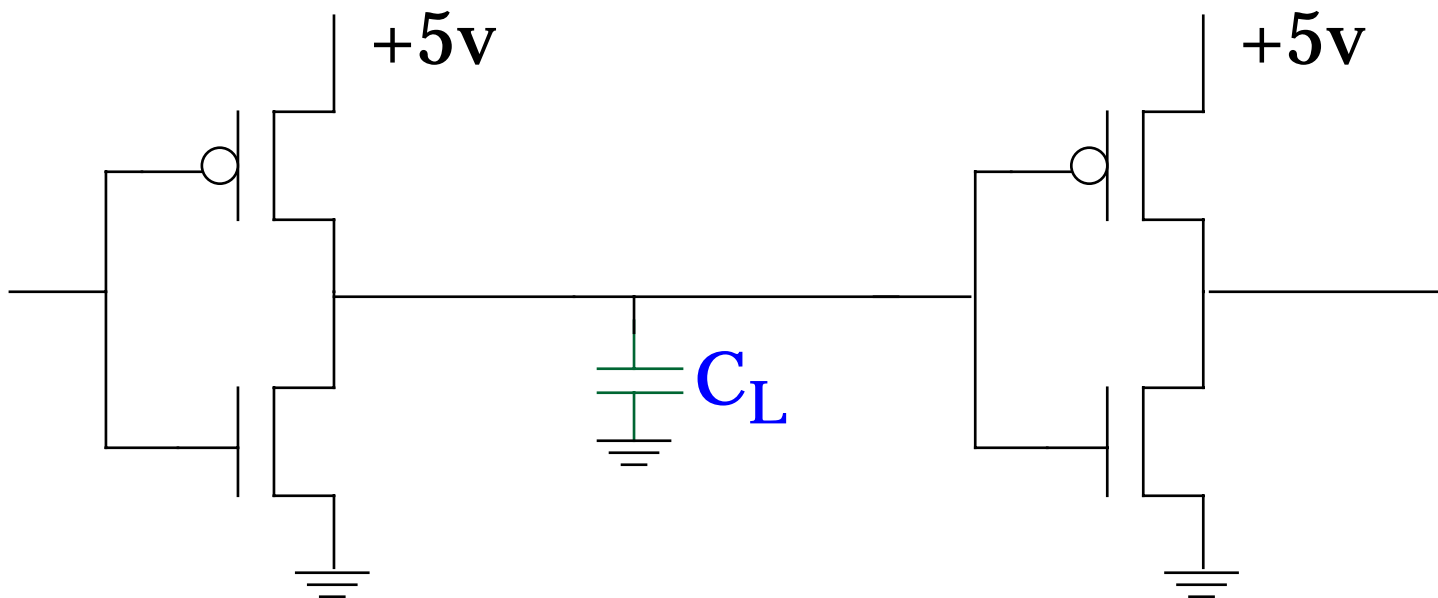- ❑ Recall that it takes time to charge capacitors
- ❑ Recall that the gate of a transistor looks like a capacitor
- ❑ Wires have resistance and capacitance also!




CMOS NAND Gate

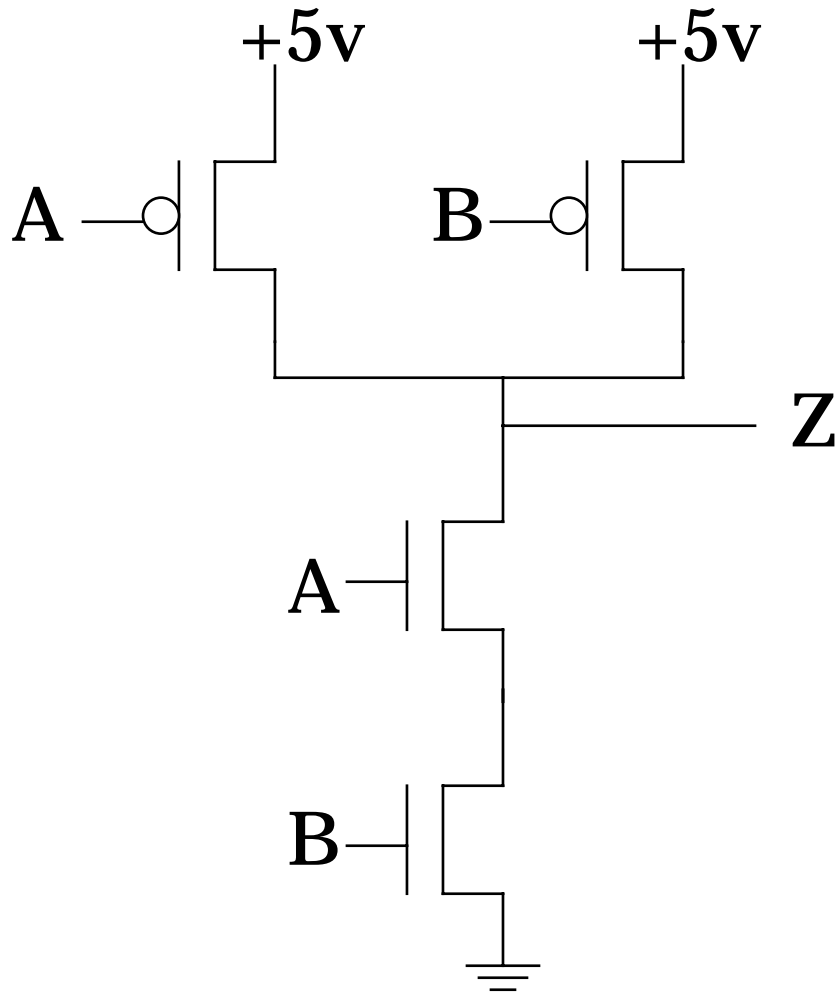


A	B	Z
0	0	1
0	1	1
1	0	1
1	1	0



CMOS NOR Gate

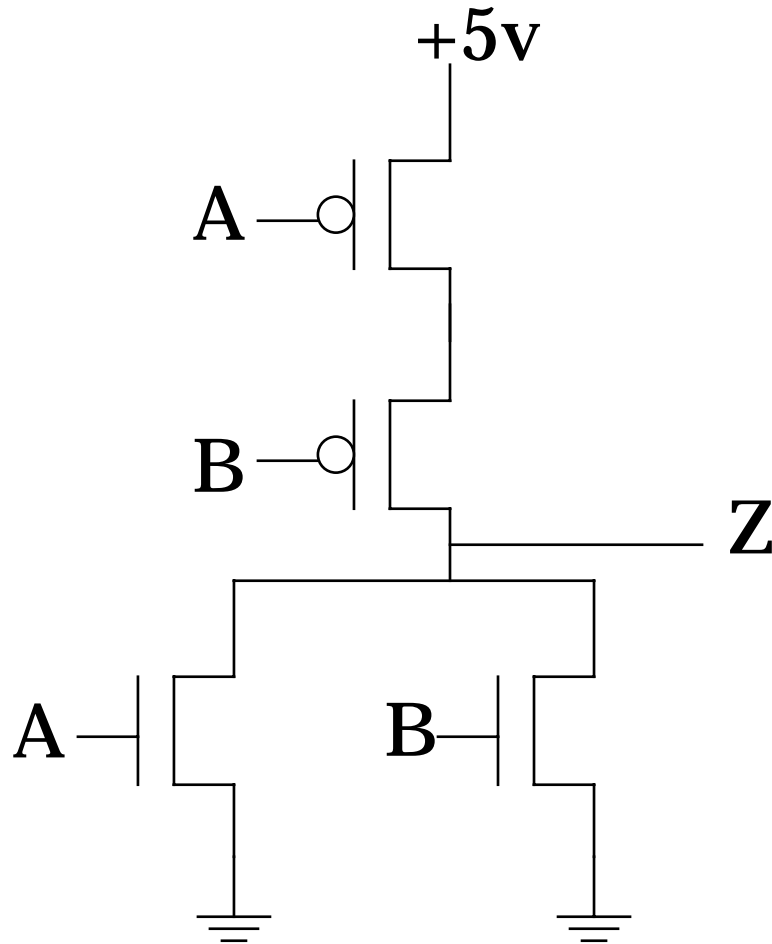

A	B	Z
0	0	1
0	1	0
1	0	0
1	1	0

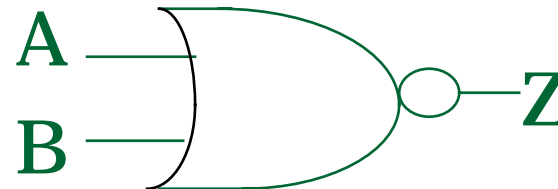

CMOS Power Consumption

- ❑ Power is consumed in CMOS by charging and discharging capacitors
 - Note that there no static power dissipation in CMOS
 - There's never a DC path to ground
- ❑ Good news:
 - You're not consuming power unless you're switching
- ❑ Bad news:
 - Switching activity is caused by clock, which is going faster and faster
- ❑ If the first-order power effect is capacitor charging/discharging, and the clock causes this:

$$P = (1/2) C V^2 f$$

Is That All There is to VLSI?

- ❑ We've got NAND, NOR, and INV gates
 - With those we should be able to build anything
- ❑ We've also got some idea of why things can't go infinitely fast
 - We've got to keep charging and discharging those darn capacitors!
- ❑ We've got some idea of where and why power is consumed
 - We've got to keep charging and discharging those darn capacitors!
- ❑ And a hint why power supply voltages are getting lower
 - $P = (1/2)CV^2f$, Which one would you optimize first?

Conclusions

- ❑ That's about all I have the stamina for
 - I'll be a little surprised if we even make it through all the slides to the end!
- ❑ A little knowledge of basic electronics can explain a lot about computer hardware
- ❑ A little more knowledge about VLSI could explain even more!
 - But that's a subject for another lecture!