 


## CS/ECE 5710/6710 Digital VLSI Design



## Electronics Summary

- ♦ **Voltage** is a measure of electrical potential energy
  - ♦ **Current** is moving charge caused by voltage
  - ♦ **Resistance** reduces current flow
    - Ohm's Law:  $V = I R$
  - ♦ **Power** is work over time
    - $P = I V = I^2 R = V^2 / R$
  - ♦ **Capacitors** store charge
    - It takes time to charge/ discharge a capacitor
    - Time to charge/discharge is related exponentially to RC
    - It takes energy to charge a capacitor
    - Energy stored in a capacitor is  $(1/2)CV^2$
- Energy (joules):** work required to move one coulomb of charge by one volt or work done to produce one watt for one sec

## Reminder: Voltage Division

- Find the voltage across any series-connected resistors

$$V_X = \frac{R_X}{R_{\text{tot}}} V_S$$

Resistance of resistor X


Voltage across resistor X

Total series resistance

Total voltage

 
## Example of Voltage Division

- Find the voltage at point A with respect to GND


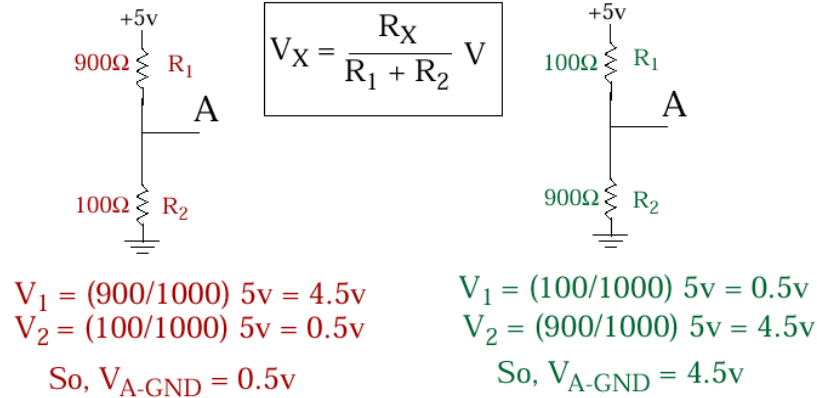
## Example of Voltage Division

- Find the voltage at point A with respect to GND





## How Does This Relate to VLSI?

### Recall the voltage division example:


- Consider what we could do if we had a device that we could switch from high resistance to low resistance
- We could use it to force A high or low depending on the relative resistance of the elements
  
### This is a transistor


- Specifically a CMOS FET
- Complementary Metal-Oxide Semiconductor Field Effect Transistor
- If voltage on Gate is high, then there is a low-resistance between Source and Drain, otherwise it's a very high-resistance




## Model of a CMOS Transistor

 

Switch Level Model

 

Switch is closed if Gate voltage is high

 

Switch is open if Gate voltage is low


$R_{on}$  = Some resistance in FET itself

$C_G$  = Capacitance of the gate

## Two Types of CMOS Transistors

 
### □ N-type transistor

- High voltage on Gate connects Source to Drain
- Passes 0 well, passes 1 poorly


 
### □ P-type transistor

- Low voltage on Gate connects Source to Drain
- Passes 1 well, passes 0 poorly





# CMOS Transistors

- ♦ Complementary Metal Oxide Semiconductor
- ♦ Two types of transistors
  - Built on silicon substrate
  - “majority carrier” devices
  - Field-effect transistors
    - An electric field attracts carriers to form a conducting channel in the silicon...
    - We’ll get much more of this later...
    - For now, just some basic abstractions
  
## Silicon Lattice


- ♦ Transistors are built on a silicon substrate
- ♦ Silicon is a Group IV material
- ♦ Forms crystal lattice with bonds to four neighbors



Figures from Reid Harrison
 
## “Semi” conductor?


- ◆ Thermal energy (atomic-scale vibrations) can shake an electron loose
  - Leaves a “hole” behind



Figures from Reid Harrison
 
## “Semi” conductor?


- Room temperature:  $1.5 \times 10^{10}$  free electrons per cubic centimeter
  - But,  $5 \times 10^{22}$  silicon atoms / cc
  - So, one out of every 3 trillion atoms has a missing  $e$



Figures from Reid Harrison
 
## Dopants


- ♦ Group V: extra electron (n-type)
  - Phosphorous, Arsenic,
- ♦ Group III: missing electron, (p-type)
  - Usually Boron



Figures from Reid Harrison
 
## Dopants


- ♦ Note that each type of doped silicon is electrostatically neutral in the large
  - Consists of mobile electrons and holes
  - And fixed charges (dopant atoms)




Figures from Reid Harrison
 
## p-n Junctions

- ♦ A junction between p-type and n-type semiconductor forms a diode.
  - Current flows only in one direction




anode      cathode

 
 
## p-n Junctions

- Two mechanisms for carrier (hole or electron) motion
  - Drift - requires an electric field
  - Diffusion - requires a concentration gradient



Figures from Reid Harrison




## p-n Junctions

- With no external voltage diffusion causes a depletion region

- Causes an electric field because of charge recombination


- Causes drift current...

 

Figures from Reid Harrison
 
## p-n Junctions


- Eventually reaches equilibrium where diffusion current offsets drift current



Figures from Reid Harrison


 
## p-n Junctions

- By applying an external voltage you can modulate the width of the depletion region and cause diffusion or drift to dominate...




Figures from Reid Harrison

## N-type Transistor

  

 
## nMOS Operation

- ◆ Body is commonly tied to ground (0 V)
- ◆ When the gate is at a low voltage:
  - P-type body is at low voltage
  - Source-body and drain-body diodes are OFF
  - No current flows, transistor is OFF




 
## nMOS Operation Cont.

- ◆ When the gate is at a high voltage:
  - Positive charge on gate of MOS capacitor
  - Negative charge attracted to body
  - Inverts a channel under gate to n-type
  - Now current can flow through n-type silicon from source through channel to drain, transistor is ON




## P-type Transistor

  

 
## pMOS Transistor

- ◆ Similar, but doping and voltages reversed
  - Body tied to high voltage ( $V_{DD}$ )
  - Gate low: transistor ON
  - Gate high: transistor OFF
  - Bubble indicates inverted behavior



 
## A Cutaway View

- ♦ CMOS structure with both transistor types


 
## Transistors as Switches


- ♦ For now, we'll abstract away most analog details...



Not Perfect Switches!

 
## “Switching Circuit”

- ♦ For example, a switch can control when a light comes on or off



 
## “AND” Circuit

- ♦ Both switch **X** AND switch **Y** need to be closed for the light to light up



 
## “OR” Circuit

- ♦ The light comes on if either **X** **OR** **Y** are closed




 
## CMOS Inverter

- Consider this connection of transistors
  - If input is at a high voltage, output is low
  - If input is at a low voltage, output is high
- By changing the resistances, it becomes one of two different voltage dividers
  - It's a voltage inverter!



 
 
## CMOS Inverter

$\begin{matrix} A & Y \\ 0 & \\ 1 & \end{matrix}$


  
## CMOS Inverter



$\begin{matrix} A & Y \\ 0 & \\ 1 & ? \end{matrix}$







## CMOS Inverter

A	Y
0	1
1	0

  


## CMOS Inverter

A	Y
0	1
1	0

  
 
## Timing Issues in CMOS

- ❑ Recall that it takes time to charge capacitors
- ❑ Recall that the gate of a transistor looks like a capacitor
- ❑ Wires have resistance and capacitance also!




## Power Consumption

- ❑ Power is consumed in CMOS by charging and discharging capacitors
  - Note that there no static power dissipation in CMOS
  - There's never a DC path to ground
- ❑ Good news:
  - You're not consuming power unless you're switching
- ❑ Bad news:
  - Switching activity is caused by clock, which is going faster and faster
- ❑ If the first-order power effect is capacitor charging/discharging, and the clock causes this:

$$P = C V^2 f$$

## CMOS NAND Gate


 


A	B	Z
0	0	1
0	1	1
1	0	1
1	1	0



## CMOS NAND Gate

A	B	Y
0	0	
0	1	
1	0	
1	1	

  



## CMOS NAND Gate

A	B	Y
0	0	1

0 1

1 0

1 1

 
 


## CMOS NAND Gate

A	B	Y
0	0	1
0	1	1



1 0

1 1

  



## CMOS NAND Gate

A	B	Y
0	0	1
0	1	1
<b>1</b>	<b>0</b>	<b>1</b>
1	1	

  


## CMOS NAND Gate

A	B	Y
0	0	1
0	1	1
1	0	1
<b>1</b>	<b>1</b>	<b>0</b>

  

## CMOS NOR Gate

 


## 3-input NAND Gate

- ♦ Y pulls low if ALL inputs are 1
- ♦ Y pulls high if ANY input is 0

Take a moment and draw what you think the transistor circuit for a 3-input NAND gate should be...

 
## 3-input NAND Gate

- ♦ Y pulls low if ALL inputs are 1
- ♦ Y pulls high if ANY input is 0



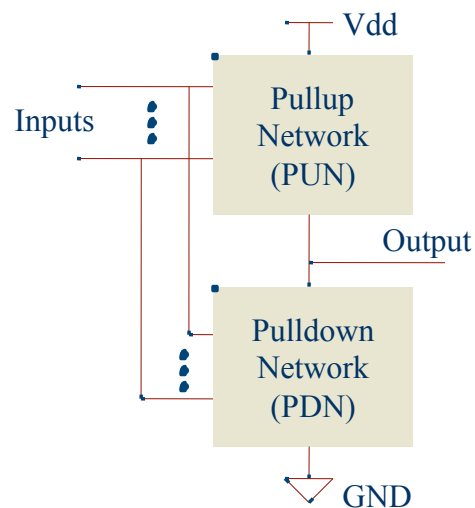
## Static CMOS Gate Template

- ♦ P-Type pullups and N-Type pulldowns
  - Boolean duals of each other...
  - Note the natural inverting behavior...
    - N-types turn on with high voltages, but pull low
    - P-types turn on with low voltages, but pull high


 
## N-type and P-type Uses

- ◆ Because of the imperfect nature of the the transistor switches
  - ALWAYS use N-type to pull low
  - ALWAYS use P-type to pull high
  - If you need to pull both ways, use them both



## Switch to Chalkboard

- ◆ Complex Gate
- ◆ Tri-State
- ◆ Latch
- ◆ D-register
- ◆ XOR