 




## Where are we?



- ▶ Lots of Layout issues
  - ▶ Line of diffusion style
  - ▶ Power pitch
  - ▶ Bit-slice pitch
  - ▶ Routing strategies
  - ▶ Transistor sizing
  - ▶ Wire sizing
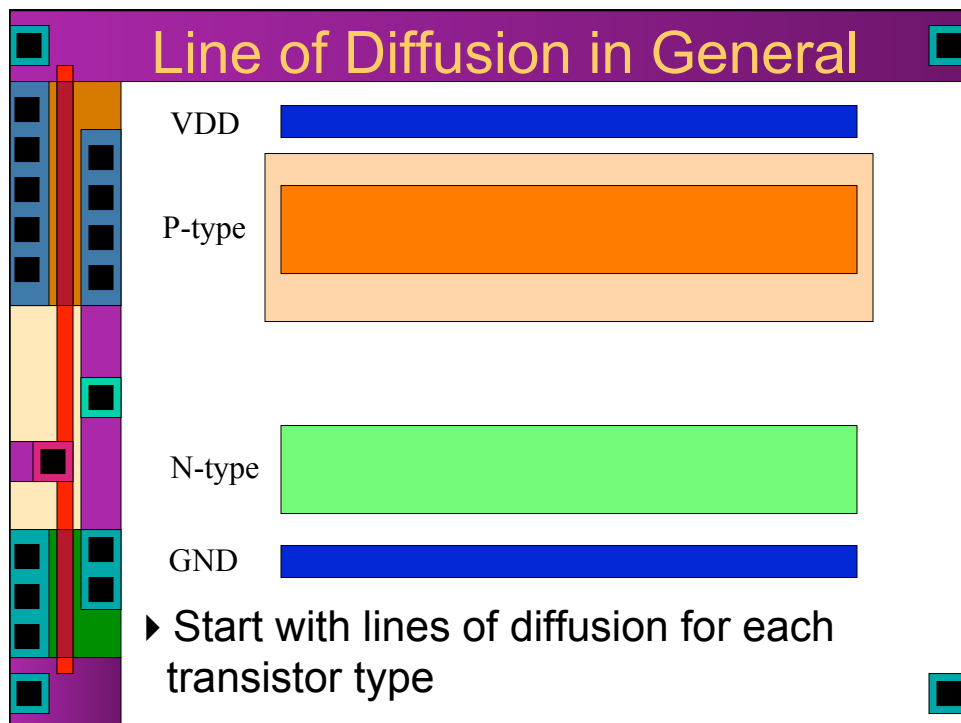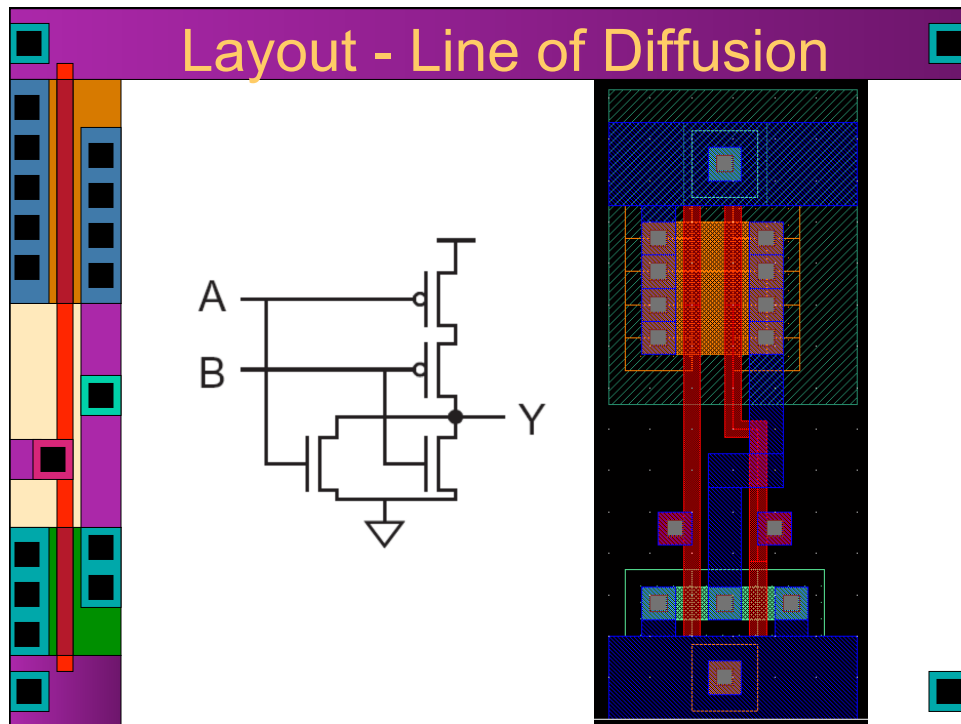
## Layout - Line of Diffusion


- ▶ Very common layout method
  - ▶ Start with a “line of diffusion” for each transistor type
  - ▶ Cross with poly to make transistors
  - ▶ This is the “type 2” NOR gate






 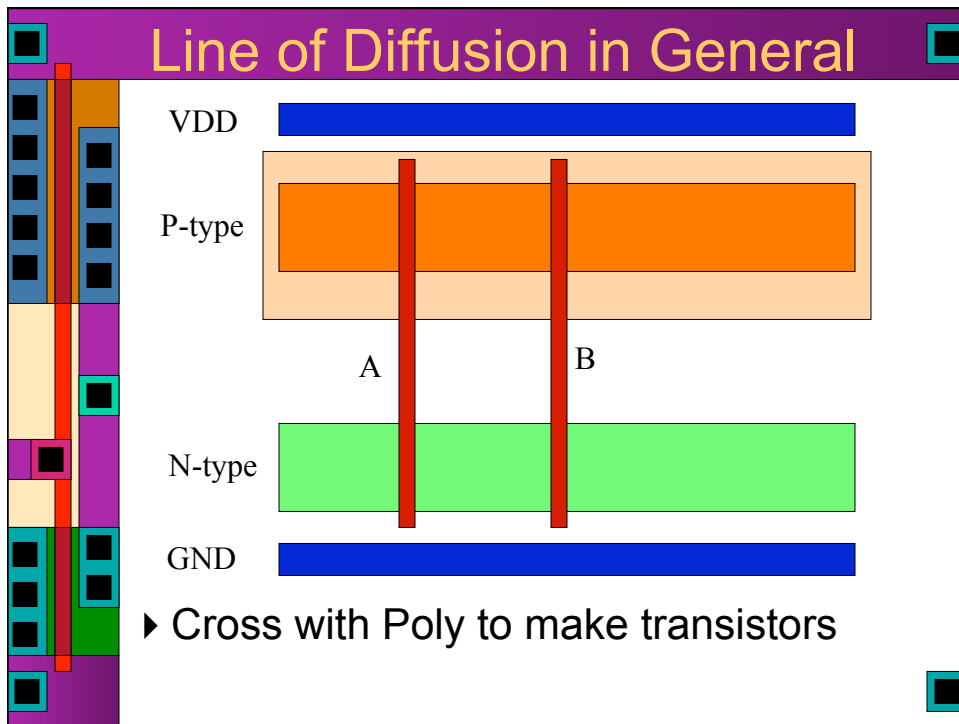

## Line of Diffusion in General

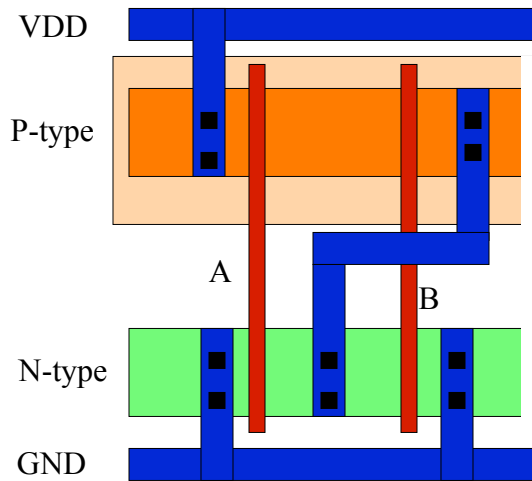


 - Now break and connect diff
- There's our NOR gate



 
## Stick Diagrams

- You can plan things with paper and pencil using Stick Diagrams – **Great for sketchbooks!!!!**
  - You'll need colored pencils
  - Draw lines for layers instead of rectangles
  - Then you can translate to layout




## My Sketchbooks

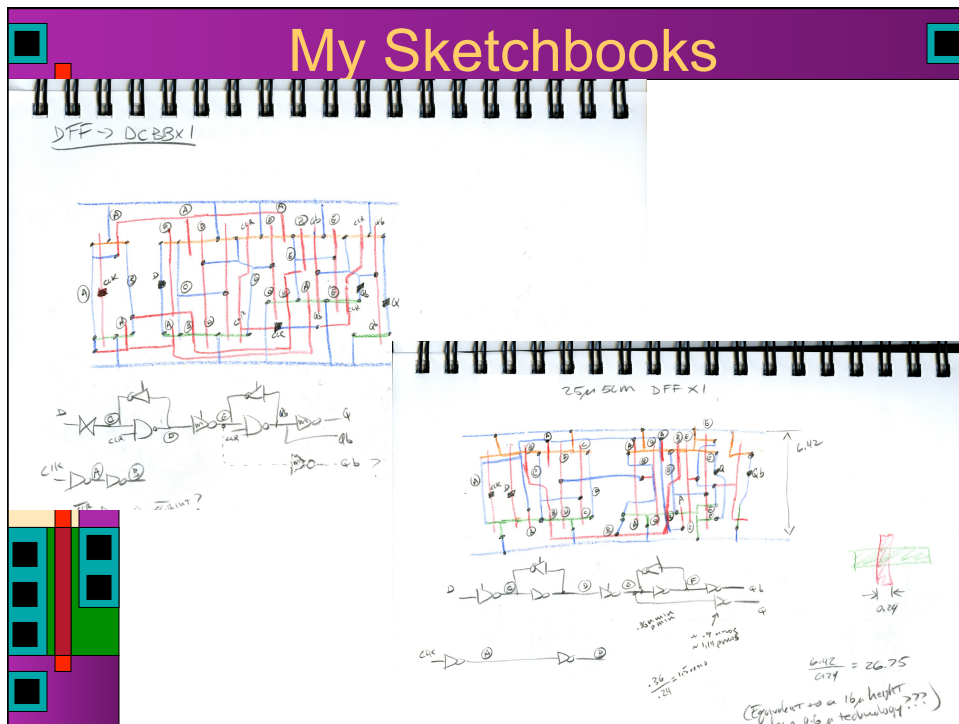

## Gate Layout


- ▶ Layout can be very time consuming
  - ▶ Design gates to fit together nicely
  - ▶ Build a library of standard cells
- ▶ Standard cell design methodology
  - ▶  $V_{DD}$  and GND should abut (standard height)
  - ▶ Adjacent gates should satisfy design rules
  - ▶ nMOS at bottom and pMOS at top
  - ▶ All gates include well and substrate contacts

## Example: Inverter

 

 
## Example: NAND3

- ▶ Horizontal N-diffusion and p-diffusion strips
- ▶ Vertical polysilicon gates
- ▶ Metal1  $V_{DD}$  rail at top
- ▶ Metal1 GND rail at bottom
- ▶  $32\lambda$  by  $40\lambda$
- ▶  $9.6\mu \times 12\mu$


 
## Stick Diagrams


- ▶ *Stick diagrams* help plan layout quickly
  - ▶ Need not be to scale
  - ▶ Draw with color pencils


 
## Wiring Tracks


- ▶ A *wiring track* is the space required for a wire
  - ▶  $1.2\mu$  width,  $1.2\mu$  spacing from neighbor results in  $2.4\mu$  pitch
- ▶ Transistors also consume one wiring track

In our rules M1 and M2 width & spacing is  $3\lambda$ , so pitch is  $1.8\mu$



 
## Well spacing

- ▶ Wells must surround transistors by  $1.8u$ 
  - ▶ Implies  $3.6u$  ( $12\lambda$ ) between opposite transistor flavors
  - ▶ Leaves room for one wire track


 
## Area Estimation

- ▶ Estimate area by counting wiring tracks
  - ▶ Multiply by 8 to express in  $\lambda$ , or by 2.4 to express in microns






## Example: O3AI

- ▶ Sketch a stick diagram for O3AI and estimate area



$$Y = \overline{(A + B + C)} \cdot D$$

 

## Example: O3AI

- ▶ Sketch a stick diagram for O3AI and estimate area



$$Y = \overline{(A + B + C)} \cdot D$$

  

## Example: O3AI

- Sketch a stick diagram for O3AI and estimate area



$$Y = \overline{(A + B + C)} \cdot D$$

  

## Example: O3AI

- Sketch a stick diagram for O3AI and estimate area



$$Y = \overline{(A + B + C)} \cdot D$$

  

## Example: O3AI

- Sketch a stick diagram for O3AI and estimate area



$$Y = \overline{(A + B + C)} \cdot D$$

  

## Example: O3AI

- Sketch a stick diagram for O3AI and estimate area



$$Y = \overline{(A + B + C)} \cdot D$$

  

## Example: O3AI

- Sketch a stick diagram for O3AI and estimate area



$$Y = \overline{(A + B + C)} \cdot D$$

  

## Example: O3AI

- Sketch a stick diagram for O3AI and estimate area



$$Y = \overline{(A + B + C)} \cdot D$$

  

## Example: O3AI

- Sketch a stick diagram for O3AI and estimate area


$$Y = \overline{(A + B + C)} \cdot D$$

  

## Example: O3AI

- Sketch a stick diagram for O3AI and estimate area


$$Y = \overline{(A + B + C)} \cdot D$$

 

## Example: O3AI

- ▶ Sketch a stick diagram for O3AI and estimate area


$$Y = (A + B + C)gD$$

 

## Euler Paths

- ▶ A graphical method for planning complex gate layout
  - ▶ Take the transistor netlist and draw it as a graph
  - ▶ Note that the pull-up and pull-down trees can be duals of each other
  - ▶ Find a path that traverses the graph with the same variable ordering for pull-up and pull-down graphs
  - ▶ This guides you to a line of diffusion layout



## Simple example: NOR

 

- ▶ Euler path is a tour of all edges
- ▶ Find a path that has the same ordering for pull-up and pull-down, i.e. **A B**
  - ▶ **Vdd A 1 B Out**    **GND A Out B GND**
- ▶ Another great bit of sketchbooking...
  
## This Path Translates to Layout

- ▶ Find a path that has the same ordering for pull-up and pull-down, e.g. **A B**
  - ▶ You can also include all the internal nodes
  - ▶ Pull-up: **Vdd A 1 B Out**
  - ▶ Pull-Down: **GND A Out B GND**
  - ▶ Line of diffusion layout




## Examples

- ▶ Switch to chalkboard for examples
  - ▶ Hopefully with colored chalk...
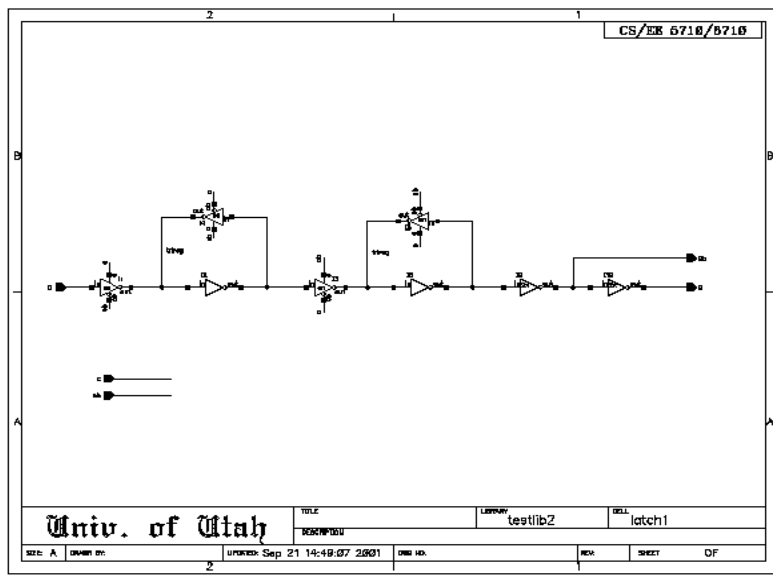
## Layout Example: Flip Flop


- ▶ Simple D-type edge triggered flip flop





 
## Zoom in on Latch

- Need two copies of this for a full D flip flop


 
## Zoom in on Latch

- Need two copies of this for a full D flip flop



## Zoom in on Latch


► Need two copies of this for a full D flip flop

The diagram illustrates the internal structure of a latch and its connection to a D flip-flop. On the left, a schematic of a latch is shown with inputs A,  $\overline{EN}$ , EN, and Y. A red arrow points from this schematic to a detailed view of the latch's internal structure, which consists of two cross-coupled NMOS transistors. The top transistor has gate A and source  $\overline{EN}$ , while the bottom transistor has gate Y and source EN. A red arrow also points from the latch schematic to a D flip-flop circuit. The D flip-flop is composed of two D-type latches (labeled I1 and I4) and two inverters (labeled 12 and 13). The output of the first latch (I1) is connected to the input of the second latch (I4), and the output of the second latch (I4) is connected back to the input of the first latch (I1). The output of the first latch (I1) is labeled 'trireg'.

[illegible]

 
## Stick Diagram of Latch

- First add the gates
  - Note where outputs can be shared
  - Ignore details of signal crossings for now...



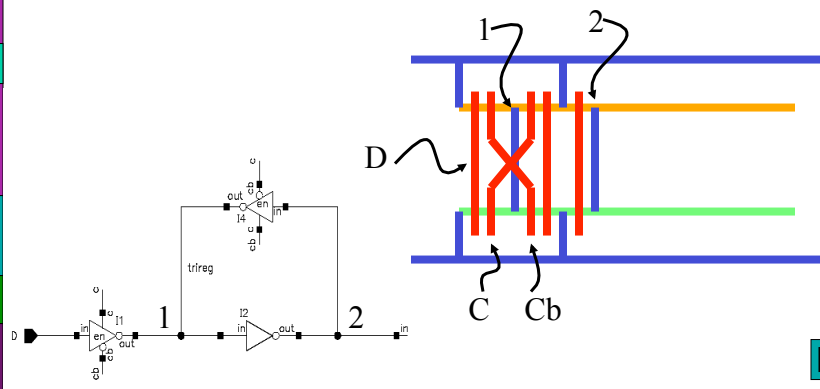
## Stick Diagram of Latch

- First add the gates
  - Note where the signals are relative to the schematic



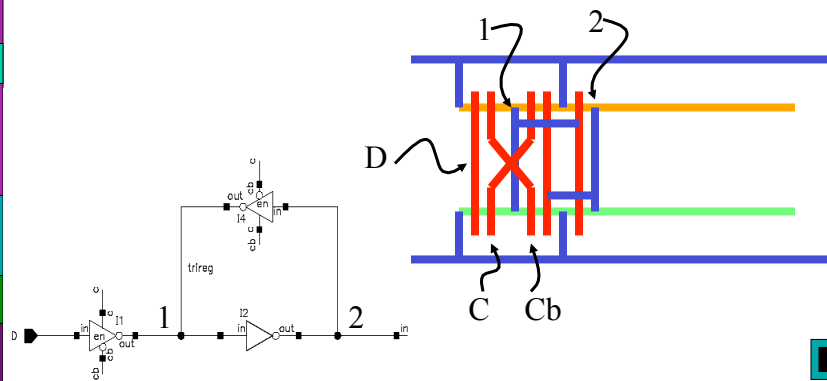
## Stick Diagram of Latch

- First add the gates
  - Note where the signals are relative to the schematic
  - Note where additional connections are needed



 
## Start With First Enabled Inv

- I'm using 5u power wires, 29u vertical pitch based on a C5x standard cell model from AMI
  - Probably overkill...
- Add DIF for N- and P-type transistors
  - Note 2x standard size because of series connection



 
## Add Next Enabled Inverter

- ▶ Add two more poly gates for second enabled inverter
- ▶ Note that the two enabled inverters share an output (not connected yet)
- ▶ Note that I've added vdd! and gnd! For DRC
- ▶ I'll deal with C-Cb crossover later...





## Aside: Multiple Contacts

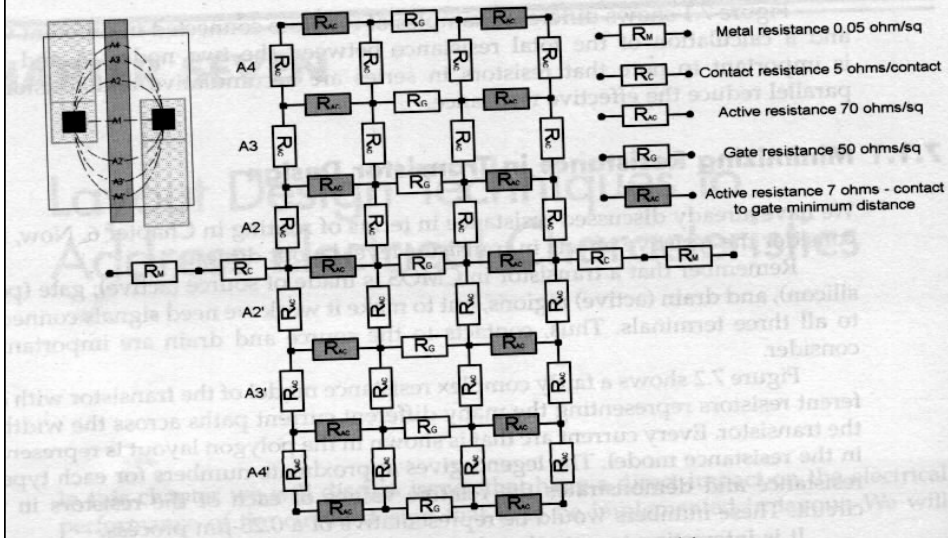



- ▶ Look at a model of transistor resistance

## Contact Option #1

  

- ▶ Total equivalent resistance = 56.1 Ohms
- ▶ Metal resistance = 0.05  $\Omega$ /square
- ▶ Contact resistance = 5  $\Omega$ /contact
- ▶ Active resistance = 70  $\Omega$ /square
- ▶ Gate resistance = 50  $\Omega$ /square
- ▶ Active resistance 70 - contact to gate


## Contact Option #2

  


Case 2

- ▶ Total equivalent resistance = 105.1 Ohms

## Contact Option #3

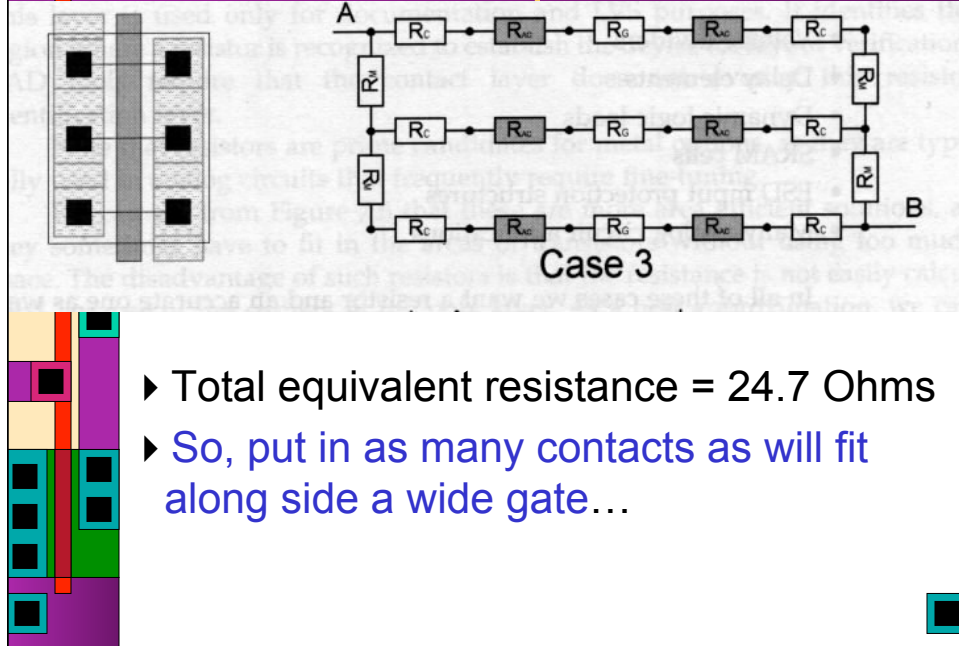


## Meanwhile, Add inverter

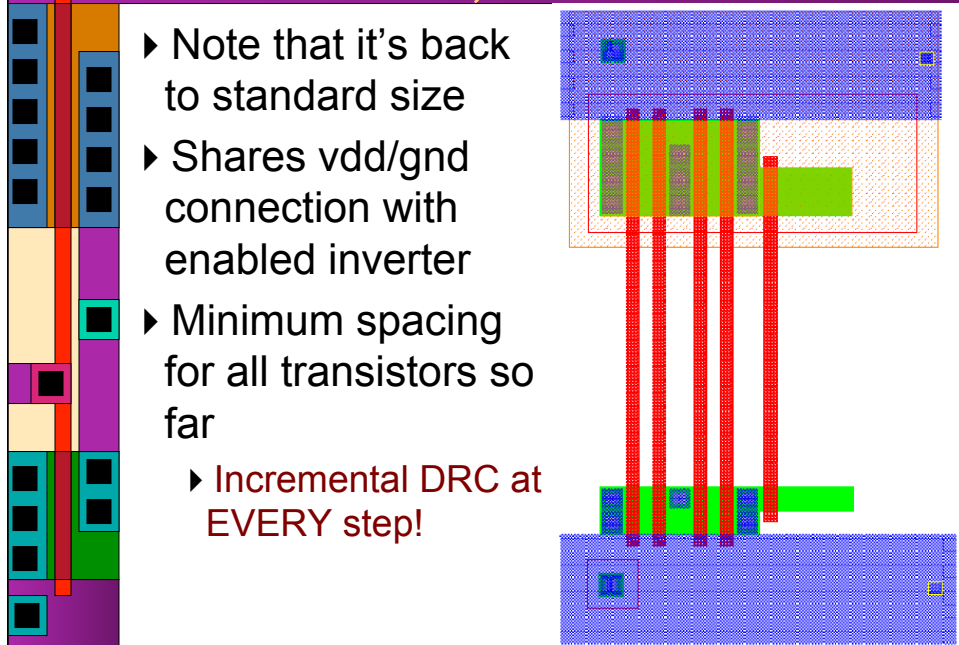

 
## Finish Inverter (mostly)

- ▶ Make inverter output connections
  - ▶ Don't connect yet
  - ▶ I'm going to use M1 as a horizontal layer
  - ▶ Which means being careful about vertical use of M1


 
## Make Feedback Connections



- ▶ Output of inverter (connected in M1 for now) goes to input of 2<sup>nd</sup> enabled inverter
- ▶ Output of enabled inverters goes to input of inverter
  - ▶ Note that output of enabled inverters goes through POLY





  
## Deal With C/Cb Crossover

- ▶ Start by cutting the “select” gates of the enabled inverters



 
## Connect the C Input

- ▶ Prepare for M1 crossover in C wire
  - ▶ C is N-type in first enabled inverter, P-type in second enabled inverter
  - ▶ Use M1PLY contacts
- ▶ PROBLEM! We need to squeeze a poly wire inbetween those contacts...
- ▶ Use design rules to plan for space



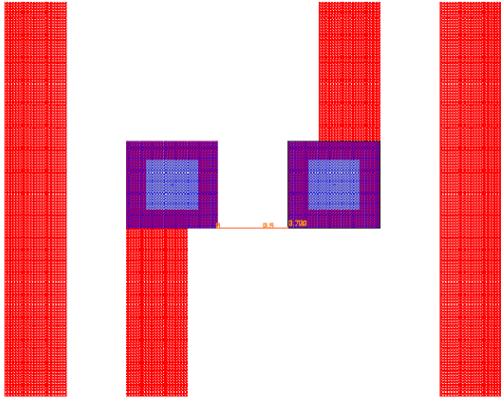
## Look at Gap


- ▶ You need to have enough space for minimum width poly to fit through gap


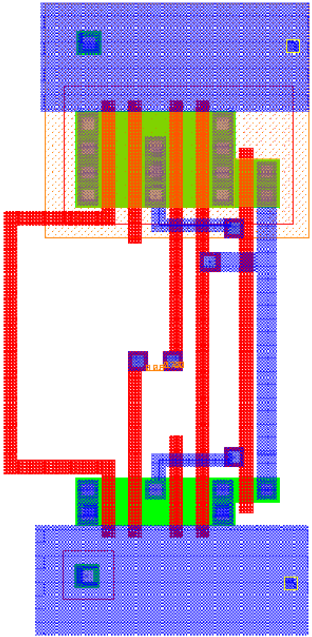
## Start Making Room


- ▶ Push D-signal poly out of the way with minimum spacing to DIF
  - ▶ We'll move it back later
- ▶ Make sure to continue to DRC at every step!



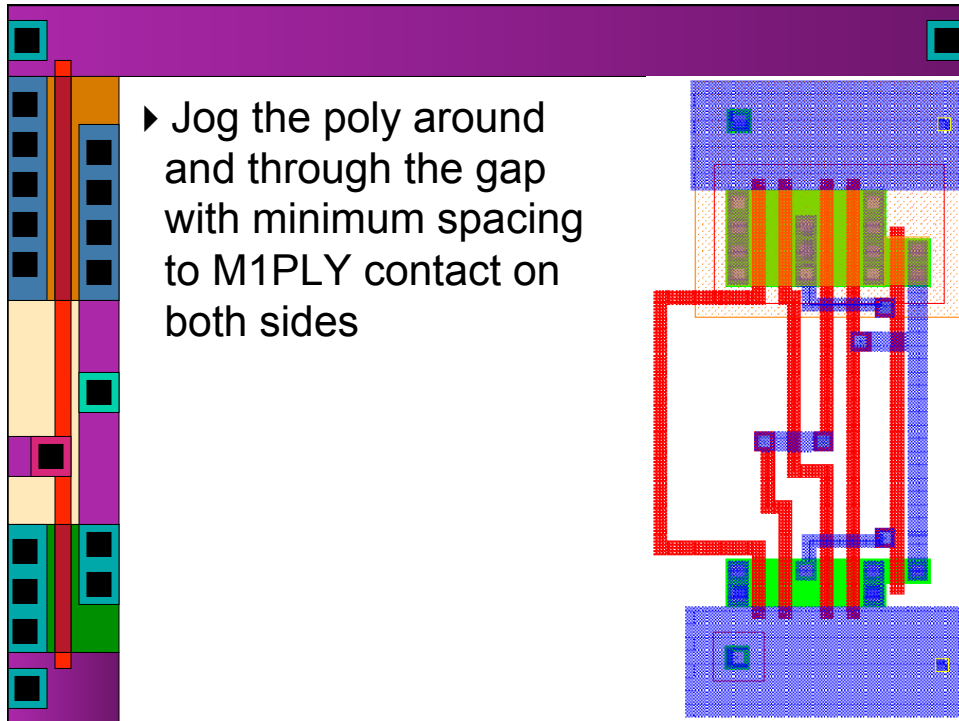


► Jog the poly around and through the gap with minimum spacing to M1PLY contact on both sides

### Fit Things Back Together

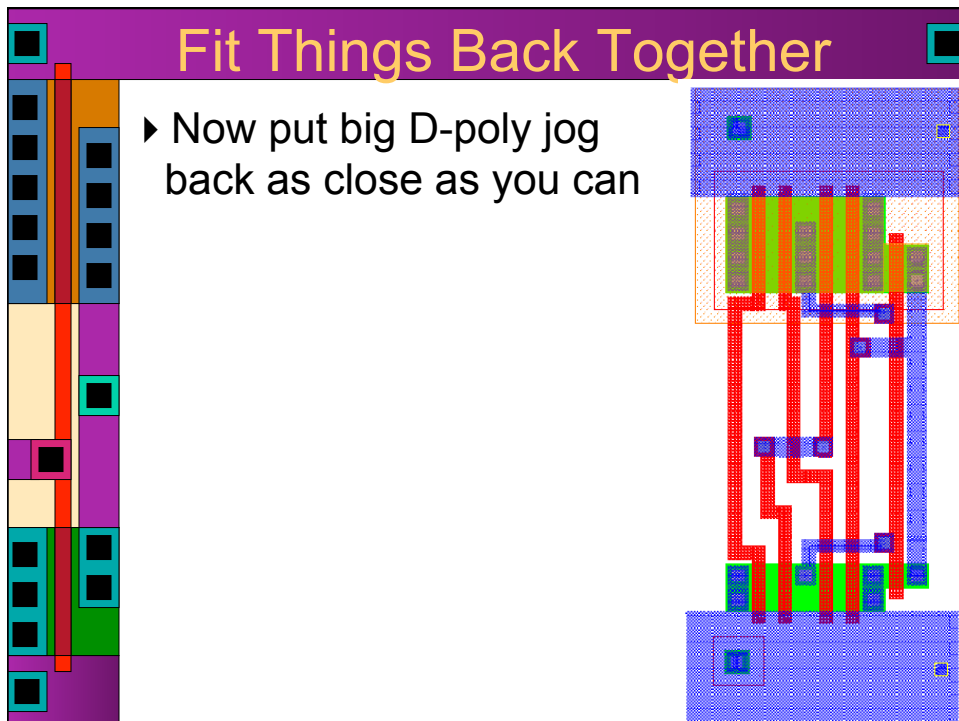


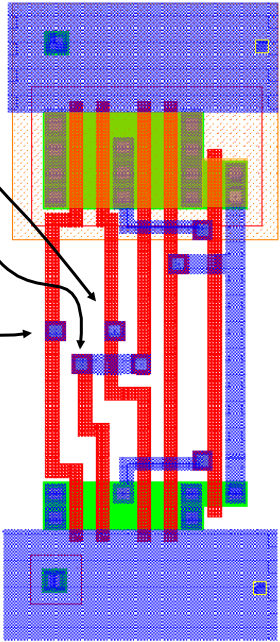► Now put big D-poly jog back as close as you can




- ▶ Add M1PLY contacts for future connections
- ▶ Need to get Cb, C, D signals into the latch in the future
- ▶ Those will most likely be routed on some type of metal
- ▶ So we need the M1 metal connection at the bottom

## Plan For Clock Routing

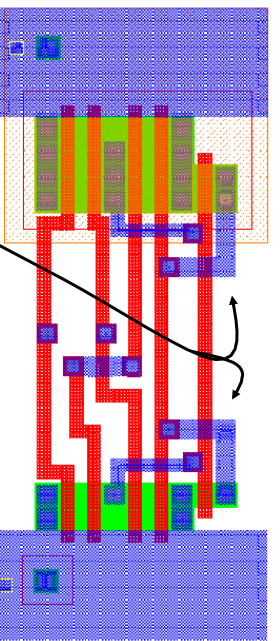


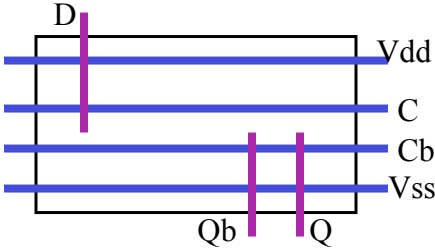- ▶ Break M1 output connection on inverter to leave room for horizontal M1 routing
- ▶ I'll eventually route C and Cb through the cell horizontally on M1



 
## Bit Slice Plan

- Plan is to stitch these together to make a register
  - Inputs on top in M2
  - Outputs on bottom in M2
  - Clock and Clock-bar routed horizontally in M1



 
## Need Second Latch

- Basically a copy of the first latch
  - But with reversed C and Cb connections
  - Copy the first layout...



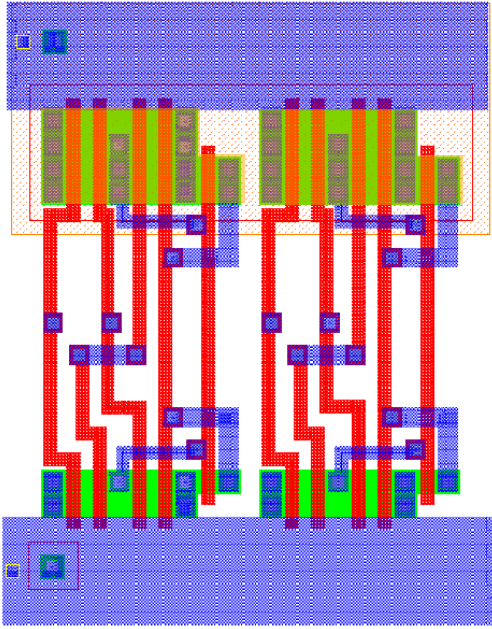
## Expand from Latch to F/F

- ▶ Select and copy the first latch
- ▶ Now I need to reverse the C and Cb connections


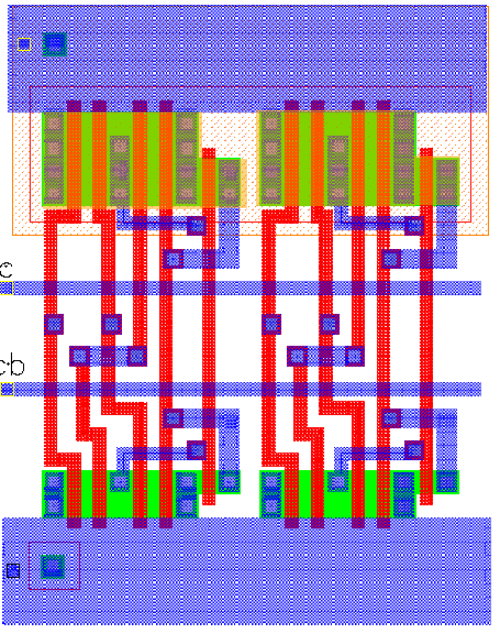
## C/Cb Routing Plan


- ▶ Remember my C/Cb routing plan
  - ▶ Plan for where those wires can go




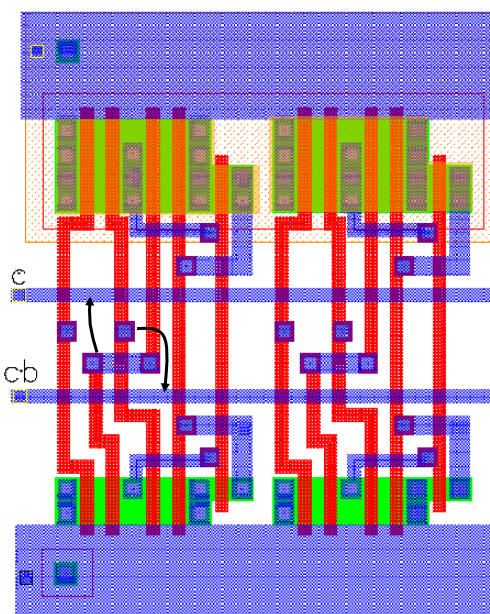
## C/Cb Routing Plan


- ▶ Remember my C/Cb routing plan
- ▶ Plan for where those wires can go



The diagram shows a routing plan with a grid of red and blue wires. A dashed box highlights a specific area. Labels 'c' and 'cb' are on the left. The wires are connected to a series of components at the top and bottom.
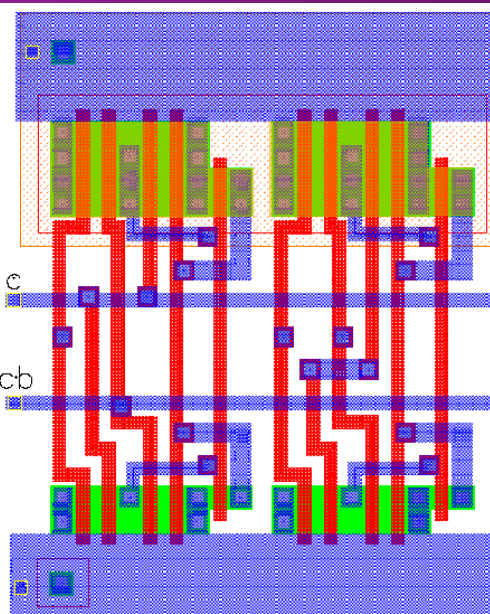
## Connect Clocks to 1<sup>st</sup> Latch


- ▶ Adjust contact positions for the first enabled inverter



The diagram shows a routing plan with a grid of red and blue wires. A dashed box highlights a specific area. Labels 'c' and 'cb' are on the left. The wires are connected to a series of components at the top and bottom.

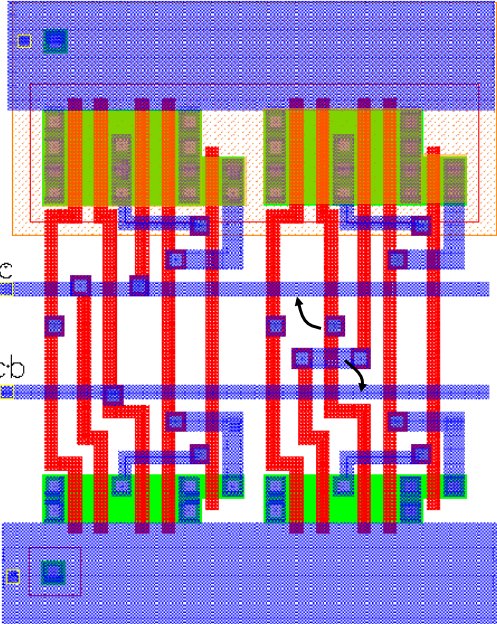
## Connect Clocks to 2nd Latch

- ▶ Now shift the contacts the other way for the second latch
- ▶ Makes the complementary C/Cb connection


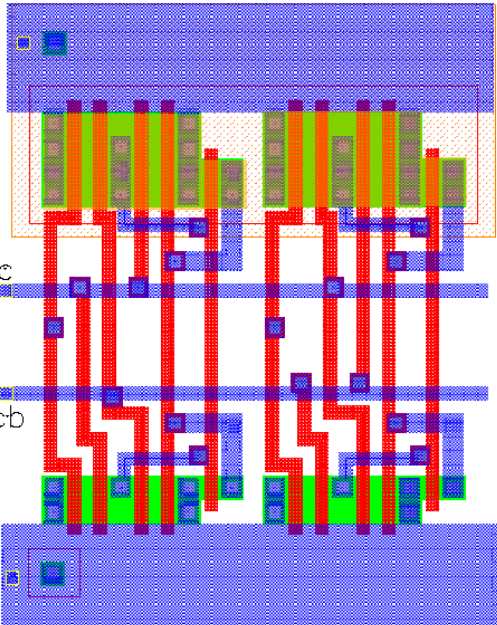
## Connect Clocks to 2<sup>nd</sup> Latch

- ▶ Now shift the contacts the other way for the second latch
- ▶ Makes the complementary C/Cb connection





## Connect the Two Latches

- ▶ Q of first goes to D of second
- ▶ Don't really need both top and bottom connections, but it doesn't hurt
- ▶ Lower resistance paths

The diagram illustrates the routing of two latches. Red vertical lines represent the signal paths of the latches. Blue horizontal lines represent the routing channels. Labels 'c' and 'cb' point to specific horizontal lines. Arrows indicate the connection from the Q output of the first latch to the D input of the second latch.

## Note Extra Routing Channels

- ▶ Note that this vertical pitch, and this cell contents have left two additional M1 horizontal routing channels through the middle of the cell

The diagram illustrates the routing of two latches with extra routing channels. Red vertical lines represent the signal paths of the latches. Blue horizontal lines represent the routing channels. Labels 'c' and 'cb' point to specific horizontal lines. An arrow points to the extra routing channels.

## Now Consider Output Inverters

- ▶ Two more inverters
- ▶ Make them 2x size for output drive

Univ. of Utah

testlib2

## Output Inverters

- ▶ Add the DIF for the output inverters
- ▶ Remember I want to make them 2x size

Univ. of Utah

testlib2



## Make Output Connections

- ▶ Add vdd, gnd and output contacts
- ▶ Add poly gates
- ▶ Make output connections in M2
- ▶ Connect to 2<sup>nd</sup> latch and to 2<sup>nd</sup> inverter
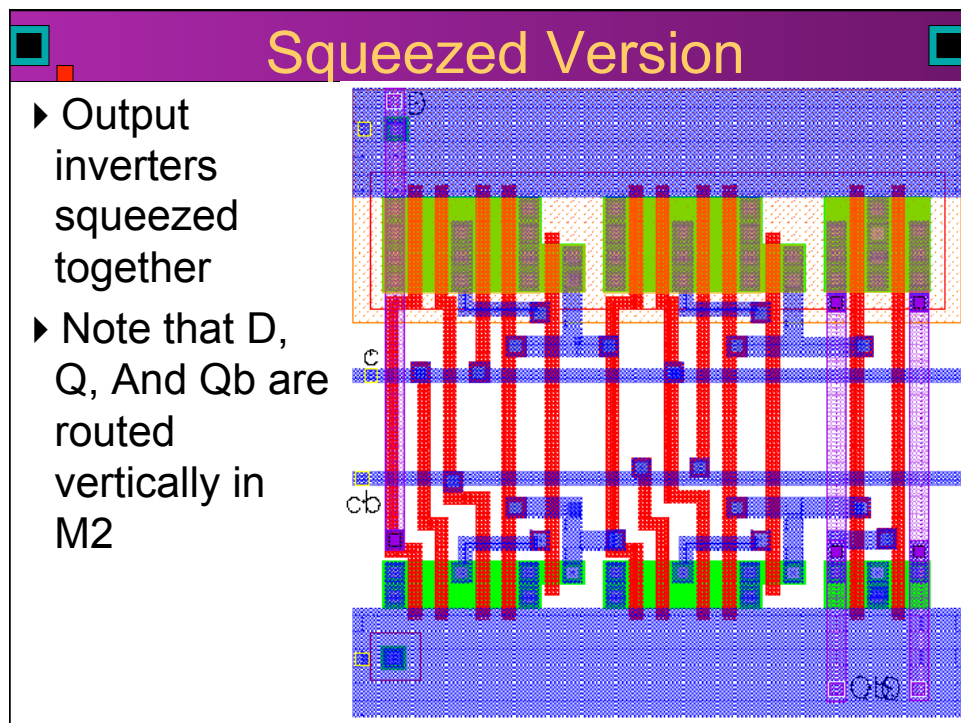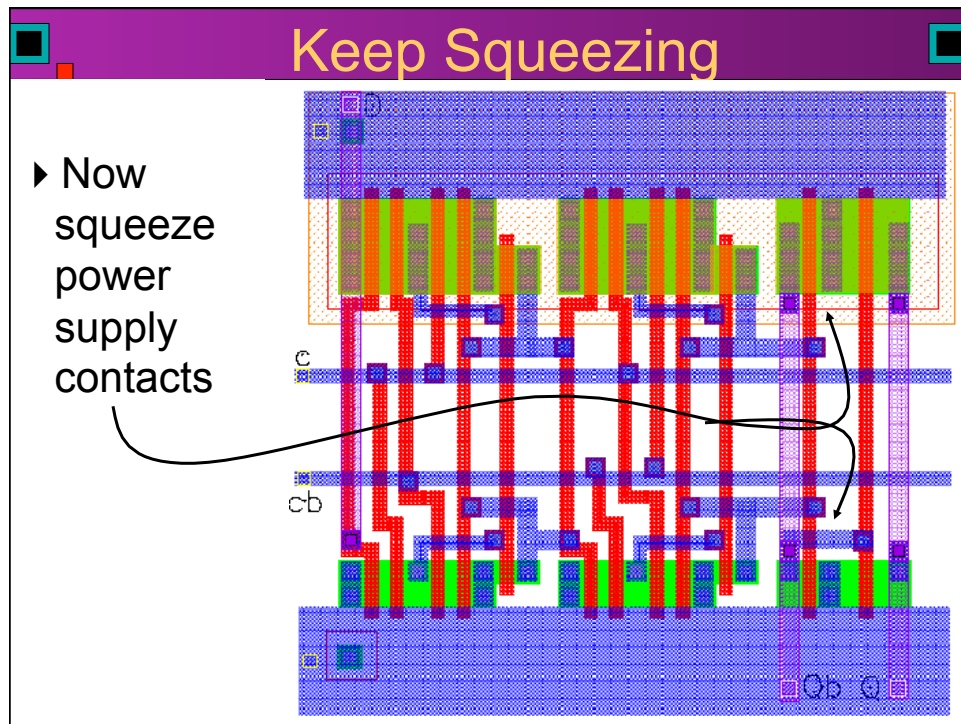
## Now Squeeze Inverter


- ▶ Select regions of the layout and stretch to move it all to a new spot





 
## Final D-Type Flip Flop

- ▶ Squeeze vertically since I don't need extra routing channels, and I don't need to match with standard cells
- ▶ Add long NWELL and SUB contacts



## Put Four of them Together

 

- ▶ Add instances that abut
  - ▶ Or use the "array" feature of the instance dialog
- ▶ Note that C and Cb are routed in horizontal M1

