

## An Example: MIPS

From the Harris/Weste book

Based on the MIPS-like processor from  
the Hennessy/Patterson book

## MIPS Architecture

- ◆ Example: subset of MIPS processor architecture
  - Drawn from Patterson & Hennessy
- ◆ MIPS is a 32-bit architecture with 32 registers
  - Consider 8-bit subset using 8-bit datapath
  - Only implement 8 registers (\$0 - \$7)
  - \$0 hardwired to 00000000
  - 8-bit program counter

# Instruction Set

Table 1.7 MIPS instruction set (subset supported)

Instruction	Function	Encoding	op	funct
add \$1, \$2, \$3	addition: $\$1 \rightarrow \$2 + \$3$	R	000000	100000
sub \$1, \$2, \$3	subtraction: $\$1 \rightarrow \$2 - \$3$	R	000000	100010
and \$1, \$2, \$3	bitwise and: $\$1 \rightarrow \$2 \text{ and } \$3$	R	000000	100100
or \$1, \$2, \$3	bitwise or: $\$1 \rightarrow \$2 \text{ or } \$3$	R	000000	100101
slt \$1, \$2, \$3	set less than: $\$1 \rightarrow 1 \text{ if } \$2 < \$3$ $\$1 \rightarrow 0 \text{ otherwise}$	R	000000	101010
addi \$1, \$2,	add immediate: $\$1 \rightarrow \$2 + \text{imm}$	I	001000	n/a
beq \$1, \$2, imm	branch if equal: $\text{PC} \rightarrow \text{PC} + \text{imm}^a$	I	000100	n/a
j destination	jump: $\text{PC}_{\text{destination}}^a$	J	000010	n/a
lb \$1, imm(\$2)	load byte: $\$1 \rightarrow \text{mem}[\$2 + \text{imm}]$	I	100000	n/a
sb \$1, imm(\$2)	store byte: $\text{mem}[\$2 + \text{imm}] \rightarrow \$1$	I	110000	n/a

# Instruction Set

Table 1.7 MIPS instruction set (subset supported)

Instruction	Function	Encoding	op	funct
add \$1, \$2, \$3	addition: $\$1 \rightarrow \$2 + \$3$	R	000000	100000
sub \$1, \$2, \$3	subtraction: $\$1 \rightarrow \$2 - \$3$	R	000000	100010
and \$1, \$2, \$3	bitwise and: $\$1 \rightarrow \$2 \text{ and } \$3$	R	000000	100100
or \$1, \$2, \$3	bitwise or: $\$1 \rightarrow \$2 \text{ or } \$3$	R	000000	100101
slt \$1, \$2, \$3	set less than: $\$1 \rightarrow 1 \text{ if } \$2 < \$3$ $\$1 \rightarrow 0 \text{ otherwise}$	R	000000	101010
addi \$1, \$2,	add immediate: $\$1 \rightarrow \$2 + \text{imm}$	I	001000	n/a
beq \$1, \$2, imm	branch if equal: $\text{PC} \rightarrow \text{PC} + \text{imm}^a$	I	000100	n/a
j destination	jump: $\text{PC}_{\text{destination}}^a$	J	000010	n/a
lb \$1, imm(\$2)	load byte: $\$1 \rightarrow \text{mem}[\$2 + \text{imm}]$	I	100000	n/a
sb \$1, imm(\$2)	store byte: $\text{mem}[\$2 + \text{imm}] \rightarrow \$1$	I	110000	n/a

What's missing from this instruction set?

## Instruction Set

Table 1.7 MIPS instruction set (subset supported)

Instruction	Function	Encoding	op	funct
add \$1, \$2, \$3	addition: $\$1 \rightarrow \$2 + \$3$	R	000000	100000
sub \$1, \$2, \$3	subtraction: $\$1 \rightarrow \$2 - \$3$	R	000000	100010
and \$1, \$2, \$3	bitwise and: $\$1 \rightarrow \$2 \text{ and } \$3$	R	000000	100100
or \$1, \$2, \$3	bitwise or: $\$1 \rightarrow \$2 \text{ or } \$3$	R	000000	100101
slt \$1, \$2, \$3	set less than: $\$1 \rightarrow 1 \text{ if } \$2 < \$3$ $\$1 \rightarrow 0 \text{ otherwise}$	R	000000	101010
addi \$1, \$2,	add immediate: $\$1 \rightarrow \$2 + \text{imm}$	I	001000	n/a
beq \$1, \$2, imm	branch if equal: $\text{PC} \rightarrow \text{PC} + \text{imm}^a$	I	000100	n/a
j destination	jump: $\text{PC}_{\text{destination}}^a$	J	000010	n/a
lb \$1, imm(\$2)	load byte: $\$1 \rightarrow \text{mem}[\$2 + \text{imm}]$	I	100000	n/a
sb \$1, imm(\$2)	store byte: $\text{mem}[\$2 + \text{imm}] \rightarrow \$1$	I	110000	n/a

What's missing from this instruction set? Lots of things!

One in particular: Support for subroutine calls... (JAL, STPC, etc.)

## Instruction Encoding

- ◆ 32-bit instruction encoding (still 8-bit data)
  - Requires four cycles to fetch on 8-bit datapath

format	example	encoding
R	add \$rd, \$ra, \$rb	6 5 5 5 5 6 0 ra rb rd 0 funct
I	beq \$ra, \$rb, imm	6 5 5 16 op ra rb imm
J	j dest	6 26 op dest

## Fibonacci (C)

```
f0 = 1; f-1 = -1  
fn = fn-1 + fn-2  
f = 0, 1, 1, 2, 3, 5, 8, 13, ...
```

```
int fib(void)  
{  
    int n = 8;           /* compute nth Fibonacci number */  
    int f1 = 1, f2 = -1; /* last two Fibonacci numbers */  
  
    while (n != 0) {    /* count down to n = 0 */  
        f1 = f1 + f2;  
        f2 = f1 - f2;  
        n = n - 1;  
    }  
    return f1;  
}
```

## Fibonacci (Assembly)

- ◆ 1<sup>st</sup> statement: int n = 8;
- ◆ How do we translate this to assembly?
  - Decide which register should hold its value
  - Load an immediate value into that register
  - But, there's no “load immediate” instruction...
  - But, there is an addi instruction, and there's a convenient register that's always pinned to 0
- ◆ addi \$3, \$0, 8 ; load 0+8 into register 3

## Fibonacci (Assembly)

```
# fib.asm
# Register usage: $3: n $4: f1 $5: f2
# return value written to address 255
fib: addi $3, $0, 8      # initialize n=8
      addi $4, $0, 1      # initialize f1 = 1
      addi $5, $0, -1     # initialize f2 = -1
loop: beq $3, $0, end    # Done with loop if n = 0
      add $4, $4, $5      # f1 = f1 + f2
      sub $5, $4, $5      # f2 = f1 - f2
      addi $3, $3, -1     # n = n - 1
      j loop              # repeat until done
end: sb $4, 255($0)      # store result in address 255
```

## Fibonacci (Binary)

- ◆ 1<sup>st</sup> statement: addi \$3, \$0, 8
- ◆ How do we translate this to machine language?
  - Hint: use instruction encodings below

format	example	encoding					
R	add \$rd, \$ra, \$rb	6	5	5	5	5	6
I	beq \$ra, \$rb, imm	0	ra	rb	rd	0	funct
J	j dest	6	5	5	16	imm	dest

# Fibonacci (Binary)

## ◆ Machine language program

Instruction	Binary Encoding	Hexadecimal Encoding
addi \$3, \$0, 8	001000 00000 00011	20030008
addi \$4, \$0, 1	001000 00000 00100	20040001
addi \$5, \$0, -1	001000 00000 00101	2005ffff
beq \$3, \$0, end	000100 00011 00000	10600005
add \$4, \$4, \$5	000000 00100 00101	00852020
sub \$5, \$4, \$5	000000 00100 00101	00852822
addi \$3, \$3, -1	001000 00011 00011	2063ffff
j loop	000010 00000000000000000000000000000011	08000003
sb \$4, 255(\$0)	110000 00000 00100	a00400ff


# Fibonacci (Binary)

Instruction	Binary Encoding	Hexadecimal Encoding
addi \$3, \$0, 8	001000 00000 00011	20030008
addi \$4, \$0, 1	001000 00000 00100	20040001
addi \$5, \$0, -1	001000 00000 00101	2005ffff
beq \$3, \$0, end	000100 00011 00000	10600005
add \$4, \$4, \$5	000000 00100 00101	00852020
sub \$5, \$4, \$5	000000 00100 00101	00852822
addi \$3, \$3, -1	001000 00011 00011	2063ffff
j loop	000010 00000000000000000000000000000011	08000003
sb \$4, 255(\$0)	110000 00000 00100	a00400ff


format	example	encoding
R	add \$rd, \$ra, \$rb	6 5 5 5 5 6 0 ra rb rd 0 funct
I	beq \$ra, \$rb, imm	6 5 5 16 op ra rb imm
J	j dest	6 26 op dest
 
# MIPS Microarchitecture

- Multicycle microarchitecture from Patterson & Hennessy




## Multicycle Controller

 
 
## Logic Design


- ◆ Start at top level
  - Hierarchically decompose MIPS into units
- ◆ Top-level interface



 
## Verilog Code

```
// top level design includes both mips processor and memory
module mips_mem #(parameter WIDTH = 8, REGBITS = 3)(clk, reset);
    input clk, reset;
    wire      memread, memwrite;
    wire [WIDTH-1:0] adr, writedata;
    wire [WIDTH-1:0] memdata;

    // instantiate the mips processor
    mips #(WIDTH,REGBITS) mips(clk, reset, memdata, memread,
                               memwrite, adr, writedata);
    // instantiate memory for code and data
    exmem #(WIDTH) exmem(clk, memwrite, adr, writedata, memdata);
endmodule
```



## Block Diagram

 


## Top-level code


```
// simplified MIPS processor
module mips #(parameter WIDTH = 8, REGBITS = 3)
    (input      clk, reset,
     input [WIDTH-1:0] memdata,
     output      memread, memwrite,
     output [WIDTH-1:0] adr, writedata);

    wire [31:0] instr;
    wire      zero, alusrc, memtoreg, iord, pcen;
    wire      regwrite, regdst;
    wire [1:0]  aluop, psource, alusrccb;
    wire [3:0]  irwrite;
    wire [2:0]  alucont;

    controller cont(clk, reset, instr[31:26], zero, memread, memwrite,
                    alusrc, memtoreg, iord, pcen, regwrite, regdst,
                    psource, alusrccb, aluop, irwrite);
    alucontrol ac(aluop, instr[5:0], alucont);
    datapath  # (WIDTH, REGBITS)
              dp(clk, reset, memdata, alusrc, memtoreg, iord, pcen,
                  regwrite, regdst, psource, alusrccb, irwrite, alucont,
                  zero, instr, adr, writedata);
endmodule
```

 

# Controller (FSM)

 

```

module controller(input clk, reset,
    input [5:0] op,
    input zero,
    output reg memread, memwrite, alusrcA, memtoreg, lIRD,
    output reg poen,
    output reg rewrite, regdst,
    output reg [1:0] pcsource, alusrcB, aluop,
    output reg [3:0] irwrite);

parameter FETCH1 = 4'b0001;
parameter FETCH2 = 4'b0010;
parameter FETCH3 = 4'b0011;
parameter FETCH4 = 4'b0100;
parameter DECODE = 4'b0101;
parameter MEMADR = 4'b0110;
parameter LBRD = 4'b0111;
parameter LBWR = 4'b1000;
parameter SBWR = 4'b1001;
parameter RTYPEEX = 4'b1010;
parameter RTYPEWR = 4'b1011;
parameter BEQEX = 4'b1100;
parameter JEX = 4'b1101;
parameter ADDIWR = 4'b1110; // added for ADDI

```

```

parameter LB = 6'b100000;
parameter SB = 6'b101000;
parameter RTYPE = 6'b0;
parameter BEQ = 6'b000100;
parameter J = 6'b000010;
parameter ADDI = 6'b001000; // added for ADDI

```

```

parameter LB = 6'b100000;
parameter SB = 6'b101000;
parameter RTYPE = 6'b0;
parameter BEQ = 6'b000100;
parameter J = 6'b000010;
parameter ADDI = 6'b001000; // added for ADDI

```

```

reg [3:0] state, nextstate;
reg pcwrite, pcwritecond;

```

State Encodings...

## Controller Parameters

Opcodes...

Local reg variables...

## Main state machine – NS logic

```
// state register
always @(posedge clk)
  if(reset) state <= FETCH1;
  else state <= nextstate;

// next state logic (combinational)
always @(*)
begin
  case(state)
    FETCH1: nextstate <= FETCH2;
    FETCH2: nextstate <= FETCH3;
    FETCH3: nextstate <= FETCH4;
    FETCH4: nextstate <= DECODE;
    DECODE: case(op)
      LB:   nextstate <= MEMADR;
      SB:   nextstate <= MEMADR;
      ADDI:  nextstate <= MEMADR;
      RTYPE: nextstate <= RTYPEEX;
      BEQ:  nextstate <= BEQEX;
      J:    nextstate <= JEX;
    // should never happen
    default: nextstate <= FETCH1;
  endcase
end


MEMADR: case(op)
  LB:   nextstate <= LBRD;
  SB:   nextstate <= SBWR;
  ADDI:  nextstate <= ADDIWR;
  // should never happen
  default: nextstate <= FETCH1;
endcase

LBRD: nextstate <= LBWR;
LBWR: nextstate <= FETCH1;
SBWR: nextstate <= FETCH1;
RTYPEEX: nextstate <= RTYPEWR;
RTYPEWR: nextstate <= FETCH1;
BEQEX: nextstate <= FETCH1;
JEX:   nextstate <= FETCH1;
ADDIWR: nextstate <= FETCH1;
// should never happen
default: nextstate <= FETCH1;
endcase
end
```

## Setting Control Signal Outputs

```
always @(*)
begin
  // set all outputs to zero, then
  // conditionally assert just the
  // appropriate ones
  iwrite <= 4'b0000;
  pcwrite <= 0; pcwritecond <= 0;
  regwrite <= 0; regdst <= 0;
  memread <= 0; memwrite <= 0;
  alusrca <= 0; alusrcb <= 2'b00;
 aluop <= 2'b00; pcsource <= 2'b00;
  iord <= 0; memtoreg <= 0;
  case(state)
    FETCH1:
      begin
        memread <= 1;
        iwrite <= 4'b0001;
        alusrcb <= 2'b01;
        pcwrite <= 1;
      end
    ....
  endcase
end
endmodule
```

# MIPS Microarchitecture - Datapath

 

```

module datapath #(parameter WIDTH = 8, REGBITS = 3)
    (input      clk, reset,
     input [WIDTH-1:0] memdata,
     input      alusrcA, memtoreg, iord, pcen, regwrite, regdst,
     input [1:0]   pcsource, alusrcB, // mux select bits
     input [3:0]  irwritel,           // InstReg write flags
     input [2:0]  alucont,          // ALU control bits
     output      zero,              // "ALU output is zero" flag
     output [31:0] instr,            // 32-bit instruction register
     output [WIDTH-1:0] adr, wridata); // 8-bit address and write-data registers

// the size of the parameters must be changed to match the WIDTH parameter
localparam CONST_ZERO = 8'b0;
localparam CONST_ONE = 8'b1;

wire [REGBITS-1:0] ra1, ra2, wa; // register address bits
wire [WIDTH-1:0]   pc, nextpc, md, rd1, rd2, wd, a, src1, src2, aluresult, aluout, constx4;

// shift left constant field by 2
assign constx4 = {instr[WIDTH-3:0], 2'b00};

// register file address fields
assign ra1 = instr[REGBITS+20:21];
assign ra2 = instr[REGBITS+15:16];
mux2 #(REGBITS) regmux(instr[REGBITS+15:16], instr[REGBITS+10:11], regdst, wa);

```

Verilog:  
Datapath 1

```


// independent of bit width, load instruction into four 8-bit registers over four cycles
fopen #(8) ir0(clk, irwrite[0], memdata[7:0], instr[7:0]);
fopen #(8) ir1(clk, irwrite[1], memdata[7:0], instr[15:8]);
fopen #(8) ir2(clk, irwrite[2], memdata[7:0], instr[23:16]);
fopen #(8) ir3(clk, irwrite[3], memdata[7:0], instr[31:24]);

// datapath
fopenr #(WIDTH) pcreg(clk, reset, pcen, nextpc, pc);
flop #(WIDTH) mdr(clk, memdata, md);
flop #(WIDTH) areg(clk, rd1, a);
flop #(WIDTH) wrd(clk, rd2, writedata);
flop #(WIDTH) res(clk, aluresult, aluout);
mux2 #(WIDTH) adrmux(pc, aluout, iord, adr);
mux2 #(WIDTH) src1mux(pc, a, alusrcA, src1);
mux4 #(WIDTH) src2mux(writedata, CONST_ONE, instr[WIDTH-1:0], constb4, alusrcB, src2);
mux4 #(WIDTH) pcmux(aluresult, aluout, constb4, CONST_ZERO, pcsource, nextpc);
mux2 #(WIDTH) wdmux(aluout, md, memtoreg, wd);
regfile #(WIDTH,REGBITS) rf(clk, regwrite, ra1, ra2, wa, wd, rd1, rd2);
alu #(WIDTH) alunit(src1, src2, alucont, aluresult);
zerodetect #(WIDTH) zd(aluresult, zero);
endmodule

```

## Verilog: Datapath 2

### MIPS Microarchitecture - ALU

 

## Verilog: alu

```


module alu #(parameter WIDTH = 8)
  (input [WIDTH-1:0] a, b,
   input [2:0] alucont,
   output reg [WIDTH-1:0] result);
  wire [WIDTH-1:0] b2, sum, slt;

  assign b2 = alucont[2] ? ~b:b; // pre-compute B-inv for subtraction
  assign sum = a + b2 + alucont[2]; // A + B or A + Binv + 1 (i.e. subtraction)
  // slt should be 1 if most significant bit of sum is 1
  assign slt = sum[WIDTH-1];

  always@(*) // compute ALU result (based on alucont bits)
    case(alucont[1:0])
      2'b00: result <= a & b;
      2'b01: result <= a | b;
      2'b10: result <= sum;
      2'b11: result <= slt;
    endcase
  endmodule

```

## MIPS Microarchitecture - ALUctl

 


## Verilog: alucontrol

```
module alucontrol(input [1:0] aluop, input [5:0] funct, output reg [2:0] alucont);

    always @(*)
        case(aluop)
            2'b00: alucont <= 3'b010;           // add for lb/sb/addi
            2'b01: alucont <= 3'b110;           // sub (for beq)
            default: case(funct)               // R-Type instructions
                6'b100000: alucont <= 3'b010; // add (for add)
                6'b100010: alucont <= 3'b110; // subtract (for sub)
                6'b100100: alucont <= 3'b000; // logical and (for and)
                6'b100101: alucont <= 3'b001; // logical or (for or)
                6'b101010: alucont <= 3'b111; // set on less (for slt)
                default: alucont <= 3'b101;   // should never happen
        endcase
    endcase
endmodule
```

## MIPS Microarchitecture - Regfile

 

## Verilog: regfile

```
module regfile #(parameter WIDTH = 8, REGBITS = 3)
    (input      clk,
     input      regwrite,
     input [REGBITS-1:0] ra1, ra2, wa,
     input [WIDTH-1:0] wd,
     output [WIDTH-1:0] rd1, rd2);

    reg [WIDTH-1:0] RAM [(1<<REGBITS)-1:0];

    // three ported register file
    // read two ports (combinational)
    // write third port on rising edge of clock
    always @(posedge clk)
        if (regwrite) RAM[wa] <= wd;

    assign rd1 = ra1 ? RAM[ra1] : 0; // register 0 is hardwired to 0
    assign rd2 = ra2 ? RAM[ra2] : 0; // register 0 is hardwired to 0

endmodule
```

## Verilog: Support Structures

```
module zerodetect #(parameter WIDTH = 8)
    (input [WIDTH-1:0] a,
     output      y);
    assign y = (a==0);
endmodule

module flop #(parameter WIDTH = 8)
    (input      clk,
     input      d,
     output reg [WIDTH-1:0] q);
    always @(posedge clk)
        q <= d;
endmodule

module flopen #(parameter WIDTH = 8)
    (input      clk, en,
     input      d,
     output reg [WIDTH-1:0] q);
    always @(posedge clk)
        if (en) q <= d;
endmodule


module flopnr #(parameter WIDTH = 8)
    (input      clk, reset, en,
     input      d,
     output reg [WIDTH-1:0] q);
    always @(posedge clk)
        if (reset) q <= 0;
        else if (en) q <= d;
endmodule

module mux2 #(parameter WIDTH = 8)
    (input [WIDTH-1:0] d0, d1,
     input      s,
     output      y);
    assign y = s ? d1 : d0;
endmodule

module mux4 #(parameter WIDTH = 8)
    (input [WIDTH-1:0] d0, d1, d2, d3,
     input [1:0]      s,
     output reg [WIDTH-1:0] y);
    always @(*)
        case(s)
            2'b00: y <= d0;
            2'b01: y <= d1;
            2'b10: y <= d2;
            2'b11: y <= d3;
        endcase
endmodule
```
 
## Logic Design

- ◆ Start at top level
  - Hierarchically decompose MIPS into units
- ◆ Top-level interface



## Verilog: exmemory simulation

```
// external memory accessed by MIPS
module exmemory #(parameter WIDTH = 8)
  (clk, memwrite, adr, writedata, memdata);
  input      clk;
  input      memwrite;
  input [WIDTH-1:0] adr, writedata;
  output reg [WIDTH-1:0] memdata;
  reg [31:0] RAM [(1<<WIDTH-2)-1:0];
  wire [31:0] word;

  initial
    begin
      $readmemh("memfile.dat",RAM);
    end

// read and write bytes from 32-bit word
  always @(posedge clk)
    if(memwrite)
      case (adr[1:0])
        2'b00: RAM[adr>>2][7:0] <= writedata;
        2'b01: RAM[adr>>2][15:8] <= writedata;
        2'b10: RAM[adr>>2][23:16] <= writedata;
        2'b11: RAM[adr>>2][31:24] <= writedata;
      endcase
      assign word = RAM[adr>>2];
    always @(*)
      case (adr[1:0])
        2'b00: memdata <= word[7:0];
        2'b01: memdata <= word[15:8];
        2'b10: memdata <= word[23:16];
        2'b11: memdata <= word[31:24];
      endcase
    endmodule
```


## Synthesized memory?

- ◆ If you synthesize the Verilog, you'll get a memory
  - But – it will be huge!
  - It will be made of your DFF cells
  - plus synthesized address decoders
  
- Custom memory is much smaller
- but much trickier to get right
- ... see details in VGA slides ...

## Verilog: exmemory


```
// external memory accessed by MIPS
module exmem #(parameter WIDTH = 8)
    (clk, memwrite, adr, writedata,
     memdata);
    input      clk;
    input      memwrite;
    input [WIDTH-1:0] adr, writedata;
    output [WIDTH-1:0] memdata;
    wire memwriteB, clkB;
    // UMC RAM has active low write enable...
    not(memwriteB, memwrite);
    // Looks like you need to clock the memory early
    // to make it work with the current control...
    not(clkB, clk);
    // Instantiate the UMC SPRAM module
    UMC130SPRAM_8_8 mips_ram (
        .CK(clkB),
        .CEN(1'b0),
        .WEN(memwriteB),
        .OEN(1'b0),
        .ADR(adr),
        .DI(writedata),
        .DOUT(memdata));
endmodule
```

## MIPS (8-bit) size comparison

 


One big EDI run of the whole thing  
With some work, could probably get this in a single TCU...

## MIPS (8-bit) size comparison

 

Separate EDI for controller, alucontrol, datapath  
and custom RF, assembled with ccar

## MIPS (8-bit) whole chip

 

Includes poly/m1/m2/m3 fill, and logos  
Routed to the pads using ccar

## System Verilog

- ◆ Enhanced version of “classic Verilog”
  - More data types
    - typedef, struct, union, enum
  - Some OO features
  - Adds better support for verification
- ◆ Backward compatible with Verilog

## New data type: logic

- ◆ “logic” as a data type is like a reg
  - But can be used everywhere, not just in sequential blocks (always, initial)
  - It must have a single driver – only one gate driving the value (like a logic value!)
  - If you have more than one driver (think tri-state), then it must be a “wire”

```
logic [7:0] my_var; // 8-bit logic type variable
```

## mips module definition

```
// simplified MIPS processor
module mips #(parameter WIDTH = 8, REGBITS = 3)
    (input logic clk, reset,
     input logic [WIDTH-1:0] memdata,
     output logic memread, memwrite,
     output logic [WIDTH-1:0] adr, writedata);

    logic [31:0] instr;
    logic zero, alusrc, memtoreg, iord, pcen, regwrite, regdst;
    logic [1:0] psrc, alusrb;
    logic [3:0] irwite;
    logic [2:0] alucontrol;
    logic [5:0] op, funct;
    assign op = instr[31:26];
    assign funct = instr[5:0];
    controller cont(clk, reset, op, funct, zero, memread, memwrite,
                    alusrc, memtoreg, iord, pcen, regwrite, regdst,
                    psrc, alusrb, alucontrol, irwite);
    datapath #(WIDTH, REGBITS)
        dp(clk, reset, memdata, alusrc, memtoreg, iord, pcen,
            regwrite, regdst, psrc, alusrb, irwite, alucontrol,
            zero, instr, adr, writedata);
endmodule
```

## C-type Data Structuring

- ◆ Enumerated data types allow numeric quantities to be assigned meaningful names
  - Like “parameters” in Verilog


```
typedef enum logic [2:0] {  
    RED, GREEN, BLUE, CYAN, MAGENTA, YELLOW  
} color_t;  
color_t my_color = GREEN;  
initial $display("The color is %s", my_color.name());  
// note the use of the name() built-in function
```

## C-type Data Structuring

- ◆ Structs are like C structs...

```
typedef struct {  
    byte a;  
    reg b;  
    shortint unsigned c;  
} myStruct;  
  
module struct_data ();  
// Define a local struct.  
struct {  
    byte a;  
    reg b;  
    shortint unsigned c;  
} myLocalStruct = '{11,1,101};  
  
initial begin  
    $display ("a = %b b = %b c = %h", object.a, object.b, object.c);  
    $display ("a = %b b = %b c = %h", myLocalStruct.a,  
             myLocalStruct.b, myLocalStruct.c);  
    #1 $finish;  
end  
endmodule
```

 Disclaimer – I don't know much about how these interact with synthesis...



Controller  
Parameters:  
Verilog

```

module controller(input clk, reset,
                  input [5:0] op,
                  input zero,
                  output reg memread, memwrite, alusrcA, memtoreg, lrd,
                  output reg poen,
                  output reg rewrite, regdst,
                  output reg [1:0] pcsource, alusrcB, aluop,
                  output reg [3:0] iwrite);

parameter F1 = 4'b0001;
parameter F2 = 4'b0010;
parameter F3 = 4'b0011;
parameter F4 = 4'b0100;
parameter DECODE = 4'b0101;
parameter MEMADR = 4'b0110;
parameter LBRD = 4'b0111;
parameter LBWR = 4'b1000;
parameter SBWR = 4'b1001;
parameter RTYPEEX = 4'b1010;
parameter RTYPEWR = 4'b1011;
parameter BEQEX = 4'b1100;
parameter JEX = 4'b1101;
parameter ADDIWR = 4'b1110; // added for ADDI

parameter LB = 6'b100000;
parameter SB = 6'b101000;
parameter RTYPE = 6'b0;
parameter BEQ = 6'b0000100;
parameter J = 6'b0000010;
parameter ADDI = 6'b001000; // added for ADDI

reg [3:0] state, nextstate;
reg pcwrite, pcwritecond;

```

State Encodings...  
Opcodes...  
Local reg variables...

System Verilog Version

```

// states and instructions
typedef enum logic [3:0] {F1 = 4'b0000, F2, F3, F4,
                           DECODE, MEMADR, LBRD, LBWR, SBWR,
                           RTYPEEX, RTYPEWR, BEQEX, JEX} statetype;

typedef enum logic [5:0] {LB = 6'b100000,
                        SB = 6'b101000,
                        RTYPE = 6'b000000,
                        BEQ = 6'b0000100,
                        J = 6'b0000010} opcode;

typedef enum logic [5:0] {ADD = 6'b100000,
                        SUB = 6'b100010,
                        AND = 6'b100100,
                        OR = 6'b100101,
                        SLT = 6'b101010} functcode;

```

## SystemVerilog Version

```
module controller(input logic clk, reset,
                  input logic [5:0] op, funct,
                  input logic zero,
                  output logic memread, memwrite, alusrca,
                  output logic memtoreg, iord, pcen,
                  output logic regwrite, regdst,
                  output logic [1:0] psrc, alusrcb,
                  output logic [2:0] alucontrol,
                  output logic [3:0] irwrite);
    statetype state;
    logic pcwrite, branch;
    logic [1:0] aluop;
    // control FSM
    statelogic statelog(clk, reset, op, state);
    outputlogic outputlog(state, memread, memwrite, alusrca,
                           memtoreg, iord,
                           regwrite, regdst, psrc, alusrcb, irwrite,
                           pcwrite, branch, aluop);
    // other control decoding
    aludec ac(aluop, funct, alucontrol);
    assign pcen = pcwrite | (branch & zero); // program counter enable
endmodule
```

## New Sequential Blocks

### ◆ Old: Verilog

- `always @(*)` // combinational
- `always @(posedge clk)` // sequential (latch or ff)

### ◆ New: SystemVerilog

- `always_comb` // combinational – like `@(*)`
- `always_ff @(posedge clk)` // sequential with ff
- `always_latch` // level-sensitive latch  
// gate inferred from the code  
// don't use this one...

## NS logic: Verilog

```
// state register
always @(posedge clk)
  if(reset) state <= FETCH1;
  else state <= nextstate;

// next state logic (combinational)
always @(*)
begin
  case(state)
    FETCH1: nextstate <= FETCH2;
    FETCH2: nextstate <= FETCH3;
    FETCH3: nextstate <= FETCH4;
    FETCH4: nextstate <= DECODE;
    DECODE: case(op)
      LB:   nextstate <= MEMADR;
      SB:   nextstate <= MEMADR;
      ADDI:  nextstate <= MEMADR;
      RTYPE: nextstate <= RTYPEEX;
      BEQ:  nextstate <= BEQEX;
      J:    nextstate <= JEX;
    // should never happen
    default: nextstate <= FETCH1;
  endcase
end

MEMADR: case(op)
  LB:   nextstate <= LBRD;
  SB:   nextstate <= SBWR;
  ADDI:  nextstate <= ADDIWR;
  // should never happen
  default: nextstate <= FETCH1;
endcase

LBRD: nextstate <= LBWR;
LBWR: nextstate <= FETCH1;
SBWR: nextstate <= FETCH1;
RTYPEEX: nextstate <= RTYPEWR;
RTYPEWR: nextstate <= FETCH1;
BEQEX: nextstate <= FETCH1;
JEX:   nextstate <= FETCH1;
ADDIWR: nextstate <= FETCH1;
// should never happen
default: nextstate <= FETCH1;
endcase
end
```

## NS logic: SystemVerilog

```
module statelogic(input logic clk, reset,
                   input logic [5:0] op,
                   output statetype state);
  statetype nextstate;
  always_ff @(posedge clk)
    if (reset) state <= FETCH1;
    else state <= nextstate;
  always_comb
    begin
      case (state)
        FETCH1: nextstate = FETCH2;
        FETCH2: nextstate = FETCH3;
        FETCH3: nextstate = FETCH4;
        FETCH4: nextstate = DECODE;
        DECODE: case(op)
          LB:   nextstate = MEMADR;
          SB:   nextstate = MEMADR;
          RTYPE: nextstate = RTYPEEX;
          BEQ:  nextstate = BEQEX;
          J:    nextstate = JEX;
        // should never happen
      endcase
    end
  endmodule
```

## Outputs: Verilog

```
always @(*)  
begin  
    // set all outputs to zero, then  
    // conditionally assert just the  
    // appropriate ones  
    iwrite <= 4'b0000;  
    pcwrite <= 0; pcwritecond <= 0;  
    regwrite <= 0; regdst <= 0;  
    memread <= 0; memwrite <= 0;  
    alusrca <= 0; alusrcb <= 2'b00;  
    aluop <= 2'b00; pcsrce <= 2'b00;  
    iord <= 0; memtoreg <= 0;  
    case(state)  
        FETCH1:  
            begin  
                memread <= 1;  
                iwrite <= 4'b0001;  
                alusrcb <= 2'b01;  
                pcwrite <= 1;  
            end  
        FETCH2:  
            begin  
                memread <= 1;  
                iwrite <= 4'b0010;  
                alusrcb <= 2'b01;  
                pcwrite <= 1;  
            end  
        FETCH3:  
            begin  
                memread <= 1;  
                iwrite <= 4'b0100;  
                alusrcb <= 2'b01;  
                pcwrite <= 1;  
            end  
        FETCH4:  
            begin  
                memread <= 1;  
                iwrite <= 4'b1000;  
                alusrcb <= 2'b01;  
                pcwrite <= 1;  
            end  
        DECODE: alusrcb <= 2'b11;  
        ....  
    endcase  
end  
endmodule
```

## Outputs: SystemVerilog

```
module outputlogic(input statetype state,  
                  output logic memread, memwrite, alusrca,  
                  output logic memtoreg, iord,  
                  output logic regwrite, regdst,  
                  output logic [1:0] pcsrce, alusrcb,  
                  output logic [3:0] iwrite,  
                  output logic pcwrite, branch,  
                  output logic [1:0] aluop);  
  
    always_comb  
    begin  
        // set all outputs to zero, then  
        // conditionally assert just the appropriate ones  
        iwrite = 4'b0000;  
        pcwrite = 0; branch = 0;  
        regwrite = 0; regdst = 0;  
        memread = 0; memwrite = 0;  
        alusrca = 0; alusrcb = 2'b00; aluop = 2'b00;  
        pcsrce = 2'b00;  
        iord = 0; memtoreg = 0;  
        case (state)  
            FETCH1:  
                begin  
                    memread = 1;  
                    iwrite = 4'b0001;  
                    alusrcb = 2'b01;  
                    pcwrite = 1;  
                end  
            FETCH2:  
                begin  
                    memread <= 1;  
                    iwrite <= 4'b0010;  
                    alusrcb <= 2'b01;  
                    pcwrite <= 1;  
                end  
            FETCH3:  
                begin  
                    memread <= 1;  
                    iwrite <= 4'b0100;  
                    alusrcb <= 2'b01;  
                    pcwrite <= 1;  
                end  
            FETCH4:  
                begin  
                    memread <= 1;  
                    iwrite <= 4'b1000;  
                    alusrcb <= 2'b01;  
                    pcwrite <= 1;  
                end  
            DECODE: alusrcb <= 2'b11;  
            ....  
        endcase  
    end  
endmodule
```

## Outputs: SystemVerilog

```
module aludec(input logic [1:0] aluop,
               input logic [5:0] funct,
               output logic [2:0] alucontrol);
    always_comb
        case (aluop)
            2'b00: alucontrol = 3'b010; // add for lb/sb/addi
            2'b01: alucontrol = 3'b110; // subtract (for beq)
            default: case(funct)      // R-Type instructions
                ADD: alucontrol = 3'b010;
                SUB: alucontrol = 3'b110;
                AND: alucontrol = 3'b000;
                OR: alucontrol = 3'b001;
                SLT: alucontrol = 3'b111;
                default: alucontrol = 3'b101; // should never happen
        endcase
    endmodule
```

## Flops, etc.: SystemVerilog

```
module flop #(parameter WIDTH = 8)
    (input logic      clk,
     input logic [WIDTH-1:0] d,
     output logic [WIDTH-1:0] q);

    always_ff @(posedge clk)
        q <= d;
endmodule

module flop #(parameter WIDTH = 8)
    (input logic      clk, en,
     input logic [WIDTH-1:0] d,
     output logic [WIDTH-1:0] q);
    always_ff @(posedge clk)
        if (en) q <= d;
endmodule
```