

# CS/ECE 5710/6710



Introduction to Layout  
Inverter Layout Example  
Layout Design Rules




## Composite Layout

- ▶ Drawing the mask layers that will be used by the fabrication folks to make the devices
  - ▶ **Very different from schematics**
    - ▶ In schematics you're describing the **LOGICAL** connections
    - ▶ In layout, you're describing the **PHYSICAL** placement of everything!
  - ▶ **Use colored regions to define the different layers that are patterned onto the silicon**



## N-type Transistor

  


## N-type from the top

 

 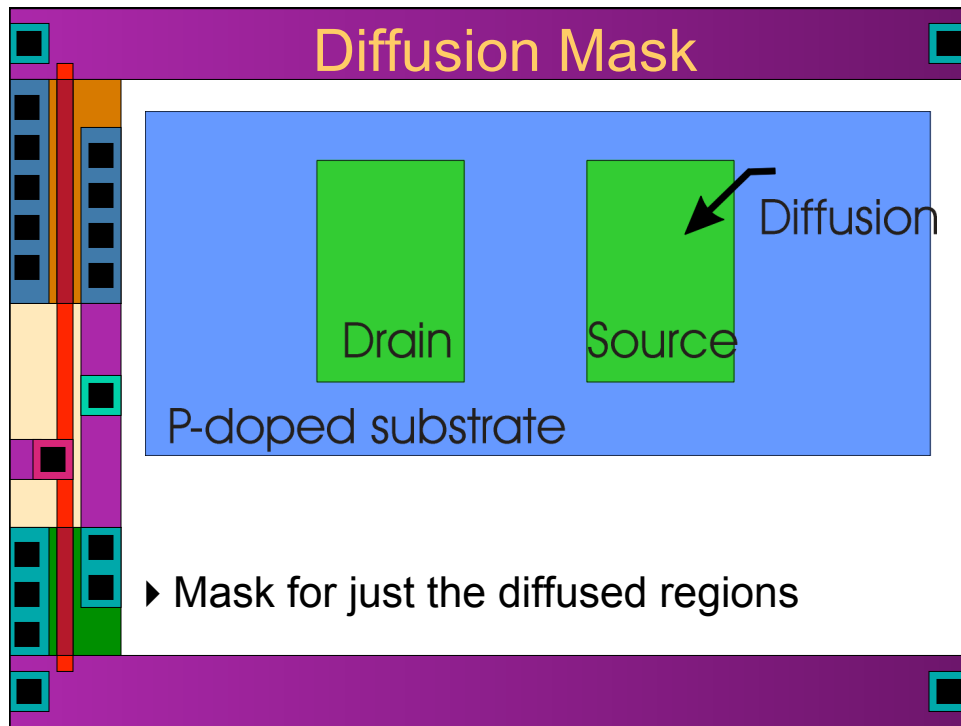- Top view shows patterns that make up the transistor




## Diffusion (active) Mask

 


- Diffused (active) mask is actually drawn as a solid rectangle

## Polysilicon Mask

 


- Polysilicon mask goes on top of the active

## Combine the two masks

 


- ▶ You get an N-type transistor
- ▶ There are other steps in the process...

## P-type transistor

 


- ▶ Same type of masks as the N-type
  - ▶ But, you have to get the substrate right
  - ▶ and you have to dope the diffusion differently

## General CMOS cross section

 


- ▶ Note that the general substrate is P-type
- ▶ The N-substrate for the P-transistor is in a “well”
- ▶ There are lots of other layers
  - ▶ Thick  $\text{SiO}_2$  oxide (“field oxide”)
  - ▶ Thin  $\text{SiO}_2$  oxide (“gate oxide”)
  - ▶ Metal for interconnect

## Cutaway Photo

 

 
## A Cutaway View

- CMOS structure with both transistor types, and top-view structure




## Top View from that Section

 


- Note the different mask layers that correspond to the different transistor layers
  - In particular, note the N-well and P-select layers

## This is an Inverter


 


## Layout in Cadence

 


  - ▶ Draw rectangles to describe mask regions
- ▶ A LOT of things to keep in mind
  - ▶ connectivity, functionality, design rules







## Photo of Interconnect

 

## Back to the Inverter

 


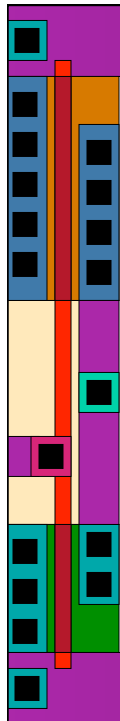- ▶ Let's walk through drawing this inverter
- ▶ You can draw layers in whatever order makes sense to you...


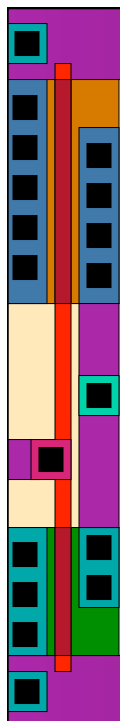
## Layout Basics


- ▶ Where **poly** crosses **active** = transistor
  - ▶ For N-type, **nactive** over the substrate (p substrate)
  - ▶ For P-type, **pactive** inside an Nwell
- ▶ There's really only one "active" mask
  - ▶ nselect and pselect layers define active types
  - ▶ Our setup has separate **nactive** and **pactive** colors to help keep things straight.



## Layout Basics


- ▶ Diffusion, Poly, and metal all conduct
  - ▶ But resistances are very different
    - ▶ Diffusion is worst, poly isn't too bad, metal is by far the best
- ▶ Contact cuts are needed to connect between layers
  - ▶ Make sure to use the right type of contact!
  - ▶ CC for **poly-M1**, **nactive-M1**, **pactive-M1**
  - ▶ Via1 for **M1-M2**
  - ▶ Via2 for **M2-M3**

## First Layout the Power Rails

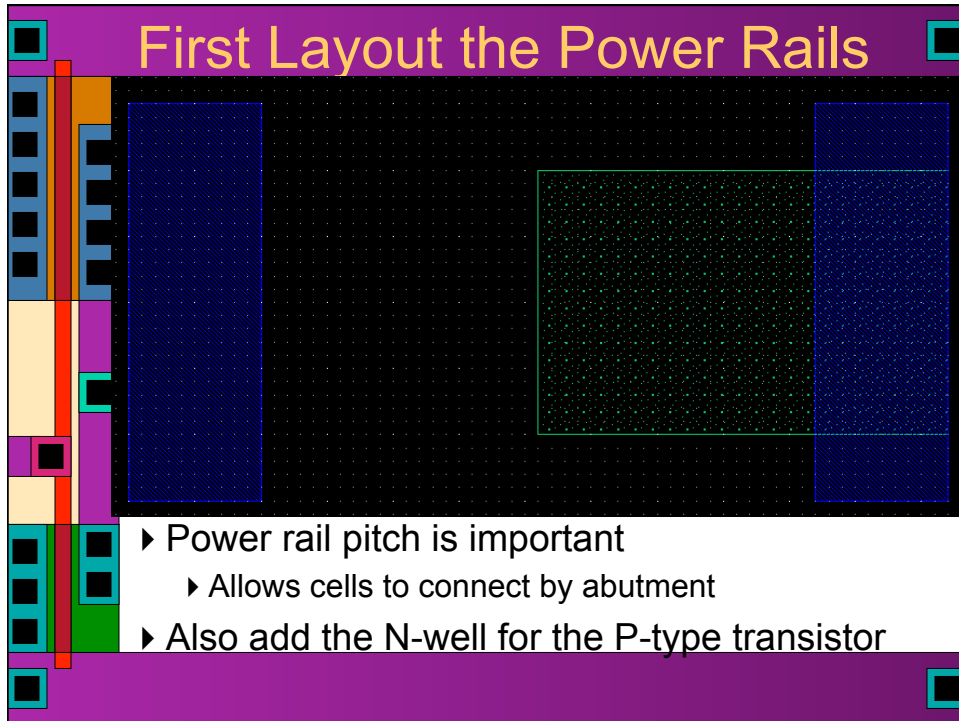


- ▶ Power rail pitch is important
  - ▶ Allows cells to connect by abutment
- ▶ Also add the N-well for the P-type transistor

## Now add Diffusion

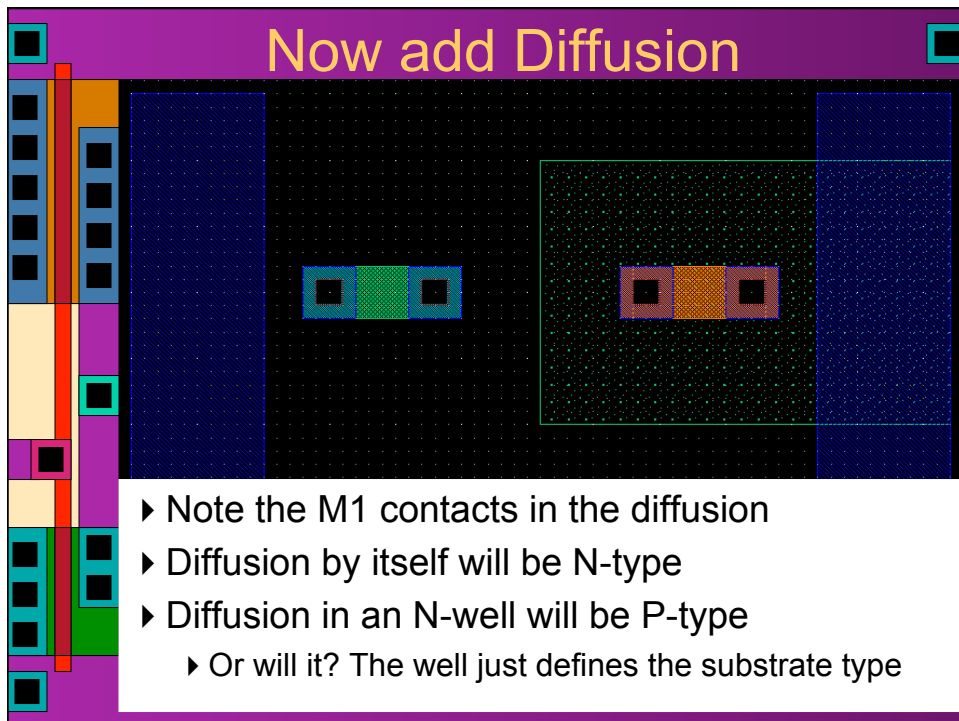


- ▶ Note the M1 contacts in the diffusion
- ▶ Diffusion by itself will be N-type
- ▶ Diffusion in an N-well will be P-type
  - ▶ Or will it? The well just defines the substrate type

## Add the Select Regions

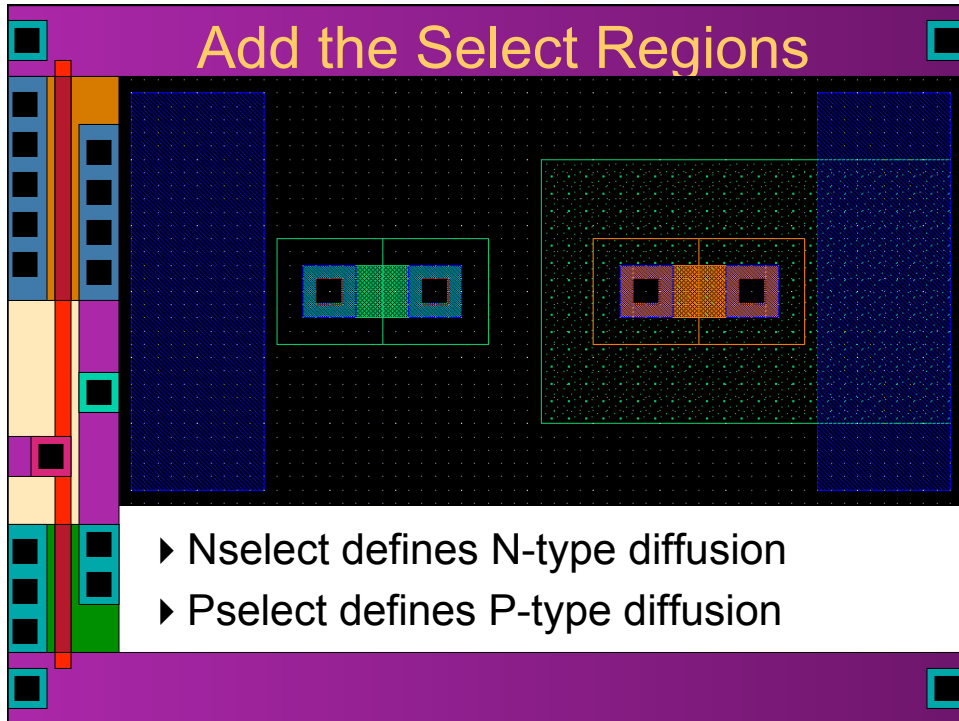


- ▶ Nselect defines N-type diffusion
- ▶ Pselect defines P-type diffusion

## Now add the Poly Gates

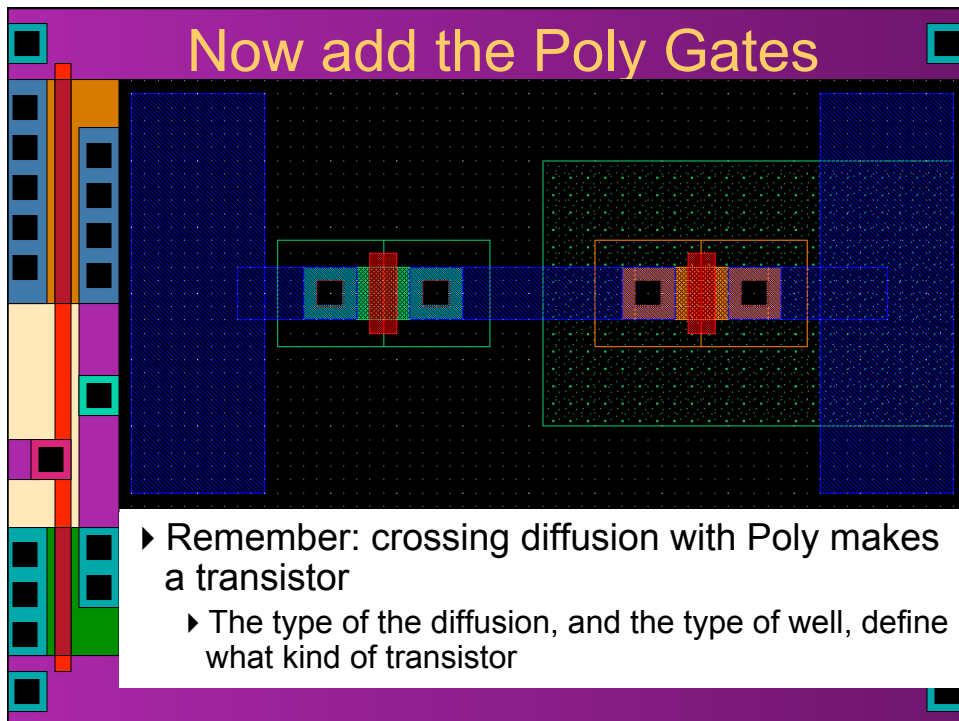


- ▶ Remember: crossing diffusion with Poly makes a transistor
  - ▶ The type of the diffusion, and the type of well, define what kind of transistor

## Note the Metal1 Connections

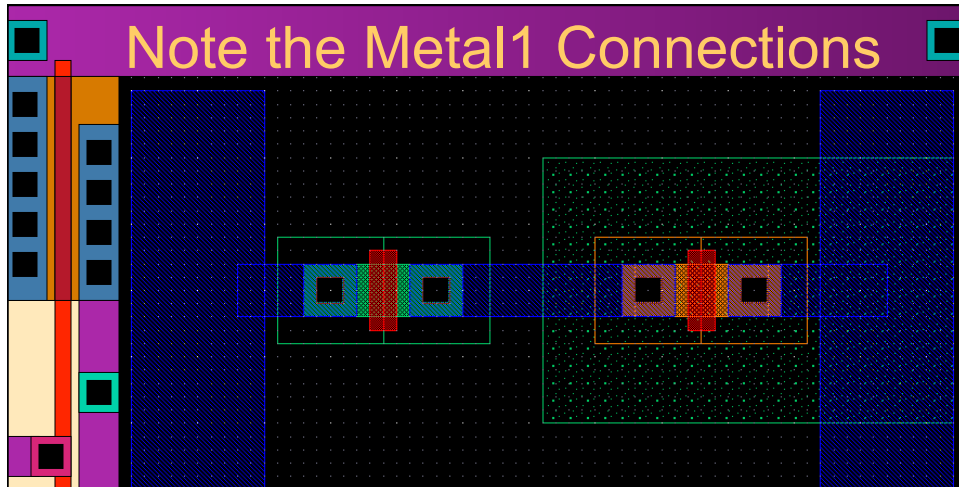

- ▶ Overlapping boxes of the same type of material make a connection
- ▶ Overlaps of different types of material need a contact cut of some sort

## Connect the Gates

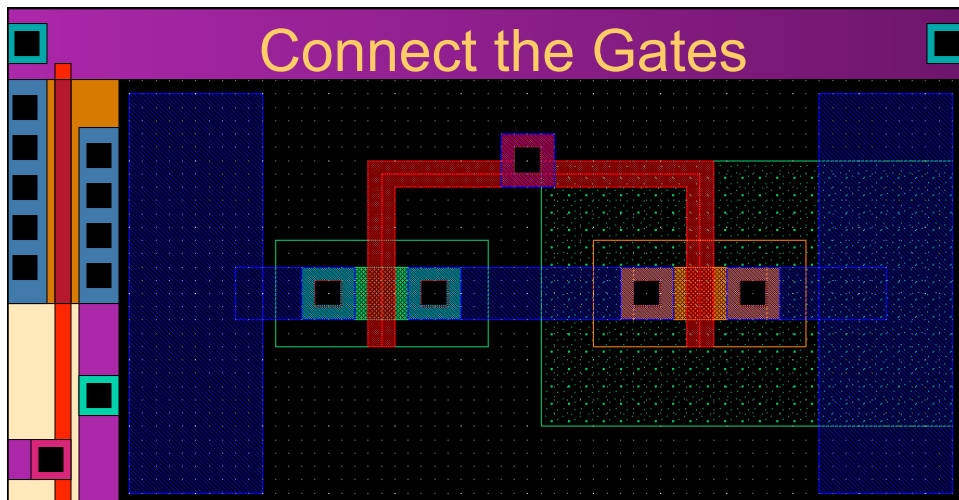

- ▶ Connect gates together to form the inverter
- ▶ Note contact cuts and metal overlaps

## Layout Subtlety

- ▶ We currently think of transistors as three-terminal devices
  - ▶ Gate, Source, Drain
- ▶ They're really four-terminal devices
  - ▶ There's also a connection to the substrate
- ▶ It's important to tie the substrate to a specific voltage
  - ▶ GND for the P-substrate
  - ▶ VDD for the N-well
    - ▶ Make sure PN-diodes from active to substrate and well are reverse-biased...


## Well (or Substrate) Contacts

- ▶ Connect P-substrate to GND (VSS) with a little stub of P-type diffusion (remember pselect)
- ▶ Connect the N-well to VDD with a little stub of N-type diffusion
  - ▶ I.e. inside the N-well, but with nselect



## Layout Design Rules

- ▶ Define the allowed geometry of the different layers
  - ▶ Guidelines for making safe process masks
  - ▶ Rules about the allowed sizes and shapes of a particular layer
  - ▶ Rules about how different layers interact
- ▶ Dimensions listed in one of two ways
  - ▶ Absolute dimensions (e.g. microns or nm)
  - ▶ Scalable dimensions in abstract units
    - ▶ Usually called "lambda"
    - ▶ Design in lambda units, then scale lambda for a particular process


## Intra-Layer Rules (Lambda)

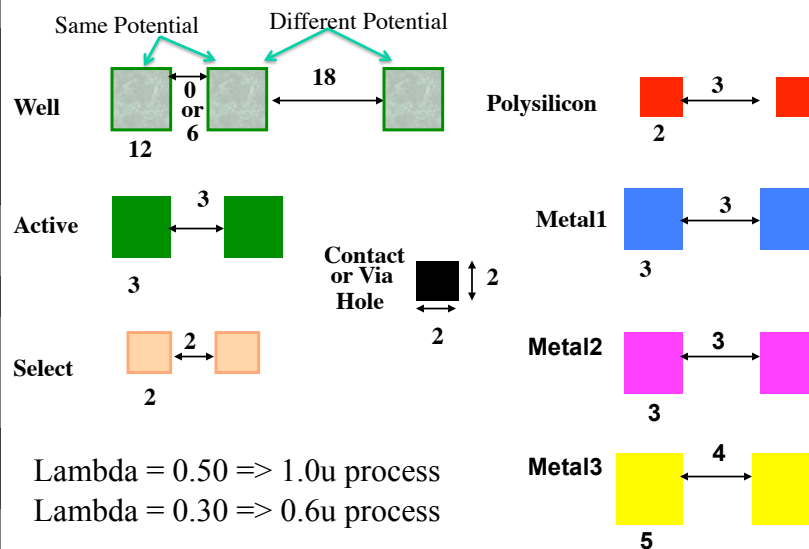




 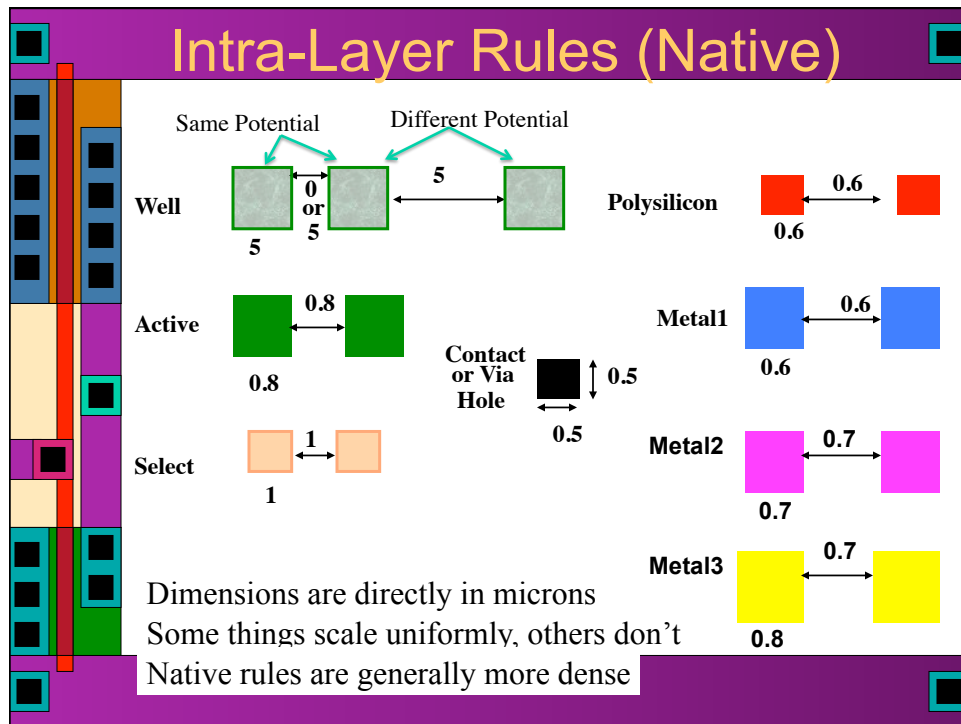

## Vias and Contacts

 

## Look at Inverter Layout Again

 


- Lots and lots of design rules to consider!
  - Use Design Rule Checking (DRC) to see if everything is OK

## Layout Design Rules

- ▶ On the Canvas page
- ▶ Modified version of the MOSIS SCMOS Rev. 8 rules
  - ▶ Modified to show both Lambda and Micron dimensions
  - ▶ All our design will be done in microns
    - ▶ Because of the NCSU tech files
  - ▶ But, even though we're using microns, we're using the SCMOS Lambda rules...
- ▶ Print them out in color if possible!

## SCMOS Nwell

Rule	Description	SUBM	
		Lambda	Microns
1.1	Minimum width	12	3.6
1.2	Minimum spacing between wells at different potential	18	5.4
1.3	Minimum spacing between wells at same potential	6	1.8
1.4	Minimum spacing between wells of different type (if both are drawn)	0	0

 

## SCMOS Active (diffusion)

Rule	Description	SUBM	
		Lambda	Microns
2.1	Minimum width	3	0.9
2.2	Minimum spacing	3	0.9
2.3	Source/drain active to well edge	6	1.8
2.4	Substrate/well contact active to well edge	3	0.9
2.5	Minimum spacing between non-abutting active of different implant. Abutting active ("split-active") is illustrated under <a href="#">Select Layout Rules</a> .	4	1.2


Note: For analog and critical digital designs, MOSIS recommends the minimum MOS *channel widths* (active under poly) to be 10 lambda i.e. 3 microns for submission to AMI ABN and C5N

## SCMOS Poly

Rule	Description	SUBM	
		Lambda	Microns
3.1	Minimum width	2	0.6
3.2	Minimum spacing over field	3	0.9
3.3	Minimum gate extension of active	2	0.6
3.4	Minimum active extension of poly	3	0.9
3.5	Minimum field poly to active	1	0.3

## SCMOS Select

Rule	Description	SUBM	
		SUBM	Microns
4.1	Minimum select spacing to channel of transistor to ensure adequate source/drain width	3	0.9
4.2	Minimum select overlap of active	2	0.6
4.3	Minimum select overlap of contact	1	0.3
4.4	Minimum select width and spacing (Note: P-select and N-select may be coincident, but must <i>not</i> overlap) (not illustrated)	2	0.6

 



\*The same rules apply with N+\_Select and P+\_Select reversed.

## SCMOS Contacts



Rule	Description	SUBM	
		SUBM	Microns
5.1	Exact contact size	2x2	0.6x0.6
5.3	Minimum contact spacing	3	0.9
5.4	Minimum spacing to gate of transistor	2	0.6
5.2.b	Minimum poly overlap	1	0.3
5.5.b	Minimum spacing to other poly	5	1.5
5.6.b	Minimum spacing to active (one contact)	2	0.6
5.7.b	Minimum spacing to active (many contacts)	3	0.9

Rule	Description	SUBM	
		Lambda	Microns
6.1	Exact contact size	2x2	0.6x0.6
6.3	Minimum contact spacing	3	0.9
6.4	Minimum spacing to gate of transistor	2	0.6
6.2.b	Minimum active overlap	1	0.3
6.5.b	Minimum spacing to diffusion active	5	1.5
6.6.b	Minimum spacing to field poly (one contact)	2	0.6
6.7.b	Minimum spacing to field poly (many contacts)	3	0.9
6.8.b	Minimum spacing to poly contact	4	1.2

## SCMOS Contact to Poly

 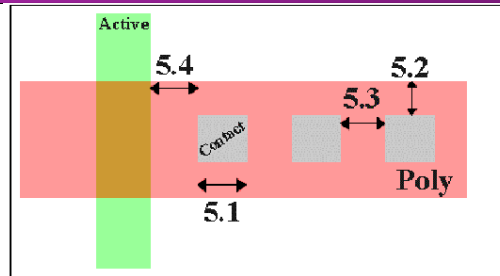


## SCMOS Contact to Active

  

# SCMOS Metal1


Rule	Description	SUBM	
		Lambda	Microns
7.1	Minimum width	3	0.9
7.2	Minimum spacing	3	0.9
7.3	Minimum overlap of any contact	1	0.3
7.4	Minimum spacing when either metal line is wider than 10 lambda	6	1.8

 

# SCMOS Via

Rule	Description	SUBM	
		3+ Metal Process	
		Lambda	Microns
8.1	Exact size	2 x 2	0.6x0.6
8.2	Minimum via1 spacing	3	0.9
8.3	Minimum overlap by metal1	1	0.3
8.5	Minimum spacing to poly or active edge	2	0.6

 Note: Rule 8.4 is not considered for the process we are using since stacked vias are allowed



SCMOS Metal2

Rule	Description	SUBM	
		3+ Metal Process	
		Lambda	Microns
9.1	Minimum width	3	0.9
9.2	Minimum spacing	3	0.9
9.3	Minimum overlap of via1	1	0.3
9.4	Minimum spacing when either metal line is wider than 10 lambda	6	1.8

SCMOS Via2


Rule	Description	SUBM	
		3 Metal Process	
		Lambda	Microns
14.1	Exact size	2x2	0.6x0.6
14.2	Minimum spacing	3	0.9
14.3	Minimum overlap by metal2	1	0.3
14.5	Via2 may be placed over contact		

Note: Rule 14.4 is not considered for the process we are using since stacked vias are allowed




# SCMOS Metal3

Rule	Description	SUBM	
		3 Metal Process	
		Lambda	Microns
15.1	Minimum width	5	1.5
15.2	Minimum spacing to metal3	3	0.9
15.3	Minimum overlap of via2	2	0.6
15.4	Minimum spacing when either metal line is wider than 10 lambda	6	1.8

 


## An Example: NOR

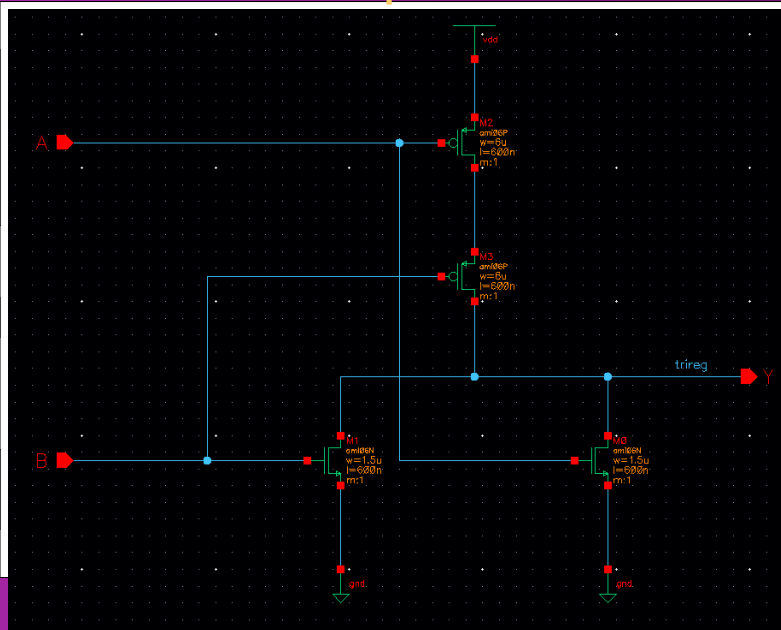
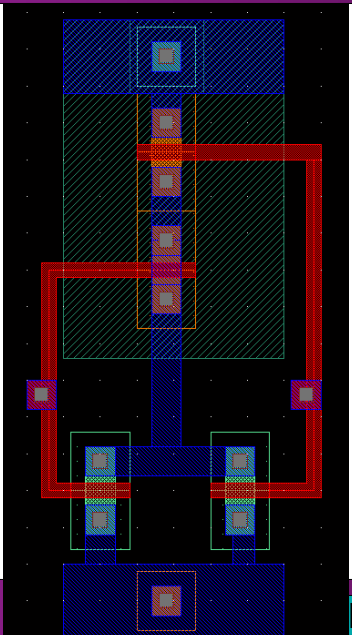
## First Layout: Follow Schematic


- ▶ Note that layout of transistors follows the schematic
  - ▶ Two P-types in series pulling up
  - ▶ Two N-types in parallel pulling down





The diagram shows a circuit layout on a black background. A red line represents the power supply rail, running vertically on the left and then horizontally across the top. A blue line represents the ground rail, running vertically on the right and then horizontally across the bottom. Four transistors are shown: two P-type transistors (represented by blue squares with a cross) are connected in series between the power and ground rails, pulling the signal up. Two N-type transistors (represented by green squares with a cross) are connected in parallel between the signal node and the ground rail, pulling the signal down. The layout is organized to match the schematic.


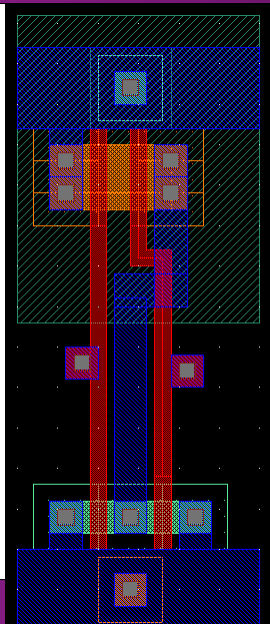
## Another Layout: Better?

- ▶ Same four transistors
  - ▶ But, organized a little differently
  - ▶ And sized a little differently



The diagram shows a circuit layout on a black background. A red line represents the power supply rail, running vertically on the left and then horizontally across the top. A blue line represents the ground rail, running vertically on the right and then horizontally across the bottom. Four transistors are shown: two P-type transistors (represented by blue squares with a cross) are connected in series between the power and ground rails, pulling the signal up. Two N-type transistors (represented by green squares with a cross) are connected in parallel between the signal node and the ground rail, pulling the signal down. The layout is organized differently from the first one, with the transistors arranged in a more compact and efficient manner.

 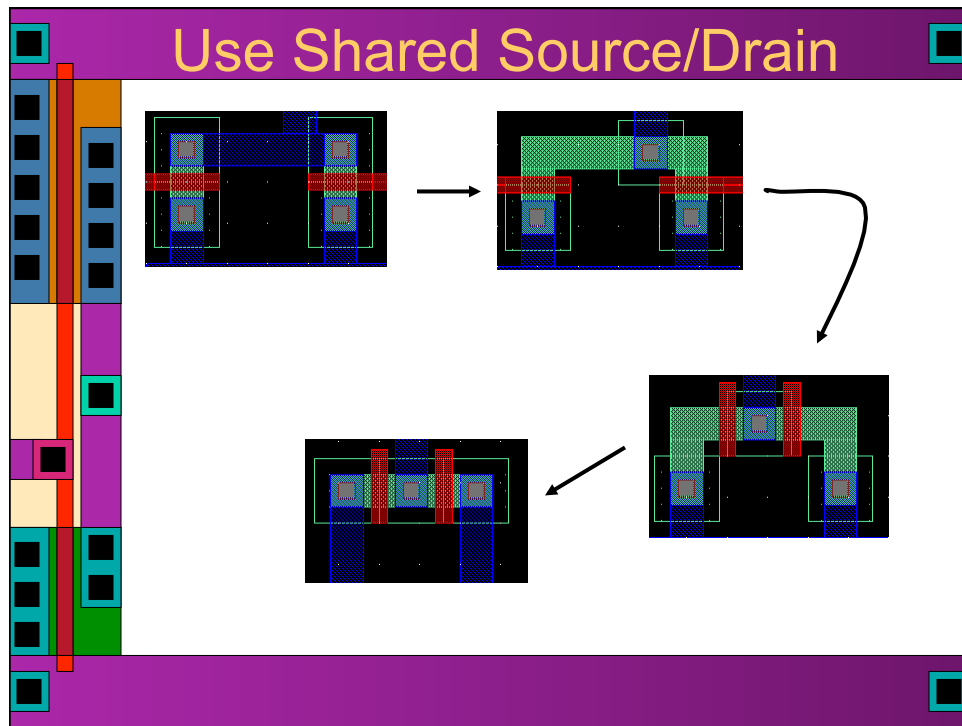

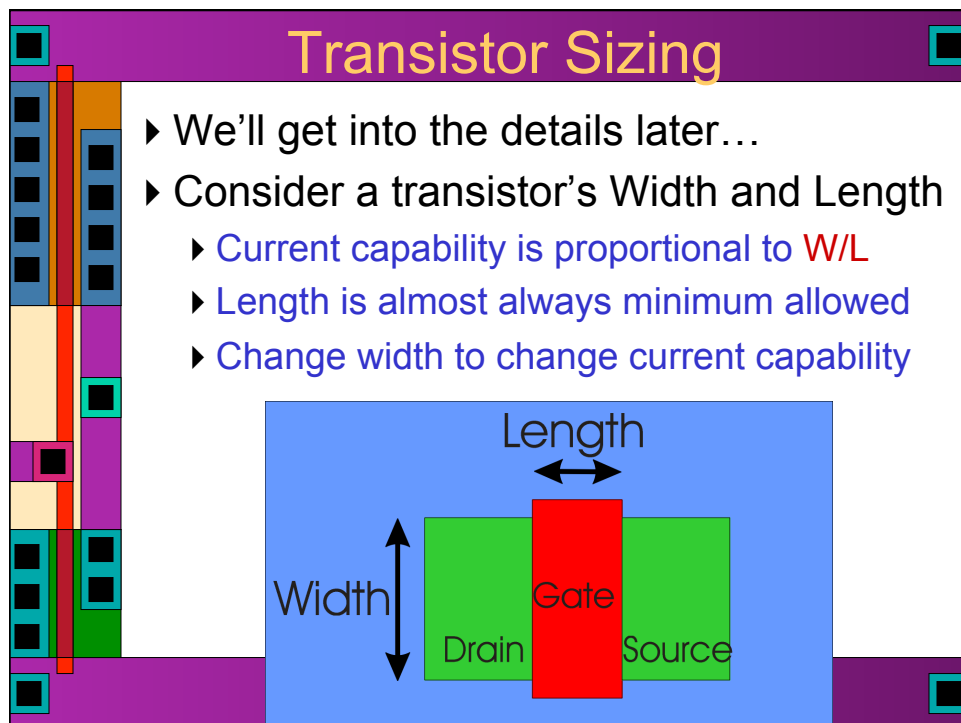 

## Sizing Rule of Thumb

- ▶ Also, P-type is about twice as bad as N-type
  - ▶ Has to do with hole mobility vs. electron mobility
- ▶ So, make P-types twice as wide as N-types to start with
- ▶ Unit size for transistors this semester
  - ▶ N-type  $1.5\mu$  (contact pitch is  $1.2\mu$ )
  - ▶ P-type  $3\mu$

## Sizing Rule of Thumb

- ▶ Now multiply each width by  $n$  for a series stack of  $n$  transistors.
  - ▶ Stack of 2 in series, each transistor should be 2x unit size
  - ▶ Stack of 3 in series, each transistor should be 3x unit size
- ▶ This is because series connections are like increasing the  $L$  of the device...
  - ▶ Current is proportional to  $W/L$

For example:

- ▶ Notice the difference in width...
- ▶ This roughly equalizes the current sourcing capability of pull-up and pull-down stacks in this gate