Homework 3 Spring 2019 Solutions

Exercise 1. 40 pts

We can use Shannon's expansion with respect to two variables inorder to derive the circuit implementation using only 4-to-1 multiplexors. The general format for this expansion is as follows:

$$f(x_3, x_2, x_1, x_0) = \overline{x}_1 \overline{x}_0 f_{\overline{x}_1 \overline{x}_0} + \overline{x}_1 x_0 f_{\overline{x}_1 x_0} + x_1 \overline{x}_0 f_{x_1 \overline{x}_0} + x_1 x_0 f_{x_1 x_0}$$

The resulting 4-to-1 multiplexor would then have the following format:



Figure 1: Generalized 4-to-1 mux

Using this template, we can solve for the four given functions.

$$sum_{1} = a_{1} + b_{1} + a_{0}b_{0}$$

= $\overline{a}_{1}\overline{a}_{0}sum_{1\overline{a}_{1}\overline{a}_{0}} + \overline{a}_{1}a_{0}sum_{1\overline{a}_{1}a_{0}} + a_{1}\overline{a}_{0}sum_{1a_{1}\overline{a}_{0}} + a_{1}a_{0}sum_{1a_{1}a_{0}}$
= $\overline{a}_{1}\overline{a}_{0}(b_{1}) + \overline{a}_{1}a_{0}(b_{0} + b_{1}) + a_{1}\overline{a}_{0}(1) + a_{1}a_{0}(1)$

We have to perform Shannon's expansion again, since the third cofactor is not a constant and contains more than one cube. Since we are implementing with 4-to-1 multiplexors only, we need to expand with respect to the remaining two variables.

$$g = b_0 + b_1$$

= $\overline{b}_1 \overline{b}_0 g_{\overline{b}_1 \overline{b}_0} + \overline{b}_1 b_0 g_{\overline{b}_1 b_0} + b_1 \overline{b}_0 g_{b_1 \overline{b}_0} + b_1 b_0 g_{b_1 b_0}$
= $\overline{b}_1 \overline{b}_0(0) + \overline{b}_1 b_0(1) + b_1 \overline{b}_0(1) + b_1 b_0(1)$



Figure 2: Implementation of sum₁ using only 4-to-1 multiplexors

The next equation only contains two variables, so we will expand using the two variables.

$$sum_{0} = \overline{a}_{0}b_{0} + a_{0}\overline{b}_{0}$$

= $\overline{a}_{0}\overline{b}_{0}sum_{0\overline{a}_{0}\overline{b}_{0}} + \overline{a}_{0}b_{0}sum_{0\overline{a}_{0}b_{0}} + a_{0}\overline{b}_{0}sum_{0a_{0}\overline{b}_{0}} + a_{1}b_{0}sum_{0a_{0}b_{0}}$
= $\overline{a}_{0}\overline{b}_{0}(0) + \overline{a}_{0}b_{0}(1) + a_{0}\overline{b}_{0}(1) + a_{0}b_{0}(0)$



Figure 3: Implementation of sum₀ using only 4-to-1 multiplexors

$$\begin{aligned} \operatorname{diff}_{1} &= a_{1}a_{0}\overline{b_{1}} + a_{1}\overline{a_{0}}\overline{b_{1}} \ \overline{b_{0}} \\ &= \overline{a_{0}}\overline{b_{0}}diff_{1\overline{a_{0}}\overline{b_{0}}} + \overline{a_{0}}b_{0}diff_{1\overline{a_{0}}b_{0}} + a_{0}\overline{b_{0}}diff_{1a_{0}\overline{b_{0}}} + a_{0}b_{0}diff_{1a_{0}b_{0}} \\ &= \overline{a_{0}}\overline{b}_{0}(a_{1}\overline{b_{1}}) + \overline{a_{0}}b_{0}(0) + a_{0}\overline{b}_{0}(a_{1}\overline{b_{1}}) + a_{0}b_{0}(a_{1}\overline{b_{1}}) \end{aligned}$$

The fourth expression needs to be expanded further.

$$g = a_1 \overline{b_1}$$

= $\overline{a_1} \overline{b_1} g_{\overline{a_1} \overline{b_1}} + \overline{a_1} b_1 g_{\overline{a_1} b_1} + a_1 \overline{b_1} g_{a_1 \overline{b_1}} + a_1 b_1 g_{a_1 b_1}$
= $\overline{a_1} \overline{b_1}(0) + \overline{a_1} b_1(0) + a_1 \overline{b_1}(1) + a_1 b_1(0)$



Figure 4: Implementation of $diff_1$ using only 4-to-1 multiplexors

The implementation of the last function is next.

$$\begin{split} \operatorname{diff}_{0} &= a_{0}\overline{b_{0}} + \overline{a_{0}}b_{0} \\ &= \overline{a_{0}}\overline{b_{0}}diff_{0\overline{a_{0}}\overline{b_{0}}} + \overline{a_{0}}b_{0}diff_{0\overline{a_{0}}b_{0}} + a_{0}\overline{b_{0}}diff_{0a_{0}\overline{b_{0}}} + a_{0}b_{0}diff_{0a_{0}b_{0}} \\ &= \overline{a_{0}}\overline{b}_{0}(0) + \overline{a_{0}}b_{0}(1) + a_{0}\overline{b}_{0}(1) + a_{0}b_{0}(0) \end{split}$$



Figure 5: Implementation of diff₀ using only 4-to-1 multiplexors

Exercise 2. 15 pts

Simply take Shannon's expansion with respect to each literal in the equation. We have four literals (a_0, b_0, a_1, b_1) , so we need to take Shannon's expansion four times to derive the set minterms covered by $dif f_0$.

$$\begin{aligned} \text{diff}_{0} &= a_{0}b_{0} + \bar{a_{0}}b_{0} \\ &= a_{1}(a_{0}\bar{b_{0}} + \bar{a_{0}}b_{0}) + \bar{a_{1}}(a_{0}\bar{b_{0}} + \bar{a_{0}}b_{0}) & \text{Shannon's on } a_{1} \\ &= a_{0}\bar{b_{0}}a_{1} + \bar{a_{0}}b_{0}a_{1} + a_{0}\bar{b_{0}}\bar{a_{1}} + \bar{a_{0}}b_{0}\bar{a_{1}} & \text{Distributive} \\ &= b_{1}(a_{0}\bar{b_{0}}a_{1} + \bar{a_{0}}b_{0}a_{1} + a_{0}\bar{b_{0}}\bar{a_{1}} + \bar{a_{0}}b_{0}\bar{a_{1}}) + \\ &\bar{b_{1}}(a_{0}\bar{b_{0}}a_{1} + \bar{a_{0}}b_{0}a_{1} + a_{0}\bar{b_{0}}\bar{a_{1}} + \bar{a_{0}}b_{0}\bar{a_{1}}) & \text{Shannon's on } b_{1} \\ &= a_{0}\bar{b_{0}}a_{1}b_{1} + \bar{a_{0}}b_{0}a_{1}b_{1} + a_{0}\bar{b_{0}}\bar{a_{1}}b_{1} + \bar{a_{0}}b_{0}\bar{a_{1}}b_{1} + \bar{a_{0}}b_{0}a_{1}\bar{b_{1}} \\ &\quad + a_{0}\bar{b_{0}}\bar{a_{1}}\bar{b_{1}} + \bar{a_{0}}b_{0}\bar{a_{1}}\bar{b_{1}} & \text{Distributive} \end{aligned}$$

To verify our result, here is a table showing all of the possible inputs to $diff_0$, the output of $diff_0$, and the specific minterm in our equation which covers that particular output.

$a_0b_0a_1b_1$	diff_0	minterms
0000	0	N/A
0001	0	N/A
0010	0	N/A
0011	0	N/A
0100	1	$\bar{a_0}b_0\bar{a_1}\bar{b_1}$
0101	1	$ar{a_0}b_0ar{a_1}b_1$
0110	1	$ar{a_0}b_0a_1ar{b_1}$
0111	1	$\bar{a_0}b_0a_1b_1$
1000	1	$a_0 \bar{b_0} \bar{a_1} \bar{b_1}$
1001	1	$a_0 \bar{b_0} \bar{a_1} b_1$
1010	1	$a_0 \bar{b_0} a_1 \bar{b_1}$
1011	1	$a_0 \bar{b_0} a_1 b_1$
1100	0	N/A
1101	0	N/A
1110	0	N/A
1111	0	N/A

Exercise 3. 15 pts

It is tempting to think that the dual of f_w is $f_{\bar{w}}$, but this is not true. For example, let f(w, x) = wx. Then $f_w = x$ and the dual of f_w is still x whereas $f_{\bar{w}} = 0$. Furtheremore, the notion of just taking one dual to $f = wf_w + \bar{w}f_{\bar{w}}$ is not correct since the dual of the right hand side is equal to the dual of f and not f. So here is a correct couple of proofs. The first directly uses dualization and the second essentially uses it in the form of DeMorgan's law.

The first proof. For notational purposes let a superscript d denote the dual of a function. For example, f^d is the dual of f and $(f_w)^d$ is the dual of f_w . For simplicity, write $(f_w)^d$ as f_w^d . Then, the dual of $f = w f_w + \bar{w} f_{\bar{w}}$ is

$$f^{d} = (w + f^{d}_{w})(\bar{w} + f^{d}_{\bar{w}}).$$

Using the distributive law (and commutativity) on the right hand side gives

$$f^{d} = w\bar{w} + wf^{d}\bar{w} + \bar{w}f^{d}_{w} + f^{d}_{w}f^{d}_{\bar{w}} = wf^{d}\bar{w} + \bar{w}f^{d}_{w} + f^{d}_{w}f^{d}_{\bar{w}}$$

After using dualization again and noting that $(f^d)^d = f$ (that is, taking the dual twice gets back the original function), one gets

$$f = (w + f_{\bar{w}})(\bar{w} + f_w)(f_w + f_{\bar{w}})$$

which yields

$$f = (w + f_{\bar{w}})(\bar{w} + f_w)(f_w + f_{\bar{w}})$$

essentially by consensus.

Now the second proof is like the first, but uses the complement so as not to go into dual

land. It works like this

$$\begin{split} f &= w f_w + \bar{w} f_{\bar{w}} \\ &= \overline{w f_w + \bar{w} f_{\bar{w}}} \\ &= \overline{w f_w + \bar{w} f_{\bar{w}}} \\ &= \overline{(\bar{w} + \bar{f}_w)(w + \bar{f}_{\bar{w}})} \\ &= \overline{(\bar{w} + \bar{w})(w + \bar{f}_w)} \\ &= \overline{w} \bar{w} \bar{w} + \bar{w} \bar{f}_w + \bar{w} \bar{f}_w + \bar{f}_w \bar{f}_{\bar{w}}} \\ &= \overline{w} \bar{f} \bar{w} + w \bar{f}_w + \bar{f}_w \bar{f}_{\bar{w}}} \\ &= (w + f_{\bar{w}})(\bar{w} + f_w)(f_w + f_{\bar{w}}) \\ &= (w + f_{\bar{w}})(\bar{w} + f_w) \\ &= (w + f_{\bar{w}})(\bar{w} + f_w) \\ \end{split}$$

Exercise 4. 30 pts

Verilog solution is not included to avoid explicit copying of code.