

ECE/CS 3700: Fundamentals of Digital System Design


Chris J. Myers

Midterm Review 2

Chapters 5 and 6: Sequential Circuits

- *Combinational* - output depends only on the input.
- *Sequential* - output depends on input and past behavior.
 - Requires use of storage elements.
 - Contents of storage elements is called *state*.
 - Circuit goes through sequence of states as a result of changes in inputs.


Chapter 5: Basic Latch

 

(a) Circuit


S	R	Q_a	Q_b	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	

(b) Truth table

 

(c) Timing diagram


Chapter 5: Gated SR Latch

 


(a) Circuit

Clk	S	R	$Q(t+1)$
0	x	x	$Q(t)$ (no change)
1	0	0	$Q(t)$ (no change)
1	0	1	0
1	1	0	1
1	1	1	x

(b) Characteristic table

 


(c) Timing diagram

 

(d) Graphical symbol


Chapter 5: Gated D Latch

 

(a) Circuit


Clk	D	$Q(t+1)$
0	x	$Q(t)$
1	0	0
1	1	1

(b) Characteristic table

 


(c) Graphical symbol

Chapter 5: Gated D Latch

 


(a) Circuit

 


(d) Timing diagram


Chapter 5: Master-slave D Flip-flop

 

(a) Circuit

 


(c) Graphical symbol

 


 (b) Timing diagram

Chapter 5: Positive-edge-triggered D Flip-flop




(a) Circuit

 


 (b) Graphical symbol


Chapter 5: Flip-flop with Clear and Preset



(a) Circuit

 


(b) Graphical symbol

 


(c) Adding a synchronous clear

Chapter 5: Flip-flop Timing Parameters

 


(a) D flip-flop with asynchronous clear

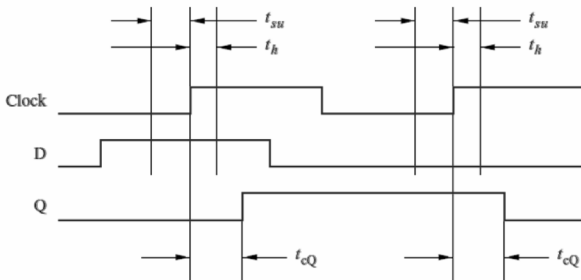

(b) Timing diagram


Chapter 5: T Flip-flop

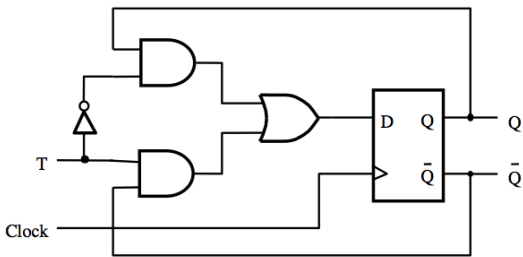


(a) Circuit

T	$Q(t+1)$
0	$\underline{Q}(t)$
1	$\overline{Q}(t)$

(b) Truth table

 


(c) Graphical symbol

 

(d) Timing diagram


Chapter 5: JK Flip-flop

 

(a) Circuit

J	K	$Q(t+1)$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	$\bar{Q}(t)$

(b) Truth table

 


(c) Graphical symbol


Chapter 5: Summary of Terminology

- Basic latch - cross-coupled NAND/NOR
- Gated latch - output changes when $\text{clk} = 1$.
 - Gated SR latch
 - Gated D latch
- Flip-flop - output changes only on clk edge.
 - Edge-triggered flip-flop
 - Master-slave flip-flop

Chapter 5: Registers

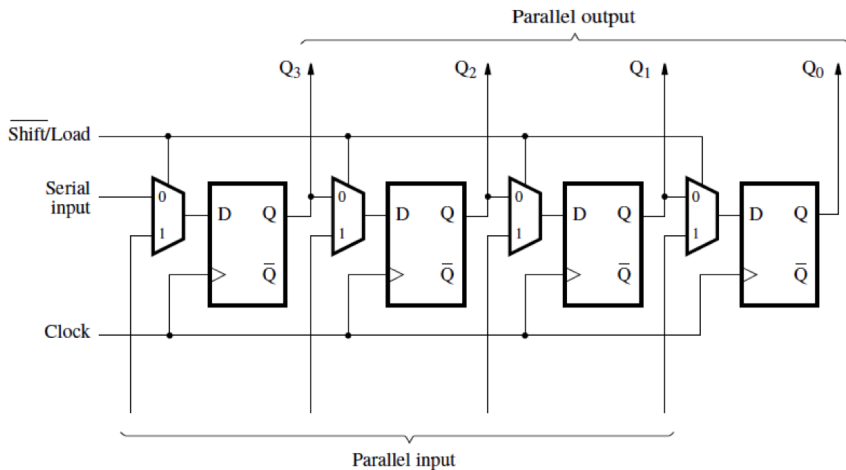

Chapter 5: Counters

 

Chapter 5: Verilog for a Gated D Latch


```
module D_latch (D, Clk, Q);  
    input D, Clk;  
    output reg Q;  
  
    always @(D, Clk)  
        if (Clk)  
            Q = D;  
  
endmodule
```

```
module flipflop (D, Clock, Q);  
    input D, Clock;  
    output reg Q;  
  
    always @(posedge Clock)  
        Q = D;  
  
endmodule
```

Chapter 5: Blocking vs. Non-blocking Assignments

```
module example5_3 (D, Clock, Q1, Q2);  
    input D, Clock;  
    output reg Q1, Q2;  
  
    always @(posedge Clock)  
    begin  
        Q1 = D;  
        Q2 = Q1;  
    end  
  
endmodule
```


Chapter 5: Blocking vs. Non-blocking Assignments

 

Chapter 5: Blocking vs. Non-blocking Assignments

```
module example5_4 (D, Clock, Q1, Q2);  
    input D, Clock;  
    output reg Q1, Q2;  
  
    always @(posedge Clock)  
    begin  
        Q1 <= D;  
        Q2 <= Q1;  
    end  
  
endmodule
```

Chapter 5: Blocking vs. Non-blocking Assignments

 

Chapter 5: Verilog for an n -bit Shift Register

```
module shiftn (R, L, w, Clock, Q);  
    parameter n = 16;  
    input [n-1:0] R;  
    input L, w, Clock;  
    output reg [n-1:0] Q;  
    integer k;  
  
    always @(posedge Clock)  
        if (L)  
            Q <= R;  
        else  
            begin  
                for (k = 0; k < n-1; k = k+1)  
                    Q[k] <= Q[k+1];  
                Q[n-1] <= w;  
            end  
  
    endmodule
```


Chapter 5: Verilog for an Up/Down Counter

```
module updowncount (R, Clock, L, E, up_down, Q);  
  parameter n = 8;  
  input [n-1:0] R;  
  input Clock, L, E, up_down;  
  output reg [n-1:0] Q;  
  always @(posedge Clock)  
    if (L)  
      Q <= R;  
    else if (E)  
      Q <= Q + (up_down ? 1 : -1);  
  
endmodule
```


Chapter 5: Register Transfer Level (RTL) Code

- Can write behavioral code like a computer program.
- This *high-level* behavioral code can make it difficult to predict the circuit that will be synthesized.
- Better to create small design modules from which larger designs are created by connecting them together.
- This approach is known as *register-transfer level* (RTL) style.

Chapter 5: Timing Analysis for a 4-bit Counter

 


 Chapter 5: Timing Analysis for a 4-bit Counter




$$T_{min} = t_{cQ} + 3(t_{AND}) + t_{XOR} + t_{su}$$

 Chapter 5: Timing Analysis for a 4-bit Counter




$$T_{min} = t_{cQ} + 3(t_{AND}) + t_{XOR} + t_{su}$$
$$T_{min} = 1.0 + 3(1.2) + 1.2 + 0.6 \text{ ns} = 6.4 \text{ ns}$$

 Chapter 5: Timing Analysis for a 4-bit Counter



$$\begin{aligned}T_{min} &= t_{cQ} + 3(t_{AND}) + t_{XOR} + t_{su} \\T_{min} &= 1.0 + 3(1.2) + 1.2 + 0.6 \text{ ns} = 6.4 \text{ ns} \\F_{max} &= 1/6.4 \text{ ns} = 156.25 \text{ MHz}\end{aligned}$$

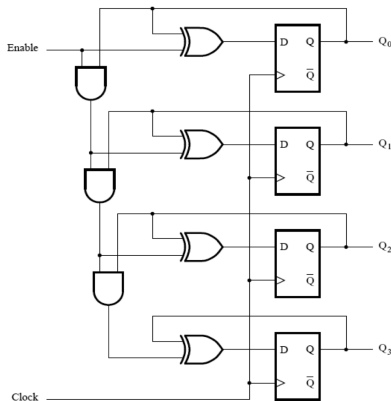Chapter 5: Timing Analysis for a 4-bit Counter




$$T_{min} = t_{cQ} + 3(t_{AND}) + t_{XOR} + t_{su}$$

$$T_{min} = 1.0 + 3(1.2) + 1.2 + 0.6 \text{ ns} = 6.4 \text{ ns}$$

$$F_{max} = 1/6.4 \text{ ns} = 156.25 \text{ MHz}$$

$$t_{cQ} + t_{XOR} = 0.8 + 1.2 = 2.0 \text{ ns} > t_h = 0.4 \text{ ns}$$

Chapter 5: Clock Skew

 

$$t_{skew} = \Delta_2 - \Delta_1$$


$$T_{min} = t_{cQ} + t_L + t_{su} - t_{skew}$$

$$t_{cQ} + t_l > t_h + t_{skew}$$


Chapter 6: Basic Design Steps

- 1 Obtain the specification of the desired circuit.
- 2 Derive a state diagram.
- 3 Derive the corresponding state table.
- 4 Reduce the number of states if possible.
- 5 Decide on the number of state variables.
- 6 Choose the type of flip-flops to be used.
- 7 Derive the logic expressions needed to implement the circuit.

Chapter 6: Basic Design Steps

 

Chapter 6: Basic Design Steps

 

Chapter 6: Basic Design Steps

Present state	Next state		Outputs						
	$w = 0$	$w = 1$	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	<i>Done</i>
A	A	B	0	0	0	0	0	0	0
B	C	C	0	0	1	0	0	1	0
C	D	D	1	0	0	1	0	0	0
D	A	A	0	1	0	0	1	0	1

Chapter 6: Basic Design Steps

	Present state	Next state		Outputs						
		$w = 0$	$w = 1$							
	$y_2 y_1$	$Y_2 Y_1$	$Y_2 Y_1$	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	$Done$
A	00	00	0 1	0	0	0	0	0	0	0
B	01	10	1 0	0	0	1	0	0	1	0
C	10	11	1 1	1	0	0	1	0	0	0
D	11	00	0 0	0	1	0	0	1	0	1

Chapter 6: Basic Design Steps

A 2x4 Karnaugh map for function Y1. The vertical axis is labeled 'w' with values 0 and 1. The horizontal axis is labeled 'y2y1' with values 00, 01, 11, and 10. The map contains 1s in the cells (w=0, y2y1=10) and (w=1, y2y1=00) and (w=1, y2y1=10). A horizontal bar is drawn under the 1s in the w=1 row, and a vertical bar is drawn to the left of the 1s in the y2y1=10 column.

$w \backslash y_2y_1$	00	01	11	10
0				1
1	1			1


$$Y_1 = w\bar{y}_1 + \bar{y}_1y_2$$

A 2x4 Karnaugh map for function Y2. The vertical axis is labeled 'w' with values 0 and 1. The horizontal axis is labeled 'y2y1' with values 00, 01, 11, and 10. The map contains 1s in the cells (w=0, y2y1=01) and (w=0, y2y1=10) and (w=1, y2y1=01) and (w=1, y2y1=10). Two vertical bars are drawn, one to the left of the 1s in the y2y1=01 column and one to the left of the 1s in the y2y1=10 column.

$w \backslash y_2y_1$	00	01	11	10
0		1		1
1		1		1

$$Y_2 = y_1\bar{y}_2 + \bar{y}_1y_2$$

Chapter 6: Basic Design Steps

 

Chapter 6: State-assignment Problem

	Present state	Next state		Outputs						
		$w = 0$	$w = 1$							
	y_2y_1	Y_2Y_1	Y_2Y_1	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	$Done$
A	00	00	0 1	0	0	0	0	0	0	0
B	01	10	1 0	0	0	1	0	0	1	0
C	10	11	1 1	1	0	0	1	0	0	0
D	11	00	0 0	0	1	0	0	1	0	1

Chapter 6: State-assignment Problem

A Karnaugh map for the function Y_1 with variables w , y_2 , and y_1 . The map is a 2x4 grid. The columns are labeled y_2y_1 as 00, 01, 11, and 10. The rows are labeled w as 0 and 1. The cells containing 1 are at (w=0, y_2y_1 =10) and (w=1, y_2y_1 =00). There are two groupings: a vertical group of two cells in the 10 column, and a horizontal group of two cells in the 00 column.

$w \backslash y_2y_1$	00	01	11	10
0				1
1	1			1

$$Y_1 = w\bar{y}_1 + \bar{y}_1y_2$$

A Karnaugh map for the function Y_2 with variables w , y_2 , and y_1 . The map is a 2x4 grid. The columns are labeled y_2y_1 as 00, 01, 11, and 10. The rows are labeled w as 0 and 1. The cells containing 1 are at (w=0, y_2y_1 =01), (w=0, y_2y_1 =10), (w=1, y_2y_1 =01), and (w=1, y_2y_1 =10). There are two groupings: a vertical group of two cells in the 01 column, and a vertical group of two cells in the 10 column.


$w \backslash y_2y_1$	00	01	11	10
0		1		1
1		1		1

$$Y_2 = y_1\bar{y}_2 + \bar{y}_1y_2$$


Chapter 6: State-assignment Problem

	Present state	Nextstate		Outputs						
		$w = 0$	$w = 1$							
	y_2y_1	Y_2Y_1	Y_2Y_1	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	$Done$
A	00	00	01	0	0	0	0	0	0	0
B	01	11	11	0	0	1	0	0	1	0
C	11	10	10	1	0	0	1	0	0	0
D	10	00	00	0	1	0	0	1	0	1

Chapter 6: State-assignment Problem

 


$$Y_1 = w\bar{y}_2 + y_1\bar{y}_2$$

 


$$Y_2 = y_1$$


Chapter 6: Mealy State Model

 

Chapter 6: Mealy State Model

 

Chapter 6: Design of FSMs Using CAD Tools

 

Chapter 6: Design of FSMs Using CAD Tools

```
module control (Clock, Resetn, w, R1in, R1out, R2in, R2out, R3in,
R3out,Done);
    input Clock, Resetn, w;
    output R1in, R1out, R2in, R2out, R3in, R3out, Done;
    reg [2:1] y, Y;
    parameter [2:1] A = 2'b00, B = 2'b01, C = 2'b10, D = 2'b11;


    // Define the next state combinational circuit
    always @(w, y)
        case (y)
            A: if (w) Y = B;
               else Y = A;
            B: Y = C;
            C: Y = D;
            D: Y = A;
        endcase

    // Define the sequential block
    always @(negedge Resetn, posedge Clock)
        if (Resetn == 0) y <= A;
        else y <= Y;

    // Define outputs
    assign R2out = (y == B);
    assign R3in = (y == B);
    assign R1out = (y == C);
    assign R2in = (y == C);
    assign R3out = (y == D);
    assign R1in = (y == D);
    assign Done = (y == D);

endmodule
```

Chapter 6: Verilog for a Mealy Machine

 

Present state	Next state		Output z	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
A	A	B	0	0
B	A	B	0	1

Chapter 6: Verilog for a Mealy Machine

```
module mealy (Clock, Resetn, w, z);
    input Clock, Resetn, w;
    output reg z;
    reg y, Y;
    parameter A = 1'b0, B = 1'b1;

    // Define the next state and output combinational circuits
    always @(w, y)
        case (y)
            A: if (w)
                begin
                    z = 0;
                    Y = B;
                end
                else
                begin
                    z = 0;
                    Y = A;
                end
            B: if (w)
                begin
                    z = 1;
                    Y = B;
                end
                else
                begin
                    z = 0;
                    Y = A;
                end
        endcase

    // Define the sequential block
    always @(negedge Resetn, posedge Clock)
        if (Resetn == 0) y <= A;
        else y <= Y;
endmodule
```

Chapter 6: State Minimization

Present state	Next state		Outputz	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
A	B	C	0	0
B	D	—	0	—
C	F	E	0	1
D	B	G	0	0
E	F	C	0	1
F	E	D	0	1
G	F	—	0	—

Chapter 6: State Minimization

Present state	Next state		Outputz	
	w = 0	w = 1	w = 0	w = 1
A	B	C	0	0
B	D	—	0	—
C	F	E	0	1
D	B	G	0	0
E	F	C	0	1
F	E	D	0	1
G	F	—	0	—

Assume unspecified outputs are 0:

$$P_1 = (ABCDEFGG)$$

Chapter 6: State Minimization

Present state	Next state		Outputz	
	w = 0	w = 1	w = 0	w = 1
A	B	C	0	0
B	D	—	0	—
C	F	E	0	1
D	B	G	0	0
E	F	C	0	1
F	E	D	0	1
G	F	—	0	—

Assume unspecified outputs are 0:

$$P_1 = (ABCDEFGG)$$

$$P_2 = (ABDG)(CEF)$$

Chapter 6: State Minimization

Present state	Next state		Outputz	
	w = 0	w = 1	w = 0	w = 1
A	B	C	0	0
B	D	—	0	—
C	F	E	0	1
D	B	G	0	0
E	F	C	0	1
F	E	D	0	1
G	F	—	0	—

Assume unspecified outputs are 0:

$$P_1 = (ABCDEFGG)$$

$$P_2 = (ABDG)(CEF)$$

$$P_3 = (AB)(D)(G)(CE)(F)$$

Chapter 6: State Minimization

Present state	Next state		Outputz	
	w = 0	w = 1	w = 0	w = 1
A	B	C	0	0
B	D	—	0	—
C	F	E	0	1
D	B	G	0	0
E	F	C	0	1
F	E	D	0	1
G	F	—	0	—

Assume unspecified outputs are 0:

$$P_1 = (ABCDEFGG)$$

$$P_2 = (ABDG)(CEF)$$

$$P_3 = (AB)(D)(G)(CE)(F)$$

$$P_4 = (A)(B)(D)(G)(CE)(F)$$

Chapter 6: State Minimization

Present state	Next state		Outputz	
	w = 0	w = 1	w = 0	w = 1
A	B	C	0	0
B	D	—	0	—
C	F	E	0	1
D	B	G	0	0
E	F	C	0	1
F	E	D	0	1
G	F	—	0	—

Assume unspecified outputs are 0:

$$P_1 = (ABCDEFGG)$$

$$P_2 = (ABDG)(CEF)$$

$$P_3 = (AB)(D)(G)(CE)(F)$$

$$P_4 = (A)(B)(D)(G)(CE)(F)$$

$$P_5 = (A)(B)(D)(G)(CE)(F)$$

Chapter 6: State Minimization

Present state	Next state		Outputz	
	w = 0	w = 1	w = 0	w = 1
A	B	C	0	0
B	D	—	0	—
C	F	E	0	1
D	B	G	0	0
E	F	C	0	1
F	E	D	0	1
G	F	—	0	—

Assume unspecified outputs are 1:

$$P_1 = (ABCDEFGG)$$

Chapter 6: State Minimization

Present state	Next state		Outputz	
	w = 0	w = 1	w = 0	w = 1
A	B	C	0	0
B	D	—	0	—
C	F	E	0	1
D	B	G	0	0
E	F	C	0	1
F	E	D	0	1
G	F	—	0	—

Assume unspecified outputs are 1:

$$P_1 = (ABCDEF G)$$

$$P_2 = (AD)(BCEFG)$$

Chapter 6: State Minimization

Present state	Next state		Outputz	
	w = 0	w = 1	w = 0	w = 1
A	B	C	0	0
B	D	—	0	—
C	F	E	0	1
D	B	G	0	0
E	F	C	0	1
F	E	D	0	1
G	F	—	0	—

Assume unspecified outputs are 1:

$$P_1 = (ABCDEFGG)$$

$$P_2 = (AD)(BCEFG)$$

$$P_3 = (AD)(B)(CEFG)$$

Chapter 6: State Minimization

Present state	Next state		Outputz	
	w = 0	w = 1	w = 0	w = 1
A	B	C	0	0
B	D	—	0	—
C	F	E	0	1
D	B	G	0	0
E	F	C	0	1
F	E	D	0	1
G	F	—	0	—

Assume unspecified outputs are 1:

$$P_1 = (ABCDEF G)$$

$$P_2 = (AD)(BCEFG)$$

$$P_3 = (AD)(B)(CEFG)$$

$$P_4 = (AD)(B)(CEG)(F)$$

Chapter 6: State Minimization

Present state	Next state		Outputz	
	w = 0	w = 1	w = 0	w = 1
A	B	C	0	0
B	D	—	0	—
C	F	E	0	1
D	B	G	0	0
E	F	C	0	1
F	E	D	0	1
G	F	—	0	—

Assume unspecified outputs are 1:

$$P_1 = (ABCDEFG)$$


$$P_2 = (AD)(BCEFG)$$

$$P_3 = (AD)(B)(CEFG)$$


$$P_4 = (AD)(B)(CEG)(F)$$

$$P_5 = (AD)(B)(CEG)(F)$$


Chapter 6: ASM Charts

 

(a) State box


 


(b) Decision box


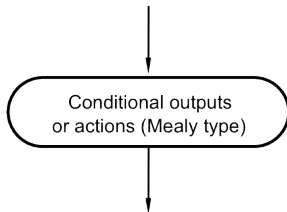


(c) Conditional output box


Chapter 6: ASM Charts

  

Chapter 6: ASM Charts

  


Reaction-timer Circuit

 

(c) Push-button switch, LED, and 7-segment displays


ASM Chart for the Reaction-timer Circuit

 

Verilog Testbenches (Sequential)

```
`timescale 1ms / 1ns
module test_reaction_timer;
    // Inputs
    reg Clock;
    reg Reset;
    reg w;
    reg Pushn;
    // Outputs
    wire LEDn;
    wire [3:0] BCD1, BCD0;
    // Instantiate the Unit Under Test (UUT)
    reaction uut (
        .Clock(Clock),
        .Reset(Reset),
        .w(w),
        .Pushn(Pushn),
        .LEDn(LEDn),
        .BCD1(BCD1),
        .BCD0(BCD0)
    );
```

Simulation for a Reaction-timer

 

Verilog Testbenches (Sequential)

initial begin

```
$display("Simulations Begins...");  
Clock = 0;  
Reset = 1;  
w = 0;  
Pushn = 1;  
#10  
Reset = 0;  
#15  
w = 1;  
#10  
w = 0;  
#170  
Pushn = 0;
```

end

always

```
#5 Clock <= ~Clock;
```

Verilog Testbenches (Sequential)

```
always@(negedge Clock)  
  if (Pushn == 0 && Ledn == 1)  
    begin  
      if (!(BCD1 == 1 && BCD0 == 8))  
        $display("Wrong Count");  
        $display("... Simulations Ends");  
    end  
endmodule
```