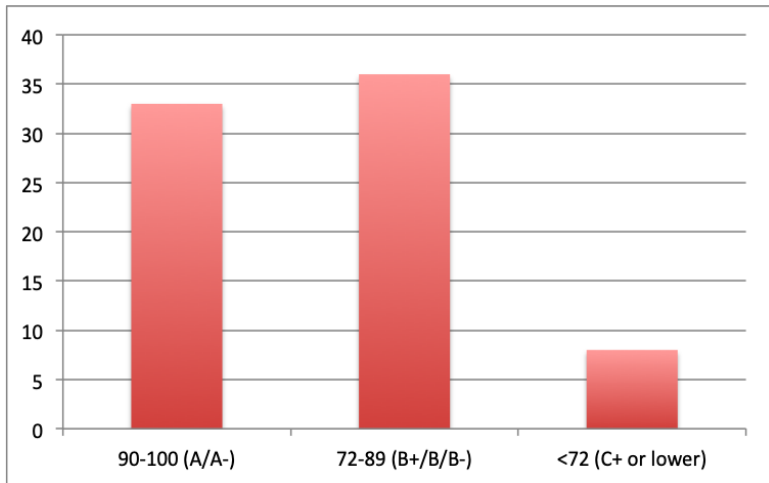


ECE/CS 3700: Fundamentals of Digital System Design

Chris J. Myers


Midterm 2 Solution

Midterm 2 Statistics



Average - 84.8
Standard deviation - 11.6

1(a) ASM Charts (Bhawna)

 

Perfect ASM : 15 pts, Logical flow correct, but wrong modules: 12 pts
Logical flow correct/missing output: 10 pts, Partial correct logical flow: 8 pts

1(b) Behavioral Verilog (Bhawna)

```
module FSM(input Clock, Resetn, c, t, s)
  input Clock, Resetn, c, t; // 2 points
  output s;
  reg [2,1] PS, NS;
  parameter [2:1] GR = 2'b00, YR = 2'b01, RG = 2'b10, RY = 2'b11;
  always@(posedge Clock, negedge Resetn) // 3 points
    if (Resetn) PS <= GR; else PS <= NS;
  always@(c,t,PS) // 5 pts for NS Logic, 5 pts for output
  case(PS)
    GR: if (c == 0) begin NS=GR; s = 0; end
    else begin NS=YR; s=1; end
    YR: if (t == 0) begin NS=YR; s = 0; end
    else begin NS=RG; s=0; end
    RG: if (c == 1) begin NS=RG; s = 0; end
    else begin NS=RY; s=1; end
    RY: if (t == 0) begin NS=RY; s = 0; end
    else begin NS=GR; s=0; end
  endcase
endmodule
```

1(c) Verilog Testbenches (Hari)

```
module testFSM;
  // Inputs
  reg Clock, Resetn, c,t; // 2 points
  // Outputs
  wire s; // 1 point
  // Instantiate the Unit Under Test (UUT)
  FSM uut ( .Clock(Clock), .Resetn(Resetn), .c(c), .t(t), .s(s) );
  initial begin
    Clock = 0; // 2 pts for initialization
    Resetn = 0; c = 0; t = 0; #12;
    Resetn = 1; #10
    c = 1; #10 // 4 pts for tests
    t = 1; #10
    t = 0; #10
    c = 0; #10
  end
  always #5 Clock = ~Clock; // 3 points for clock
  always@(negedge Clock) // 3 points for self-check
  // self-checking code here
```

1(d) Logic Minimization (Ke)

Present State $y_1 y_0$	Next State (Y_1, Y_0)				Output s			
	ct=00	ct=01	ct=10	ct=11	ct=00	ct=01	ct=10	ct=11
00	00	00	01	01	0	0	1	1
01	01	10	01	10	0	0	0	0
10	11	11	10	10	1	1	0	0
11	11	00	11	00	0	0	0	0

2 points for the correct state assignment table.

1(d) Logic Minimization (Ke)

		<i>ct</i>			
		00	01	11	10
$y_1 y_0$	00	0	0	0	0
	01	0	1	1	0
	11	1	0	0	1
	10	1	1	1	1

Y_1 (4pts)

		<i>ct</i>			
		00	01	11	10
$y_1 y_0$	00	0	0	1	1
	01	1	0	0	1
	11	1	0	0	1
	10	1	1	0	0

Y_0 (4pts)

		<i>ct</i>			
		00	01	11	10
$y_1 y_0$	00	0	0	1	1
	01	0	0	0	0
	11	0	0	0	0
	10	1	1	0	0


s (4pts)

$$Y_1 = t\bar{y}_1 y_0 + \bar{t}y_1 + y_1 \bar{y}_0 \text{ (2pts)}$$

$$Y_0 = c\bar{y}_1 \bar{y}_0 + \bar{t}y_0 + \bar{c}y_1 \bar{y}_0 \text{ (2pts)}$$

$$s = c\bar{y}_1 \bar{y}_0 + \bar{c}y_1 \bar{y}_0 \text{ (2pts)}$$

1(e) Timing Analysis (Chris)

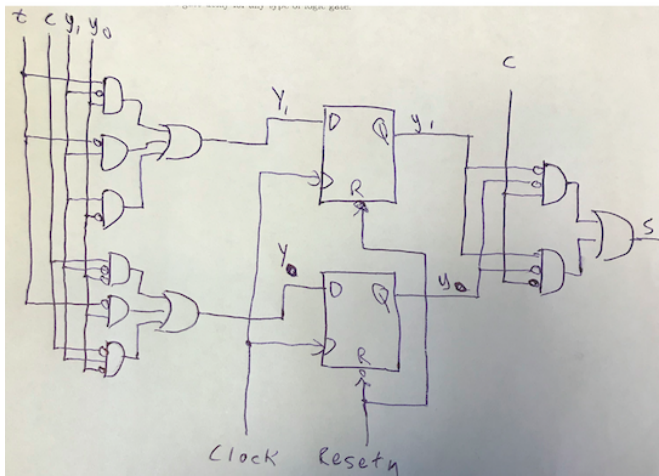

$$f_{max} = 1/T_{min} = 1/(t_{path} + t_{su} + t_{cQ}) = 1/(3.2ns + 0.8ns + 1ns) \approx 200MHz$$

Schematic (10pt), Timing (5pts).

2. State Reduction (Harsha)

$$P_1 = (S0, S1, S2, S3, S4, S5, S6) \quad (1 \text{ point})$$

$$P_2 = (S0, S1, S2, S4, S5, S6)(S3) \quad (5 \text{ points})$$

$$P_3 = (S0, S1, S2, S5, S6)(S3)(S4) \quad (5 \text{ points})$$

$$P_4 = (S0, S1, S2)(S5, S6)(S3)(S4) \quad (5 \text{ points})$$

Present State	Next state		Output z
	w = 0	w = 1	
S0	S5	S0	1
S3	S3	S0	0
S4	S3	S4	1
S5	S5	S4	1

(4 points)