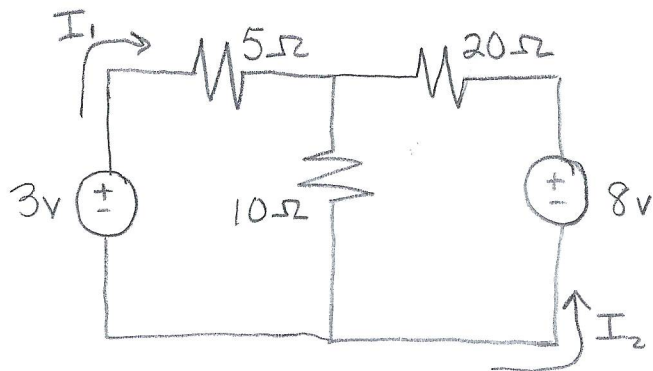


Matrix Math

Systems of equations can be solved using matrices. We'll start with a simple example using the following two loop circuit:



To find I_1 & I_2 , we use KVL (Kirchoff's Voltage Law) to obtain the following equations:

$$\Rightarrow (5\Omega + 10\Omega)(I_1) + (10\Omega)(I_2) = 3V$$

$$(10\Omega)(I_1) + (20\Omega + 10\Omega)(I_2) = 8V$$

$$\Rightarrow \begin{matrix} \text{elements of } A & \begin{matrix} \nearrow & \searrow \\ (15\Omega)(I_1) & + & (10\Omega)(I_2) & = & 3V \\ \nwarrow & \nearrow \\ (10\Omega)(I_1) & + & (30\Omega)(I_2) & = & 8V \end{matrix} & \begin{matrix} \nwarrow & \nearrow \\ & \text{elements of } b \end{matrix} \end{matrix}$$

This can be solved using a 2×2 matrix of the form:
 $Ax = b$ where

$$A = \text{coefficient matrix} = \begin{bmatrix} a & b \\ c & d \end{bmatrix}$$

$$\Rightarrow A = \begin{bmatrix} 15 & 10 \\ 10 & 30 \end{bmatrix} \text{ for this problem}$$

x = unknowns we're solving for
 $\Rightarrow x = \begin{Bmatrix} I_1 \\ I_2 \end{Bmatrix}$ for this problem

b = right-hand side values
 $\Rightarrow b = \begin{Bmatrix} 3 \\ 8 \end{Bmatrix}$ for this problem

To solve for x in $Ax=b$, multiply both sides by inverse of A , written as A^{-1}

$$\Rightarrow A^{-1} \cdot Ax = A^{-1} \cdot b$$

$$\Rightarrow A^{-1} \cdot A = I, \text{ identity matrix}$$

$$\Rightarrow (I)(x) = A^{-1} \cdot b$$

$$\text{Since } (I)(x) = x \Rightarrow x = A^{-1} \cdot b$$

$$\text{For } A = \begin{bmatrix} a & b \\ c & d \end{bmatrix}, A^{-1} = \frac{1}{ad-bc} \begin{bmatrix} d & -b \\ -c & a \end{bmatrix}$$

Now to solve $x = A^{-1} \cdot b$

$$\Rightarrow x = \frac{1}{\underset{a}{15} \underset{d}{30} - \underset{b}{10} \underset{c}{10}} \begin{bmatrix} 30 & -10 \\ -10 & 15 \end{bmatrix} \cdot b$$

$$= \frac{1}{450 - 100} \begin{bmatrix} 30 & -10 \\ -10 & 15 \end{bmatrix} \cdot \begin{Bmatrix} 3 \\ 8 \end{Bmatrix}$$

$$= \frac{1}{350} \begin{bmatrix} 30 & -10 \\ -10 & 15 \end{bmatrix} \cdot \begin{Bmatrix} 3 \\ 8 \end{Bmatrix}$$

$$= \begin{bmatrix} 3/35 & -1/35 \\ -1/35 & 3/70 \end{bmatrix} \cdot \begin{Bmatrix} 3 \\ 8 \end{Bmatrix}$$

$$\Rightarrow X = \begin{Bmatrix} (3/35)(3) + (-1/35)(8) \\ (-1/35)(3) + (3/70)(8) \end{Bmatrix} = \begin{Bmatrix} 1/35 \\ 9/35 \end{Bmatrix} = \begin{Bmatrix} I_1 \\ I_2 \end{Bmatrix}$$

$$\Rightarrow I_1 = 1/35 = 0.029 \text{ A}$$


$$I_2 = 9/35 = 0.257 \text{ A}$$

Plug these values into the original equation to check your answer

$$(15\Omega)(I_1) + (10\Omega)(I_2) = 3\text{V}$$

$$(15\Omega)(0.029\text{A}) + (10\Omega)(0.257\text{A}) = 3.00\text{V} \checkmark$$

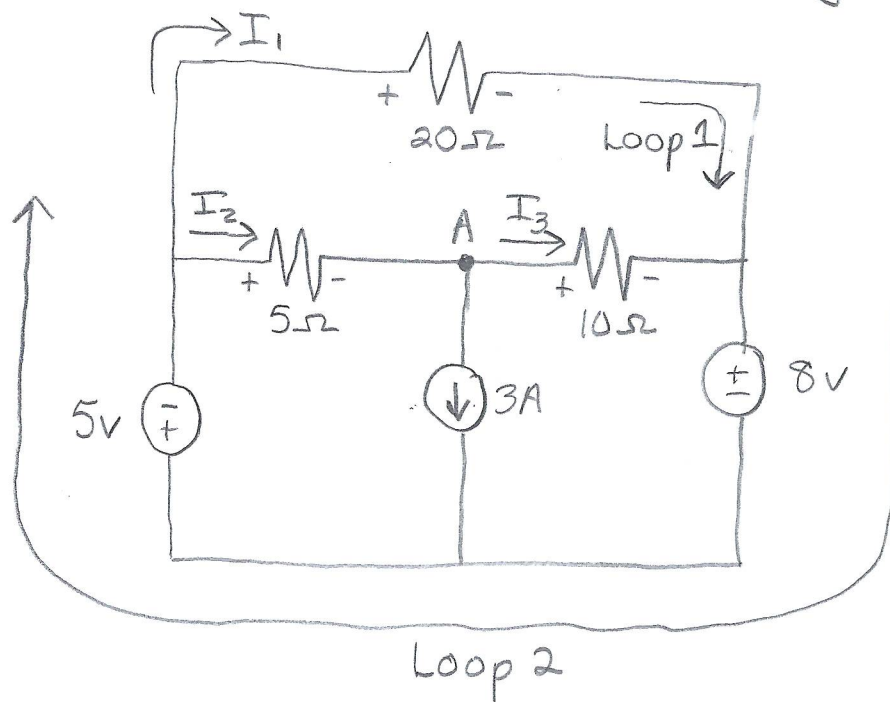Larger systems of equations require larger matrices. These are more easily solved using a calculator or Matlab. Consider the following circuit:



To solve for $I_1, I_2, + I_3$, use KVL + KCL to write equations:

$$\text{Loop 1: } (20\Omega)(I_1) - (10\Omega)(I_3) - (5\Omega)(I_2) = 0 \text{ (KVL)}$$

$$\text{Loop 2: } (20\Omega)(I_1) + 8V + 5V = 0 \text{ (KVL)}$$

$$\text{Node A: } I_2 - 3A - I_3 = 0 \text{ (KCL)}$$

$\Rightarrow$ 3 equations, 3 unknowns

Group unknowns in corresponding columns

$$\Rightarrow 20I_1 - 5I_2 - 10I_3 = 0$$

$$20I_1 = -8 - 5 = -13$$

$$I_2 - I_3 = 3$$

Now form the matrices:

$$\begin{array}{ccc} \begin{matrix} A \\ \left[\begin{array}{ccc} 20 & -5 & -10 \\ 20 & 0 & 0 \\ 0 & 1 & -1 \end{array} \right] \\ \text{coefficients} \end{matrix} & \begin{matrix} X \\ \left\{ \begin{array}{c} I_1 \\ I_2 \\ I_3 \end{array} \right\} \\ \text{unknowns} \end{matrix} & = \begin{matrix} b \\ \left\{ \begin{array}{c} 0 \\ -13 \\ 3 \end{array} \right\} \\ \text{right hand side} \end{matrix} \end{array}$$

As before:

$$X = A^{-1} \cdot b$$

Use Matlab to create a new script file to calculate:

Matlab code

- 1) Clear all;
- 2) % Define coefficient matrix A in []
- 3) % Separate elements in a row by commas
- 4) % Separate rows by semicolons
- 5) $A = [20, -5, -10; 20, 0, 0; 0, 1, -1];$
- 6) % Define right-hand side matrix b in []
- 7) $b = [0, -13, 3];$
- 8) % Solve for I_1, I_2, I_3
- 9) % Leave out the semicolon for result
- 10) % to show in Matlab window
- 11) $I = A^{-1} * b$
- 12) % This produces the following display:

$I =$

-0.6500

1.1333

-1.8666

$$\Rightarrow I_1 = -0.65, I_2 = 1.13, I_3 = -1.86$$

Plug these values into Loop 1 equation to check:

$$(20)(-0.65) - (10)(-1.867) - (5)(1.133) = 0.005 \approx 0 \checkmark$$

Using the signs (+/-) for calculated values, we can redraw the circuit accurately:

