

Problem 4.40 Develop a block-diagram representation for the circuit in Fig. P4.40 for $v_{s2} = v_{s3} = 0$ and:

- (a) $R_1 = \text{open circuit}$.
- (b) $R_1 = 10 \text{ k}\Omega$.

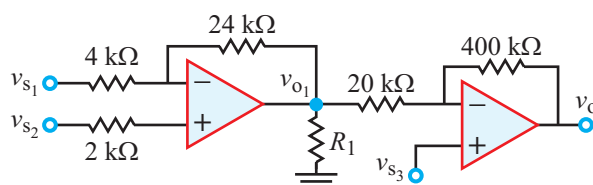


Figure P4.40: Circuit for Problem 4.40.

Solution: (a) For $v_{s2} = 0$, the first stage is an inverting amplifier with

$$v_{o1} = -\frac{24}{4} v_{s1} = -6v_{s1}.$$

For $v_{s3} = 0$, the second stage is also an inverting amplifier, with

$$v_o = -\frac{400}{20} v_{o1} = -20v_{o1}$$



(b) R_1 has no bearing on the solution, so long as $R_1 \gg R_o$, where R_o is the output resistance of the op amp, which typically is on the order of 10–100 Ω .

Hence, for $R_1 = 10 \text{ k}\Omega$, the solution in (a) remains valid.